

REET202

HINES & TRANSFORMERS

MODULE: 4

**Percentage and Per unit Impedance,
Regulation, Parallel Operation of
Transformers**

Prepared By,

ADARSH SR

Asst. Professor

EEE Department

SCET Kodakara

Syllabus

ers –constructional details, principle of operation, EMF equation, convention, magnetising current, transformation ratio, phasor no load and on load, equivalent circuit, percentage and per unit regulation. Transformer losses and efficiency, condition for 7/A rating. Testing of transformers– polarity test, open circuit test, Sumpner's test – separation of losses, all day efficiency.Parallel transformers– numerical problems

Percentage and Per-unit values

The percentage of any quantity is defined as the ratio of actual value to the base or reference value in the same unit.

When the actual value is converted into per unit quantity by dividing the actual value by the chosen base value of the same dimension.

The per-unit value is dimensionless.

When the actual value is expressed in percentage, it can be called

$$\text{Unit Value} = \frac{\text{Actual Value}}{\text{Base Value}}$$

$$\text{Percentage Value} = \text{Per Unit Value} \times 100$$

Base and Per-unit Impedance

Actual voltage

Actual current

$$\text{Per-unit Impedance} = \frac{\text{Actual Impedance}}{\text{Base Impedance}}$$

$$\text{Base Impedance} = \frac{\text{Base Voltage}}{\text{Base Current}} = \frac{V_1}{I_1}$$

$$\text{Per-unit Impedance} = \frac{Z_{01}}{V_1 / I_1} = \frac{I_1 Z_{01}}{V_1}$$

$$\text{Impedance, \%Z} = \frac{I_1 Z_{01}}{V_1} \times 100$$

Base and Per-unit Impedance

$$\text{Per-unit Resistance} = \frac{r_{01}}{V_1 / I_1} = \frac{I_1 r_{01}}{V_1}$$

$$\text{Per-unit Resistance, \%r} = \frac{I_1 r_{01}}{V_1} \times 100$$

$$\text{Per-unit Reactance} = \frac{x_{01}}{V_1 / I_1} = \frac{I_1 x_{01}}{V_1}$$

$$\text{Per-unit Reactance, \%x} = \frac{I_1 x_{01}}{V_1} \times 100$$

Voltage Regulation

is loaded with a constant primary voltage, the secondary voltage decreases with an increase in load.

resistance and leakage reactance.

If the change in secondary terminal voltage from no-load to full-load secondary terminal voltage is called

voltage regulation, because a good transformer should maintain the secondary terminal voltage as constant as possible under all load conditions.

$$\text{Voltage regulation} = \frac{V_{2_{NL}} - V_2}{V_2}$$

$$\frac{I_1 r_{01} \cos \varphi \pm I_1 x_{01} \sin \varphi}{V_1} \times 100$$

+ : Lagging pf load

– : Leading pf load

$$\frac{I_2 r_{02} \cos \varphi \pm I_2 x_{02} \sin \varphi}{V_2} \times 100$$

Operation of Transformers

Load in excess of the rating of an existing transformer may be connected in parallel.

Notified while paralleling:

1. The transformer should be suitable for the voltage and frequency.


2. It should be properly connected with regard to

3. The primary and secondary should be identical. In transformers should have same transformation ratio.



4. Impedances should be equal

5. The equivalent leakage reactance to equivalent resistance should be same for all the transformers.

Operation of Transformers

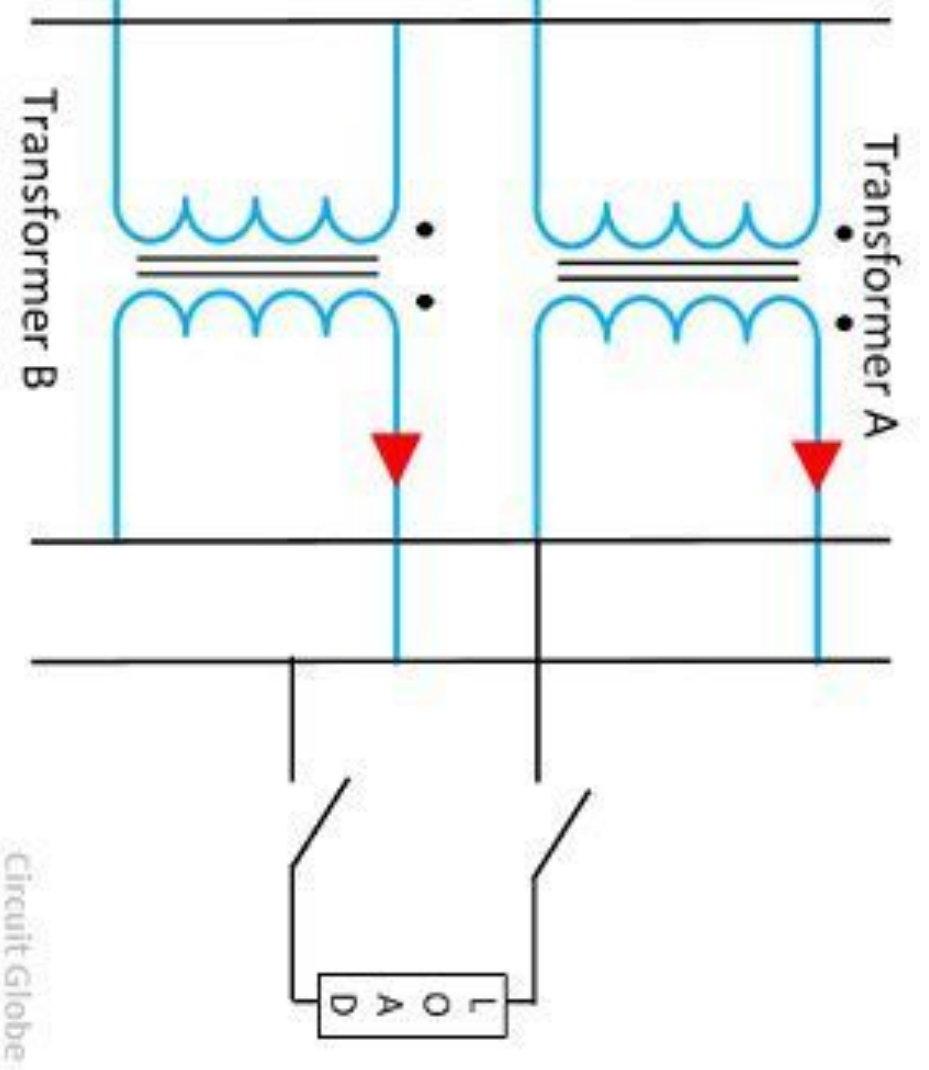

Operation of Transformers

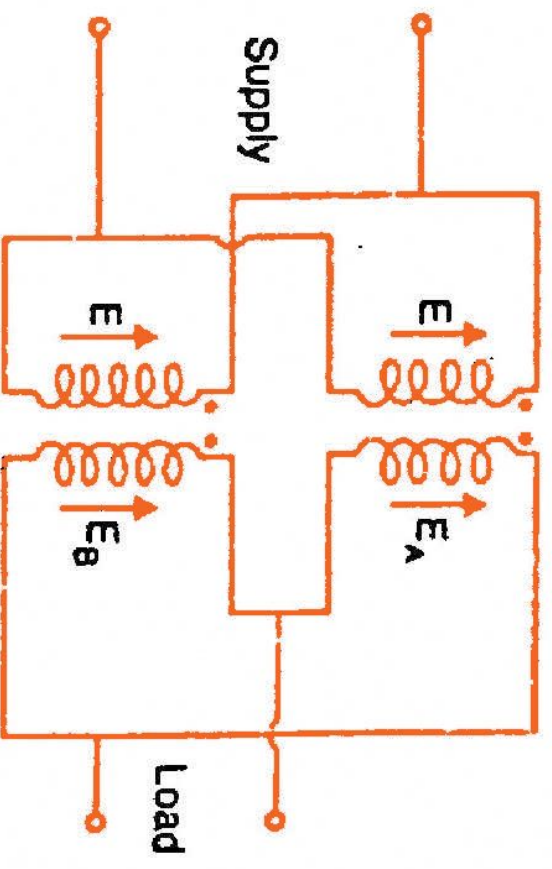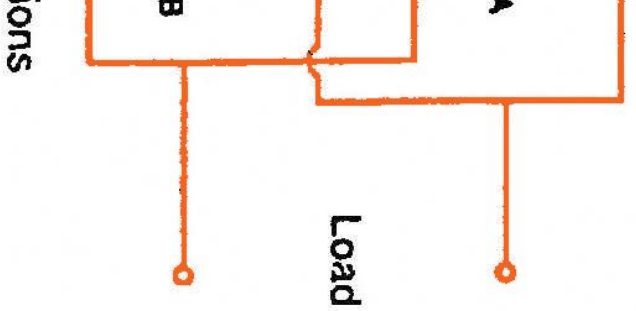

Wrong connections
(ii)