



Switch on the 3 phase supply. Adjust the autotransformer and apply rated voltage to the stator. Since the power factor of the induction motor under no load condition is generally less than 0.5, one wattmeter will show negative reading. Then switch off the supply and interchange the connections of the pressure coil (or current coil) of that wattmeter. Note down the ammeter, voltmeter and wattmeter readings at rated supply voltage. Switch of the supply.

B. BLOCKED ROTOR TEST

Make the connections as shown in figure.

Precautions:

- Keep the autotransformer in minimum voltage position
- Rotor is blocked by tightening the belt on the brake drum.

Switch on the 3 phase supply. Adjust the autotransformer so that rated current flows through ammeter. Take voltmeter, ammeter and wattmeter readings. (If any of the wattmeter reads negative, switch off the supply and interchange the connections of the pressure coil (or current coil) of that wattmeter and continue the above procedure). Switch off the supply.

C. STATOR RESISTANCE MEASUREMENT

Make the connections as shown in figure.

Precautions :

- Keep the rheostat in maximum resistance position

Switch on 30 V d.c. supply. Note down voltmeter and ammeter readings for different positions of rheostat. (Note: Resistance/phase = $\frac{3}{2}$ Delta resistance.)