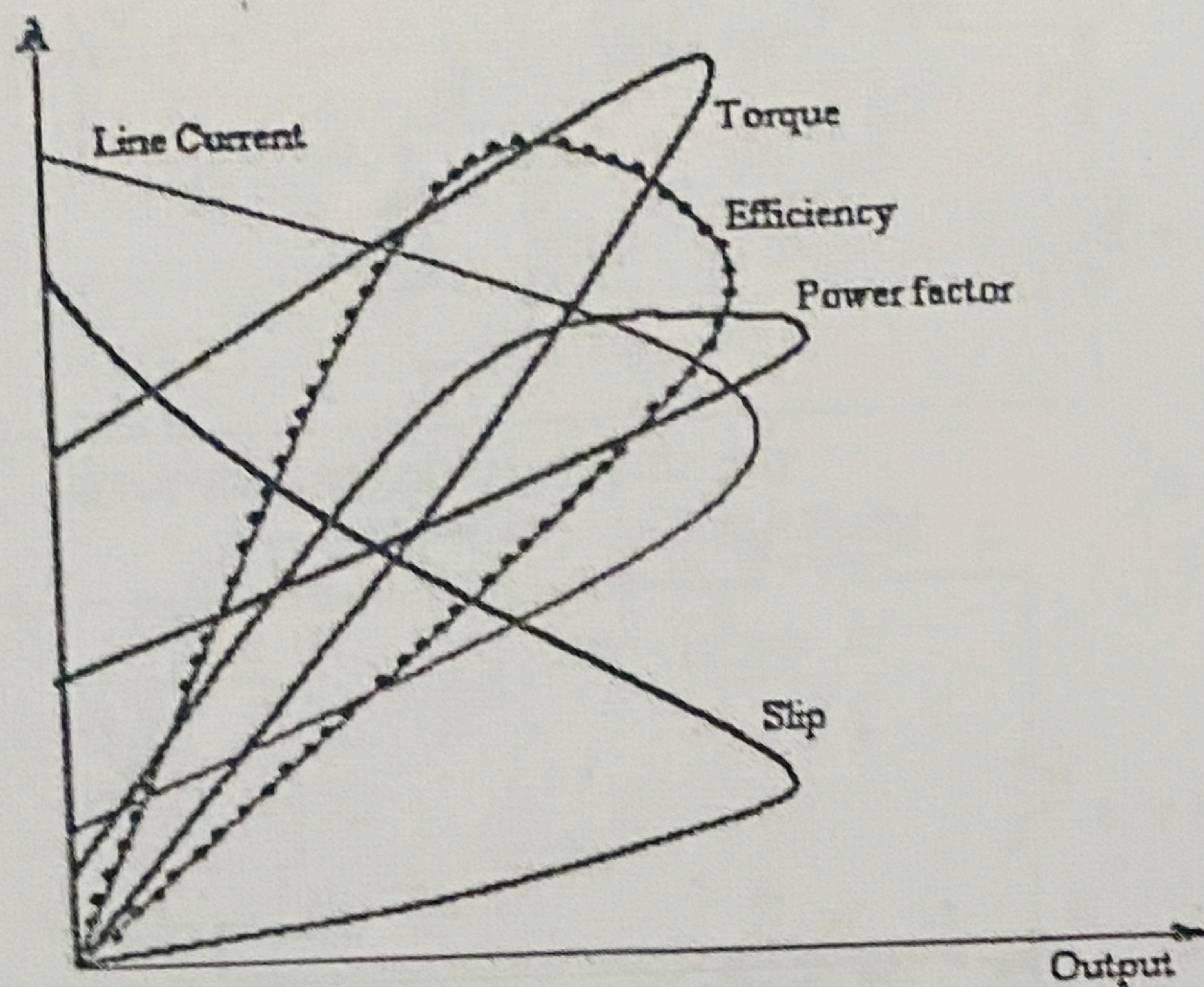




MODEL GRAPH - PERFORMANCE CHARACTERISTICS FROM CIRCLE DIAGRAM



EQUIVALENT CIRCUIT PARAMETERS

$$V_{oc} = \text{_____ V}, I_{oc} = \text{_____ A}, W_{oc} = \text{_____ W}$$

$$V_{sc} = \text{_____ V}, I_{sc} = \text{_____ A}, W_{sc} = \text{_____ W}$$

$$V_o = V_{oc} = \text{_____ V} \quad I_o = \frac{I_{oc}}{\sqrt{3}} = \text{_____ A}$$

$$V_s = V_{sc} = \text{_____ V} \quad I_s = \frac{I_{sc}}{\sqrt{3}} = \text{_____ A}$$

$$\cos \phi_0 = \left(\frac{W_{oc}}{3V_o I_o} \right) = \text{_____}$$

$$\sin \phi_0 = \text{_____}$$

$$R_c = \frac{V_o}{I_o \times \cos \phi_0} = \text{_____ } \Omega$$

$$X_m = \frac{V_o}{I_o \times \sin \phi_0} = \text{_____ } \Omega$$

$$Z_{01} = \frac{V_s}{I_s} = \text{_____ } \Omega$$

$$R_{01} = \frac{W_{sc}}{3I_s^2} = \text{_____ } \Omega$$

$$X_{01} = \sqrt{(Z_{01}^2 - R_{01}^2)} = \text{_____ } \Omega$$

$$R_1 = \frac{3}{2} \times 1.2 \times R_{dc} = 1.5 \times 1.2 \times \text{_____} = \text{_____ } \Omega$$

$$R'_2 = R_{01} - R_1 = \text{_____ } \Omega$$