




Keep the autotransformer at minimum voltage position.

Switch on the supply. Adjust the autotransformer and make the current equal to rated value. Note down the ammeter, voltmeter and wattmeter readings. Switch off the supply.

STATOR RESISTANCE MEASUREMENT

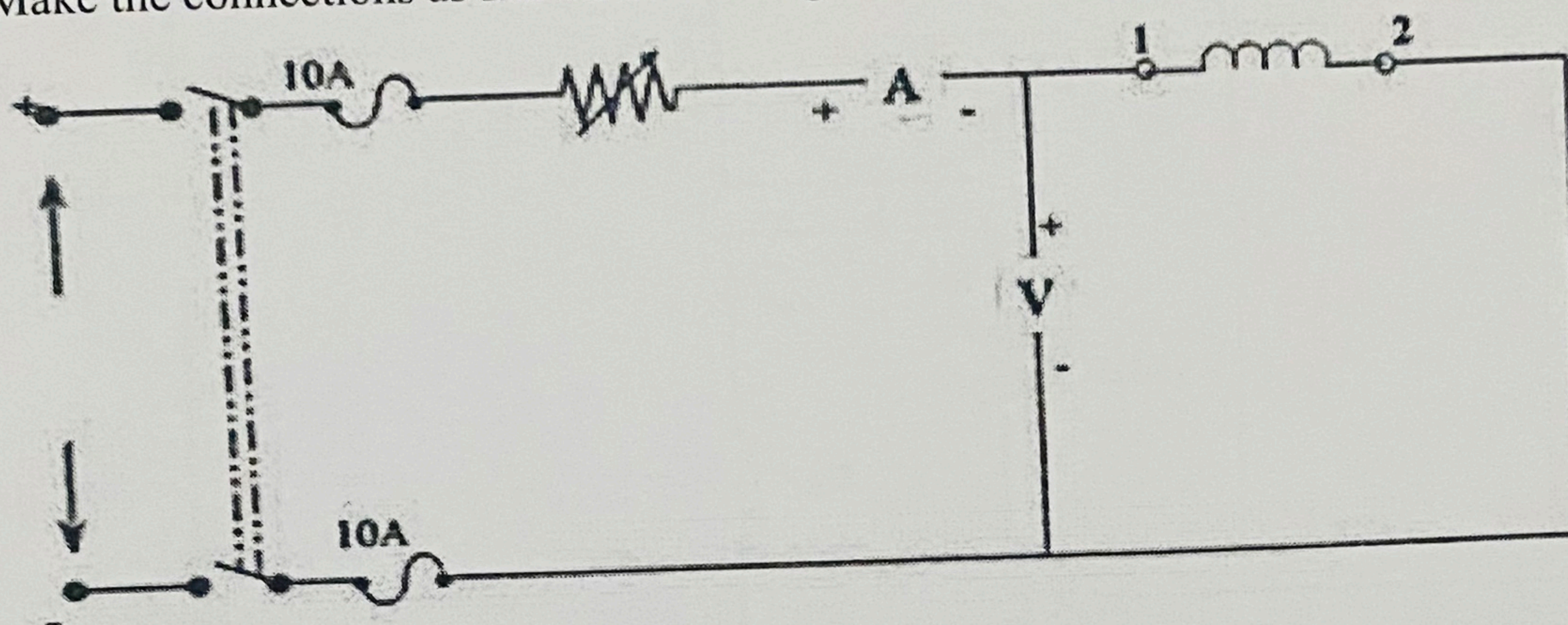Make the connections as shown in the diagram.



Precaution:

Keep the rheostat at maximum resistance position.

Switch on 30V dc. supply. Note down voltmeter and ammeter readings for different positions of rheostat. Switch off the supply.

TABULATION

No Load Test			Blocked Rotor Test		
V_o	I_o	W_o	V_{sc}	I_{sc}	W_{sc}

Stator Resistance Measurement			
S.No.	V (volts)	I (amps)	$R_{dc} = V/I$
1.			
2.			
3.			
4.			
R_{dc}			