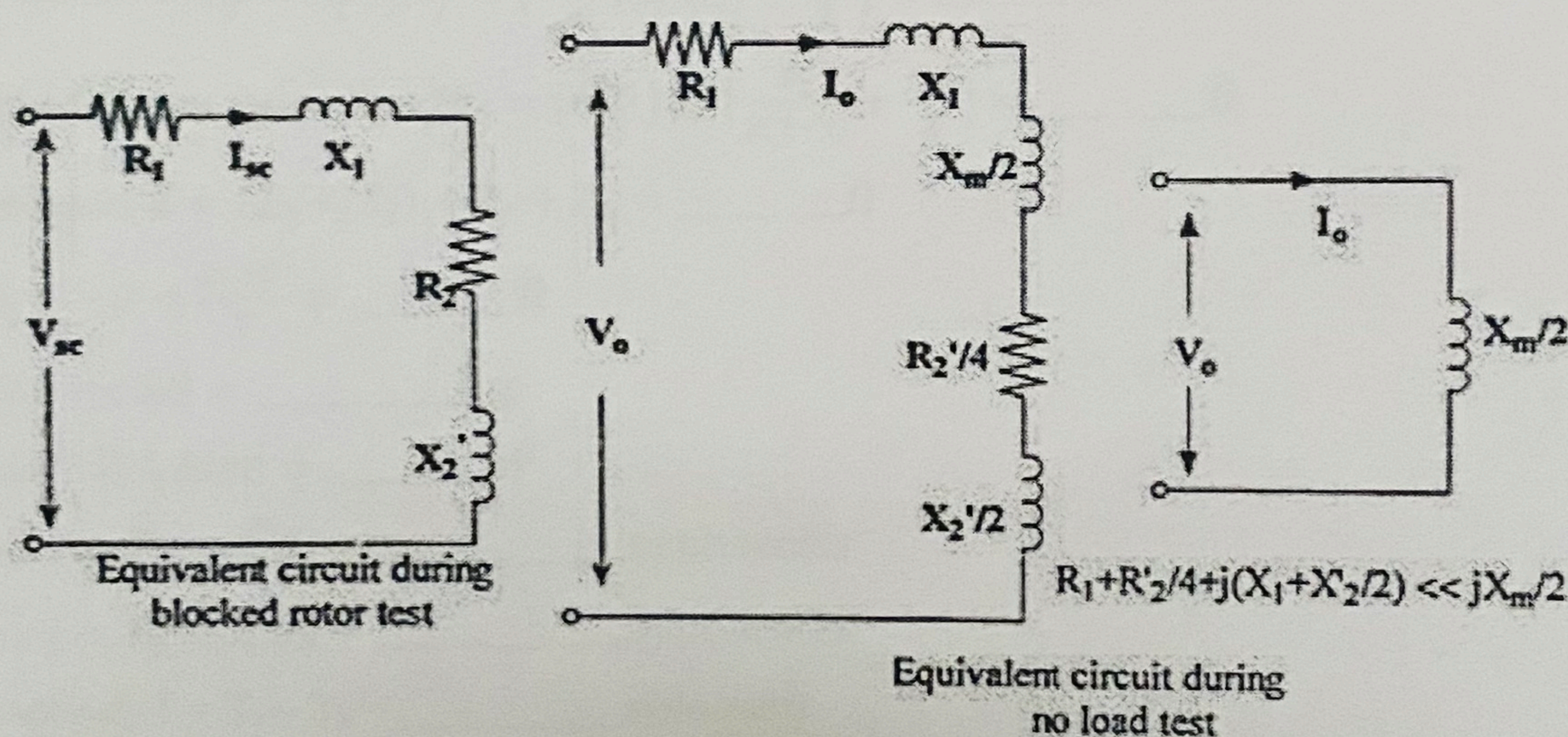
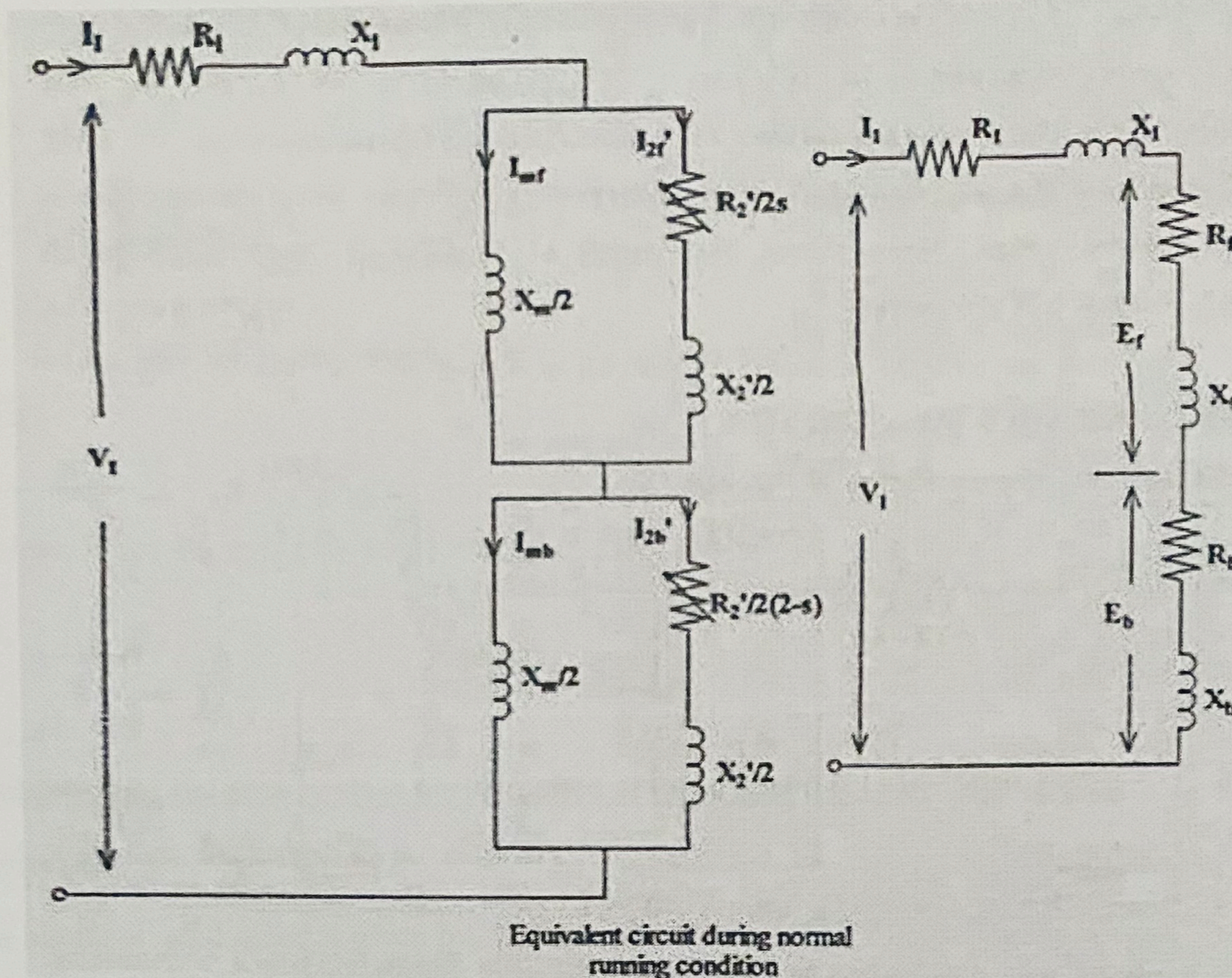




CALCULATION

EQUIVALENT CIRCUIT PARAMETERS

Blocked Rotor Test

$$V_{sc} = \text{_____ V,} \quad I_{sc} = \text{_____ A,} \quad W_{sc} = \text{_____ W}$$

$$\cos \phi_{sc} = \frac{W_{sc}}{V_{sc} I_{sc}} = \text{_____}$$

$$R_{sc} = R_1 + R_2' = \frac{W_{sc}}{I_{sc}^2} = \text{_____ } \Omega$$

$$R_{1dc} = \text{_____ } \Omega$$

$$R_1 = 1.2 \times R_{1dc} = \text{_____ } \Omega$$