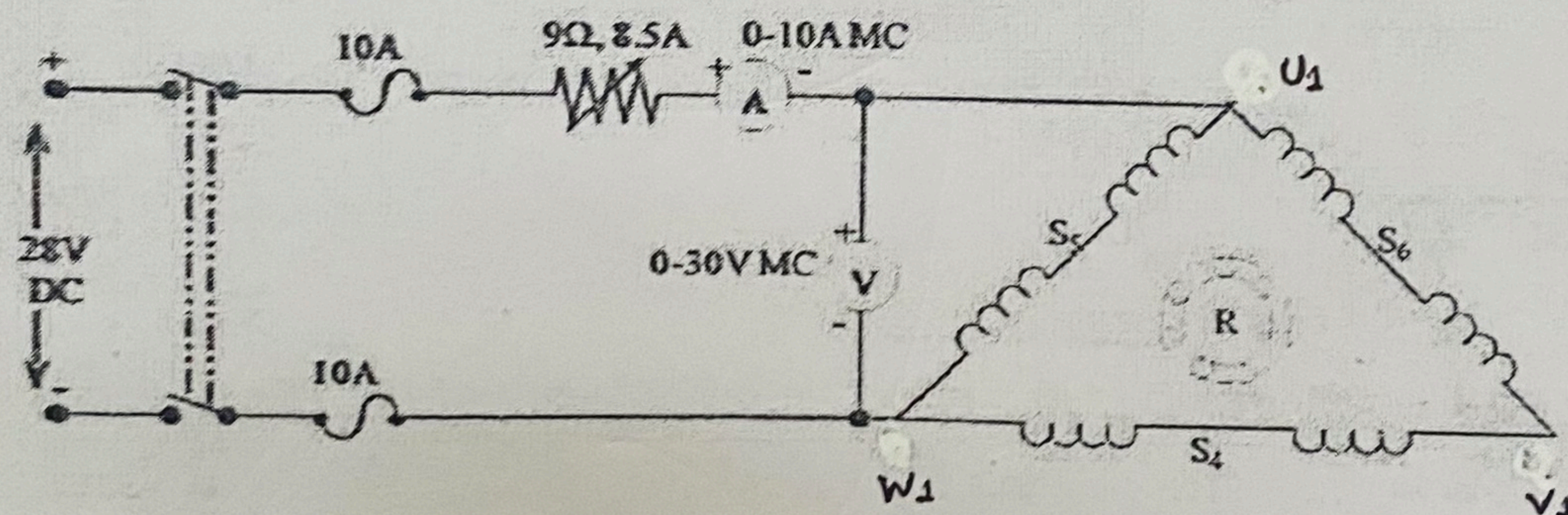


[illegible]

Make the connections as shown in figure.



Keep the rheostat in maximum resistance position

Switch on 30V d.c. supply. Note down voltmeter and ammeter readings for different positions of rheostat. (Note: For low speed connection Resistance/phase = $\frac{3}{2}$ Delta resistance, for high speed connection Resistance/phase = $\frac{3}{8}$ Delta resistance.)