



KTU NOTES

The learning companion.

**KTU STUDY MATERIALS | SYLLABUS | LIVE
NOTIFICATIONS | SOLVED QUESTION PAPER**

 Website: www.ktunotes.in


* Block diagram of a D.C power Supply

↳ Today almost every electronic device needs a DC supply for its smooth operation. These devices need to be operated within certain power limits. This required DC voltage or DC power is derived from single phase AC mains.

↳ A regulated power supply can convert AC to a constant DC. A regulated power supply is used to ensure that the output remains constant even if the input changes.

↳ Figure below shows the block diagram of a typical regulated DC power supply.

A DC power Supply

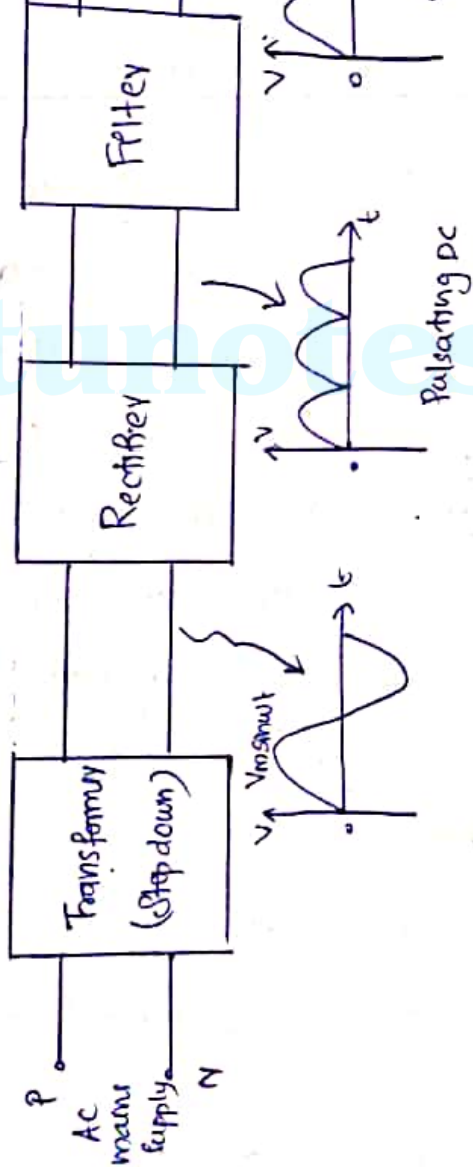

* Rectification

Rectifier is an electronic circuit of diodes which carries out the rectification. Rectification is the process of converting voltage or current into corresponding quantity.

* DC Filtration

The rectified voltage from the rectifier is a pulsating DC voltage having very high ripple. Different types of filters are used such as RC filter, LC filter, π type filter etc.

Linear voltage regulator, transistor series
Fixed and variable IC regulators (IC's)

* Rectifier


↳ Rectifiers are electronic ckt which
input ac signal in to pulsating DC

↳ Fan, heater, bulbs, air conditioner etc.
the help of ac signal. But there are some
which cannot be run with the help
such as mobile phones, toys, ~~etc~~ walk-man,
light torch light etc. These equipments
with the help of dc supply.


↳ As ac signal is generally available
equipments (electronic equipments), ac is


- ↳ Centre tap full wave rectifier
- ↳ Full wave bridge type rectifier

Op of half wave rectifier


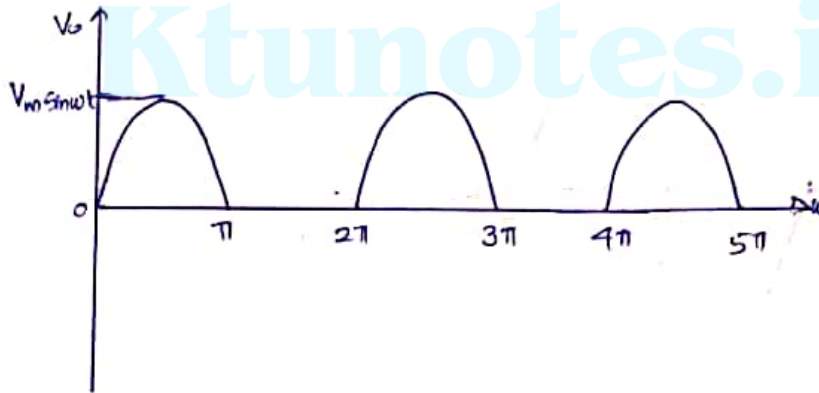


Op of full wave rectifier

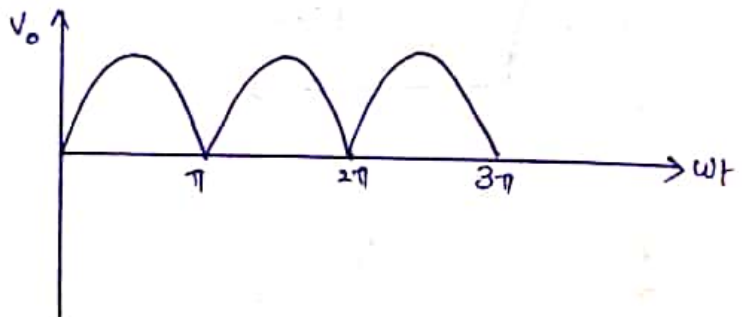

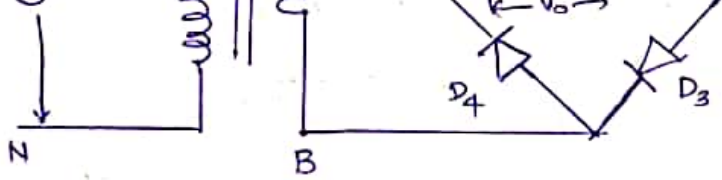

Waveforms

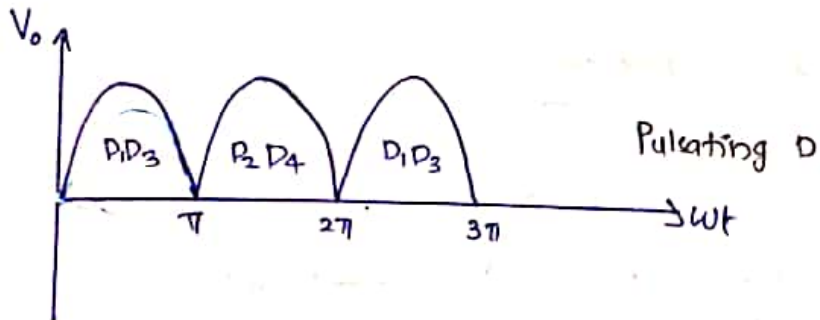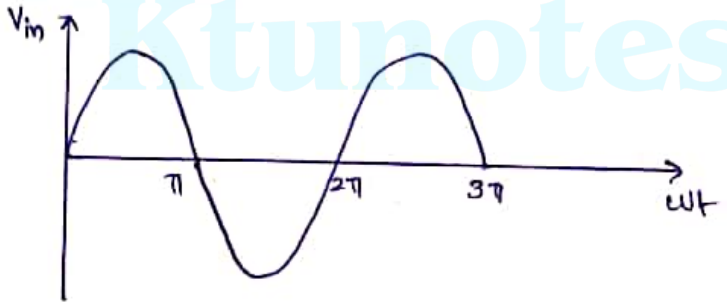

$$V_{avg} = \frac{2V_m}{\pi} = 0.636 V_m$$

transformer

↳ Between other two ends of the bridge resistor R_L is connected.

Working:

↳ During the first half cycle of ac:

↳ During the first half cycle of secondary the end 'A' of the secondary winding becomes w.r.t. other end 'B'.


↳ Now the diodes D_1 and D_3 are forward biased and hence the conventional current flows in the circuit across the R_L .

As a result the o/p voltage will be developed across R_L .

* During negative half cycle of ac:




1. During negative half cycle of second end A becomes -ve w.r.t the other end.

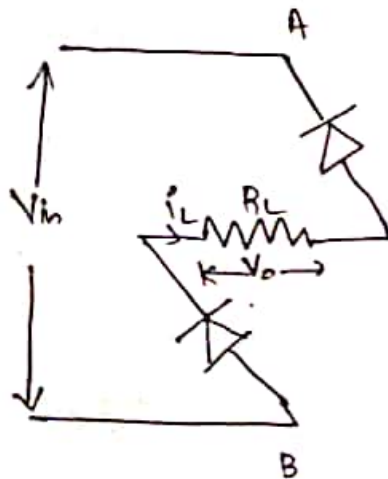2. Now the diodes D_2 and D_4 conduct in forward biasing. Hence the d/p voltage across R_L .



pure DC output voltage.

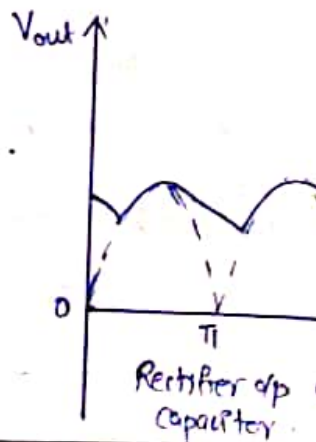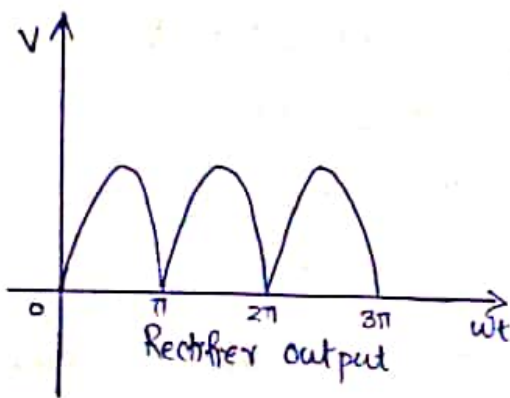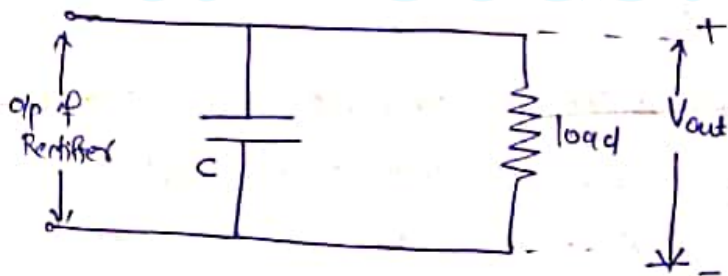↳ Ripple content from the dc voltage is
connecting an electrolytic capacitor in para
as shown below.




↳ Zener diode behaves just like a normal purpose diode consisting of a silicon and when biased in the forward direction is Anode positive with respect to its Cathode. It behaves just like a normal signal diode and carries rated current.

↳ However, unlike a conventional diode, it blocks any flow of current through it when reverse biased, that is the Cathode is positive than the Anode, as soon as the reverse voltage reaches a pre-determined value, the diode begins to conduct in the reverse direction.

↳ This happens when the voltage across the diode reaches its break down voltage or Zener voltage.

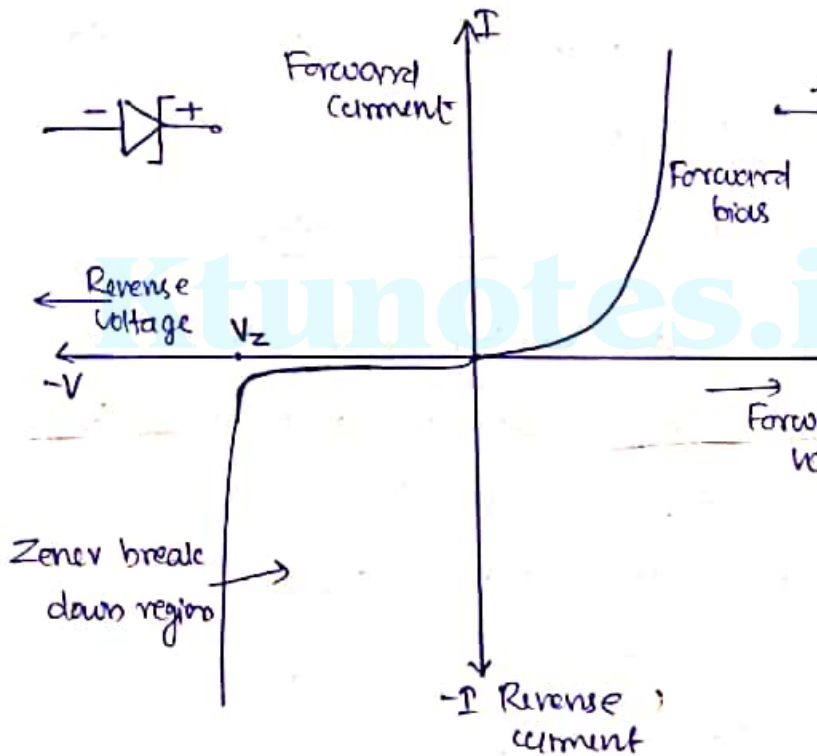↳ A reverse biased Zener diode exhibits a constant voltage across it after breakdown and the potential drop across it remains constant.




→ From the I-V characteristics curve can see that the Zener diode has a reverse bias characteristics of almost a negative voltage regardless of the value of

↳ This ability of the Zener diode to regulate voltage can be used to regulate or stabilise a source against supply or load variations.

* Zener diode as a voltage regulator.

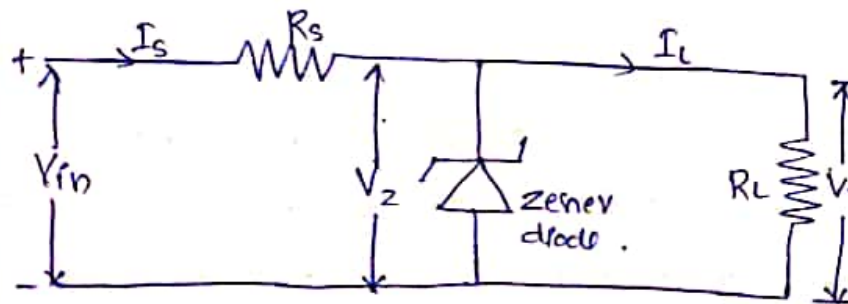↳ Because of the ability of a Zener diode to maintain a constant potential drop across it (during reverse breakdown) they are extensively used to produce a regulated voltage output. A simple voltage stabilizer circuit is shown below.



the Zener diode is connected with its cathode terminal connected to the positive rail of the supply so it is reverse biased and will be in its breakdown condition.

↳ Resistor R_s is selected so to limit the current flowing in the ckt.

↳ The load is connected in parallel with the diode, so the voltage across R_L is always same as the Zener voltage, ($V_R = V_Z$)

↳ Due to steep Zener diode characteristic near Zener breakdown, the voltage V_Z does not vary thereby the output voltage $V_o = V_Z$ irrespective of variation in load current and input voltage (V_{in}).


comfortably. This type of system is called
address system.

↳ It increases the loudness of a human
musical instrument or recorded music.

* Requirements of public address system

1. It must avoid the acoustic feedback.
2. Distribute the sound intensity uniformly.
3. Reduce reverberations.
4. It must use proper speaker orientation.
5. Select proper microphones and loud speakers.
6. It should create a sense of direction.
7. Loud speaker impedances should be properly matched.

Block Diagram.

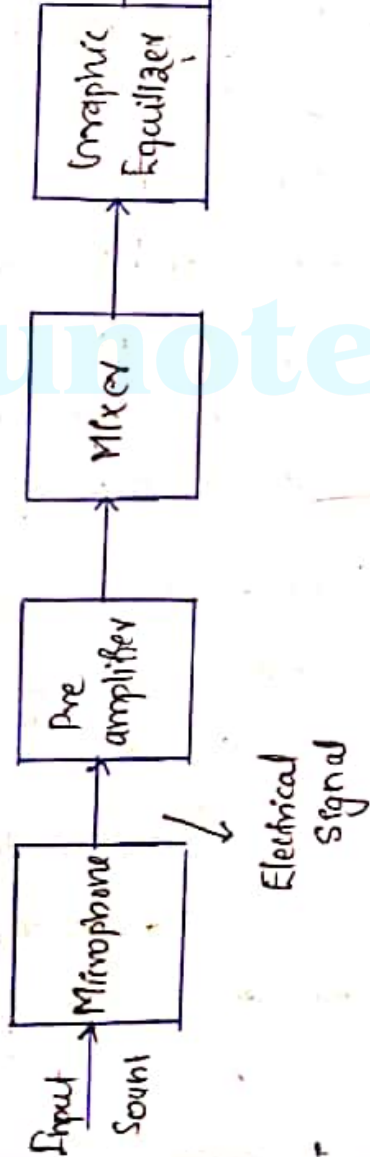

the amplitude of signal coming from the microphone for enabling for further processing.

(iii) Mixer : - The output of the microphone is fed to the mixer stage. The mixer stage isolates different channels from each other before they are fed to the amplifier.

(iv) Graphic Equalizer : - It is used to balance between different frequency within an electrical signal.

(v) Power amplifier : - Power of the electrical signal is boosted by power amplifier so that it is strong enough to drive the loud speaker.

(vi) Loud speaker : - It converts the electrical signal back into a sound signal.

signal strength by increasing the amp
a given signal without changing its ch

↳ An RC coupled amplifier is a part
multistage amplifier wherein different
amplifiers are connected using a comb
resistor and a capacitor.

↳ Common emitter configuration of a
transistor under proper biasing condi
works as an amplifier. It will have
gain and current gain.


↳ The input signal may be a current
voltage signal or a power signal.

↳ Amplifiers are mainly used in audio
instruments, communications, controllers etc

↳ Biasing can be obtained in many ways. Commonly used biasing is voltage divider biasing by resistors R_1 and R_2 and are given to base and collector base junctions.

#

Circuit Diagram.

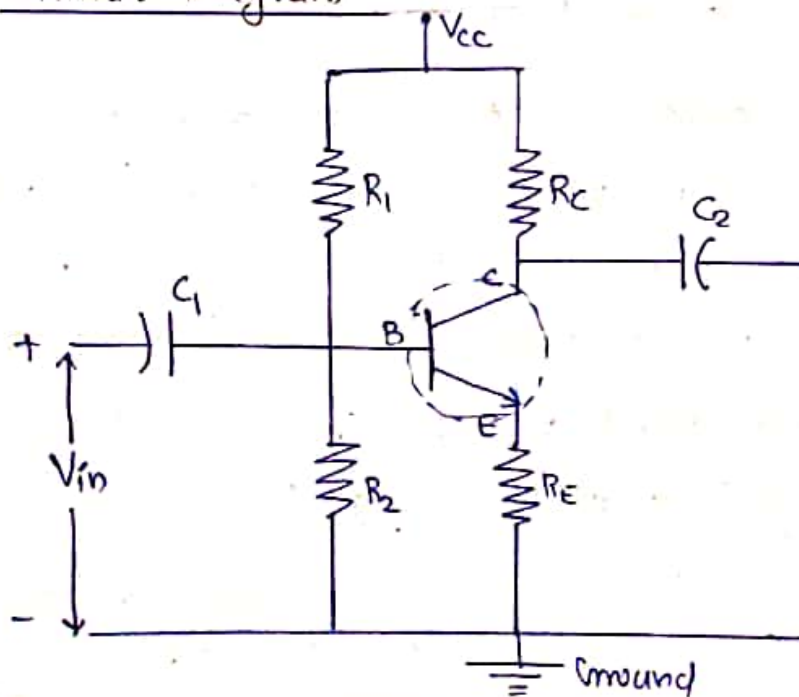

allow only AC voltage to the transistor

↳ R_1 and R_2 resistors are used for providing biasing to the bipolar transistor. R_1 and R_2 form a biasing network which provides necessary voltage to drive the transistor in active region.

↳ The region b/w cut-off and saturation is known as active region. The region of bipolar transistor operation is completely off is known as cut-off region and the region where the transistor is completely switched on is known as saturation region.


↳ Resistors R_C and R_E are used to provide voltage of V_{CC} . $R_C \rightarrow$ collector resistor
 $R_E \rightarrow$ Emitter resistor

Advantages of R-C coupled Amplifier.

- ↳ The RC coupled amplifier offers a $\text{flat frequency response}$ over a wide frequency range.
- ↳ The circuit is very compact and external components are not expensive so the cost is low.

Disadvantages

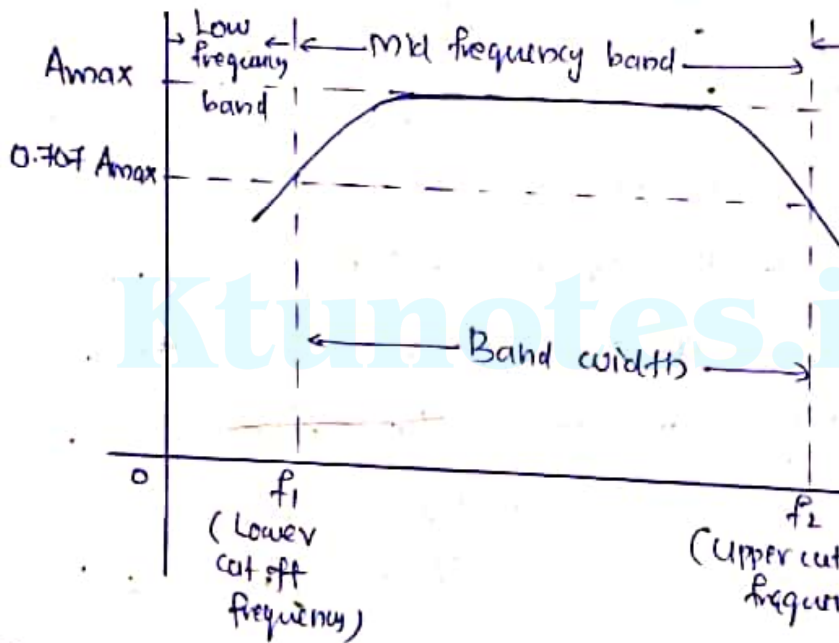- ↳ The voltage and power gain are low due to the effective load resistance.
- ↳ They become noisy with age.
- ↳ Due to poor impedance matching, the efficiency will be low.



↳ From the graph, it is understood that frequency rolls off or decreases for the frequencies below 50 Hz and for the frequencies above 20 kHz where as the voltage gain for frequencies between 50 Hz and 20 kHz is constant.

At low frequency. At low frequencies, the reactance of the input capacitor C_i and the coupling capacitor C_c are so high that a small part of the input signal is allowed to pass. $\hookrightarrow$ The reactance of the emitter bypass capacitor C_e is also very high during low frequencies. $\hookrightarrow$ Hence it cannot shunt the emitter resistor R_e effectively. With all these factors, the gain rolls off at low frequencies.

* At high frequencies (i.e. above 20 Hz)

Again considering the same point, we know that the capacitive reactance is low at high frequencies. So, a capacitor behaves as a short circuit at high frequencies. As a result of this,

reduces. Hence the voltage gain rolls off at high frequencies.


* At mid frequencies (i.e. 50 Hz to 20 kHz)

↳ The voltage gain of the capacitors is constant in this range of frequencies. As frequency increases, the reactance of the capacitors X_C decreases which tends to increase the gain.

↳ But this lower capacitive reactance has a loading effect on the next stage by which it causes a reduction in gain.

↳ Due to these two factors, the gain is constant.

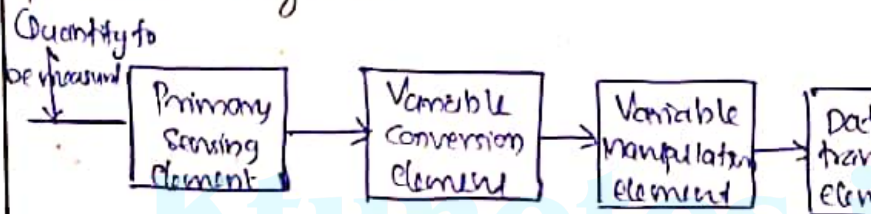manipulation element · data transmission
presentation system.



(i) Primary Sensing element

The primary sensing element is a sensor. Basically transducers are used as sensing element. Here, the physical quantity is sensed and then converted into an analog signal.

(ii) Variable conversion element

It converts the output of the primary element into a suitable form without loss of information. Basically these are secondary elements.

(iv) Data transmission element.

Some times it is not possible to give read out of the quality at a particular. In such a case, the data should transfer from one place to another place through channels known as data transmission element. Transmission paths are pneumatic pipe, cable and radio links.

(v) Data presentation or controlling element

Finally the output is recorded or given to controller to perform action. It performs functions like indicating, recording or

Feb 16/2020