



KTU NOTES

The learning companion.

**KTU STUDY MATERIALS | SYLLABUS | LIVE
NOTIFICATIONS | SOLVED QUESTION PAPERS**

🌐 Website: www.ktunotes.in

17-9-2024
Thursday

Module-II

Analyses of First and Second Orders Dynamic Circuits

Whenever, a circuit is switched from one condition to another either by a change in the applied source or a change in the circuit element, there is a transition period, during which the branch current & element voltages change from their former value to the new value. This period is called transient. After the transient has passed, the circuit is said to be in steady state.


$$V_L(t) = L \frac{di}{dt}$$
$$i_C(t) = C \frac{dV_C}{dt}$$

First order differential equation.

Complementary Function
→ Transient


Particular integral
→ Steady state

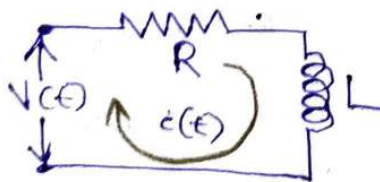Consider a combination of R & L circuit element



$$V(t) = L \frac{di(t)}{dt} + Ri(t)$$

Drawing a RLC circuit

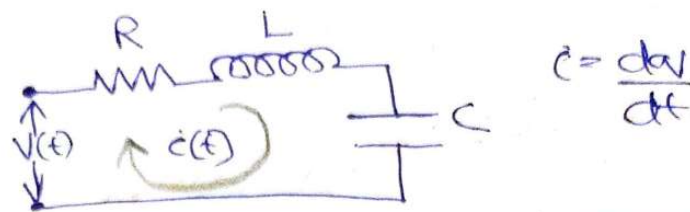

$$V(t) = Ri(t) + L \frac{di}{dt} + \frac{1}{C} \int i \cdot dt$$


$$V(t) = R \frac{dq}{dt} + L \frac{d^2q}{dt^2} + \frac{1}{C} q$$

2nd Order Differential Equation


If the circuit contains a combination of Resistor & Inductor or combination of Resistor & Capacitor, that circuit will be of 1st order. Similarly, if we take a circuit with a combination of Inductor & Capacitor, then that circuit equation will be 2nd order.

The voltage/current for an Inductor or Capacitor is differential. The circuit containing an inductor 'L' or a capacitor 'C' and resistor will have current and voltage variables given by Differential Equations. It is a linear first order differential equation with constant coefficients when the value RLC are constant. Circuit having 2 storage elements like L & C are referred to 2nd Order circuits. The circuits character are...

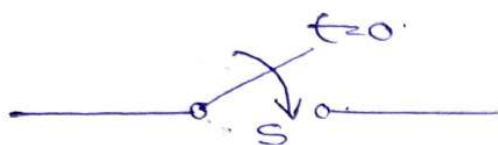at time $(t) = 0$ & is represented by a switch.



Switch is closed at $t=0$.

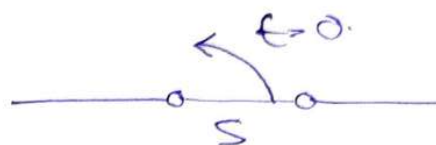

Switch is opened at $t=0$.

IMP : Switching "ON" or "OFF" of a element or source in a circuit @ $t=0$, will not disturb the storage element.

$i_L(0^-) \rightarrow$ Just before changing the circuit portion

$i_L(0^+) \rightarrow$ Just After changing the circuit portion

$$i_L(0^-) = i_L(0^+) \quad \text{Storage Elements.}$$

In the case of a capacitor, $V_C(0^-) = V_C(0^+)$

Relationship for Different Parameters

1) Resistor (R)

$$V_R(t) = R i_R(t)$$

$$i_R(t) = \frac{1}{R} V_R(t)$$

Reciprocal of Resistor is denoted by Conductance
 $= G V_R(t).$

$$G = \frac{1}{R} = \frac{dQ}{dV}$$

2) Inductors (L)

$$V_L(t) = L \frac{di_L(t)}{dt}$$

$$i_L(t) = \frac{1}{L} \int_{-\infty}^t V_L(t) \cdot dt$$

$$= \frac{1}{L} \int_0^t V_L(t) \cdot dt + i_L(0^+)$$

Taking $-\infty \rightarrow t$ as initial condition.

3) Capacitors (C)

$$V_C(t) = \frac{1}{C} \int_{-\infty}^t i_C(t) \cdot dt$$

or.

$$i_C(t) = C \frac{dV_C(t)}{dt}$$

$$V_C(t) = \frac{1}{C} \int_0^t i_C(t) \cdot dt + V_C(0^+)$$

Differential Equations

✓ Type 1: First Order Homogeneous differential Equations

$$\frac{dy(t)}{dt} + py(t) = 0 \Rightarrow \frac{dy(t)}{y(t)} = -p \cdot dt \Rightarrow y(t) = Ke^{-pt}$$

✓ Type 2: First Order Non-Homogeneous differential Equations.

$$\frac{dy(t)}{dt} + py(t) = Q$$

where 'p' is a constant & Q may be a function of independent variable or a constant.

Multiplying both sides by ' e^{pt} '

$$e^{pt} \left[\frac{dy(t)}{dt} + py(t) \right] = e^{pt} Q \Rightarrow \frac{d}{dt} [ye^{pt}] = Q \cdot e^{pt}$$

On Integrating, $ye^{pt} = \int Q \cdot e^{pt} + K$

$$y(t) \cdot e^{pt} = \int Q \cdot e^{pt} + K \Rightarrow y(t) = e^{-pt} \int Q \cdot e^{pt} + K e^{-pt}$$

The 1st term of the above Equation is known as the Particular integral which does not contain the arbitrary constant, & the 2nd term is known as Complementary function, which doesn't depend on the forcing function (input) Qe^{pt}

$$y(t) = \frac{Q}{p} + K e^{-pt}$$

This is the solution for non-homogeneous Equation.

18-9-2020
Friday

Type III (Second Order Differential Equation)





Let the differential Equation be

$$A \frac{d^2y(t)}{dt^2} + B \frac{dy(t)}{dt} + Cy(t) = 0$$

L₂
 $\frac{1}{2} \frac{d^2}{dt^2}$

The general solution is $y(t) = K_1 e^{P_1 t} + K_2 e^{P_2 t}$
 where K_1 & K_2 are constants
 P_1 and P_2 are the roots of the quadratic
 equation $AP^2 + BP + C = 0$.
 If $P_1 = P_2$, $y(t) = K_1 e^{P_1 t} + K_2 t \cdot e^{P_1 t}$.

Initial Conditions in Circuits

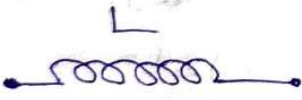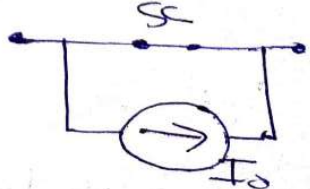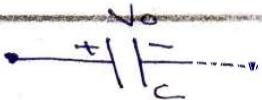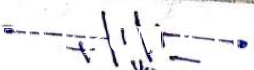Element with Initial condition $t = 0^-$	Equivalent Circuit @ $t = 0^+$	Equivalent Circuit @ $t = \infty$ [Circuit has attained Steady State value]
		
		do not allow steady change in current. 
		
		
		

Note: There is no Voltage through the inductor if the current through it is not changing with time. That is, the inductor is behaving as a short circuit to DC. Similarly, there is no current through the capacitor, if Voltage behaving as an Open circuit to DC.


Different Responses in Dynamic Circuits

1) Transient Response: The values of Voltage & Current during the transient period are known as Transient Response. It depends upon the network elements alone & independent of the forcing function. The complementary function Represents the Transient Response.

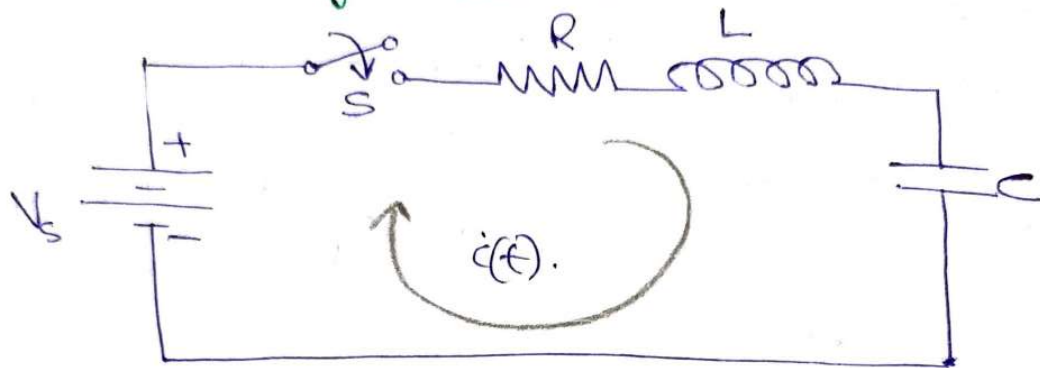2) Steady State Response: The values of Voltage & Current after the transient has died out are known as Steady State Response. It depends on both the network elements & forcing function. The particular integral represents the Steady State Response. The complete or total response is the sum of transient Response & steady state response.

$$L_2 \frac{dq_2}{dt}$$

Transient Response of Series RLC Circuit having DC Excitation



The values of the parameters are $V_s = 2V$, $R = 6\Omega$, $L = 2H$, $C = 0.25F$.

$$Ri(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int i(t) \cdot dt = V_s \rightarrow (1)$$

Differentiating, we get, $L \frac{d^2i(t)}{dt^2} + R \frac{di(t)}{dt} + \frac{1}{C} i(t) = 0$.

$$2 \frac{d^2i(t)}{dt^2} + 6 \frac{di(t)}{dt} + \frac{1}{0.25} i(t) = 0$$

$$\Rightarrow \frac{d^2i(t)}{dt^2} + 3 \frac{di(t)}{dt} + 2i(t) = 0 \rightarrow (2)$$

$$a=1, b=3, c=2$$

$$0.5p^2 + 3p + 2 = 0$$

$$p = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a} = \frac{-3 \pm \sqrt{9-8}}{2}$$

$$p = \frac{-3 \pm 1}{2} \Rightarrow p = -2, -1$$

The General Solution of the equations

$$i(t) = K_1 e^{p_1 t} + K_2 \cdot e^{p_2 t} = K_1 e^{-t} + K_2 \cdot e^{-2t}$$

$$i(t) = K_1 e^{-t} + K_2 \cdot e^{-2t}$$

The switch is closed at $t=0$.

$i(0^+) = 0$ [Current cannot change instantaneously in an inductor]

Substitute the condition in Equation (1)

In Equation (1), the 2nd & 3rd voltage term are zero at the instant of switching.

$$R_i(0^+) = 0 \therefore i(0^+) = 0$$

$$\frac{1}{C} \int_{-\infty}^0 i(t) \cdot dt = 0 \quad \left[\text{Because the initial voltage across the capacitor is zero} \right]$$

$$L \frac{di}{dt}(0^+) = V_s \text{ or } \frac{di}{dt}(0^+) = \frac{V_s}{L} = \frac{2}{2} = \underline{\underline{1 \text{ A/sec}}}$$

Evaluate the constants ' K_1 ' & ' K_2 ', we get

$$i(0^+) = 0, \quad \frac{di}{dt}(0^+) = 1$$

Now, we can evaluate the constants ' K_1 ' & ' K_2 '

$$i(t) = K_1 \cdot e^{-t} + K_2 \cdot e^{-2t}$$

$$\text{At } t = 0^+, \quad \boxed{0 = K_1 + K_2}, \quad \frac{di(t)}{dt} = -K_1 e^{-t} - 2K_2 e^{-2t}$$

$$\text{At } t = 0^+, \quad \boxed{1 = -K_1 - 2K_2}, \quad \text{Adding Equations}$$


$$K_2 - 2K_2 = 1 \Rightarrow \boxed{K_2 = -1, K_1 = 1}$$

$$\boxed{i(t) = e^{-t} - e^{-2t} \text{ A}}$$

Homework: Find the response ' V_t ' for a parallel RLC circuit.

$$I_s = 2 \text{ A}, R = \frac{1}{16} \Omega, L = \frac{1}{16} \text{ H}, C = 4 \text{ F}$$

$$L = \frac{1}{2} \frac{dq}{dt}$$

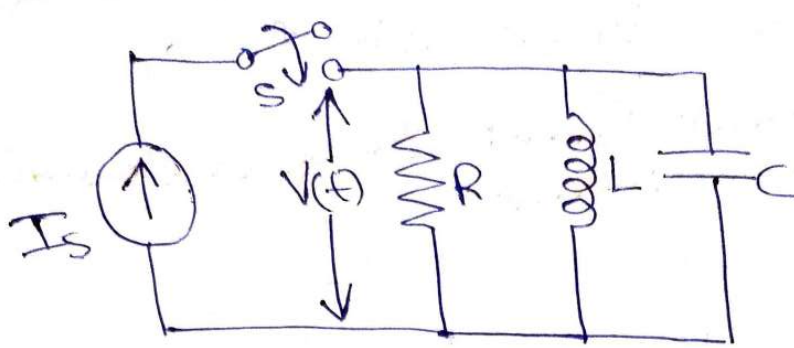


Applying KVL
Sum of voltages = 0

24-9-2020
Monday

Transient Response of Series RL circuit having DC Excitation

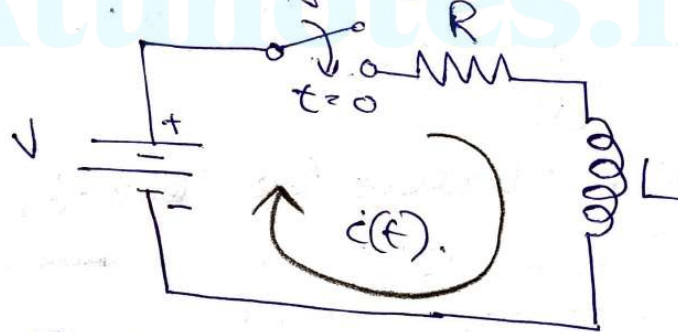Consider a Natural or Source-Free Response of RL circuit
a series RL circuit connected
across a DC voltage of 'V' Volt.



Applying KVL in circuit, we get.

$$L \frac{di(t)}{dt} + Ri(t) = V$$

Rearranging this equation,

$$\frac{di(t)}{dt} + \frac{R}{L} i(t) = \frac{V}{L}$$

Example for non-homogeneous
equation

General Solution: $i(t) = \frac{V}{R} + Ke^{-\frac{R}{L}t}$ (first order differential)

As we know, the switch is closed @ $t=0$ before that the circuit is open (disconnected). Therefore the current (current through the inductor) is zero.

Assume, $i(0^+) = 0$, Sub this in Eq (1).

$$0 = \frac{V}{R} + K \Rightarrow K = -\frac{V}{R}$$

$$i(t) = \frac{V}{R} - \frac{V}{R} e^{-R/L t} \Rightarrow i(t) = \frac{V}{R} [1 - e^{-\frac{R}{L} t}]$$

Voltage Across the Resistor, $V_R(t) = R i(t)$. Source Free response of RL circuit

$$V_R(t) = V [1 - e^{-\frac{R}{L} t}]$$

Similarly Voltage Across Inductor

$$V_L(t) = L \cdot \frac{di(t)}{dt} = L \frac{d}{dt} \left[\frac{V}{R} - \frac{V}{R} e^{-\frac{R}{L} t} \right]$$

$$V_L(t) = L \cdot \frac{V}{R} \left[0 - e^{-\frac{R}{L} t} \times -\frac{R}{L} \right]$$

$$V_L(t) = V e^{-\frac{R}{L} t}$$

Analyzing the condition of circuit @ $t=0$ & $t=\infty$

At $t=0$

$$i(0) = \frac{V}{R} [1 - 0] \Rightarrow i(0) = 0$$

$$V_R(0) = 0$$

$$V_L(0) = V$$

Similarly, at $t=\infty$

$$i(\infty) = \frac{V}{R}, V_R(\infty) = V, V_L(\infty) = 0$$

Imp Relations obtained

$$\begin{aligned} i(t) &= \frac{V}{R} [1 - e^{-\frac{R}{L} t}] \\ V_R(t) &= V [1 - e^{-\frac{R}{L} t}] \\ V_L(t) &= V e^{-\frac{R}{L} t} \end{aligned}$$

where $\tau = R/L = \tau$

$$i(t) = \frac{V}{R} [1 - e^{-t/\tau}]$$

$$i(t) = 0.632 \frac{V}{R}$$

R/L = time constant of series RLC circuit
 $\tau = R/L$


$$L = \frac{1}{2} \frac{d\phi}{di}$$

$$\tau = L/R = T, \quad i(t) = \frac{V}{R} [1 - e^{-t/\tau}] = 0.632 \frac{V}{R}$$


Time constant (τ) = L/R of the series RL circuit.

Time constant is defined as the interval after which current or voltage change 63.2% of its total change.


Plot the Response of Series RL Circuit

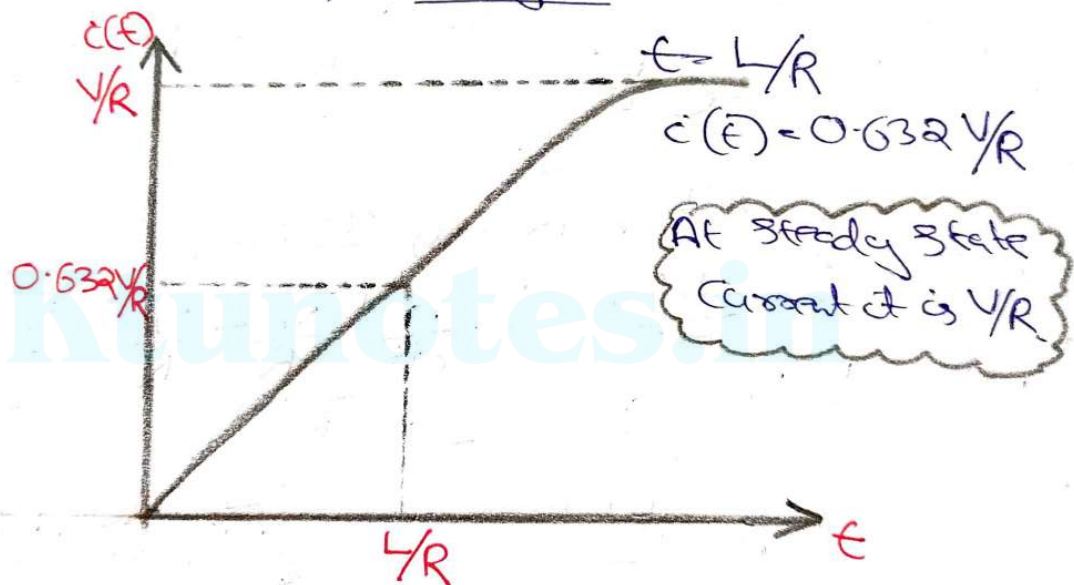

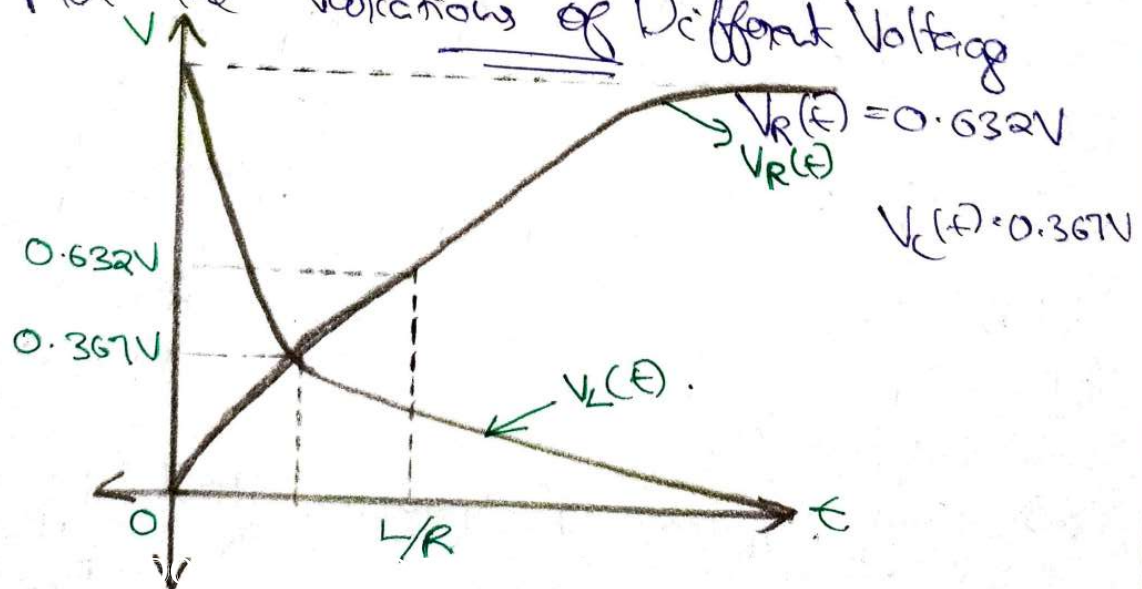Plot the Variations of Different Voltages



RL Circuit

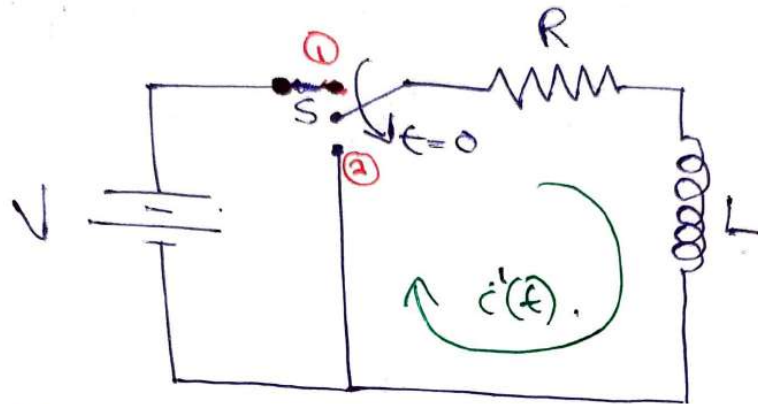


Condition: The RL Series Circuit reaches a steady state value & suddenly the voltage is withdrawn by opening the switch and throwing the switch to 2nd position.

The switch is moved to position 2 at $t = 0$.
At position ②, Applying KVL, we get,

$$L \frac{di'(t)}{dt} + Ri'(t) = 0 \Rightarrow \frac{di'(t)}{dt} + \frac{R}{L} i'(t) = 0.$$

$$\dot{C}(t) = Ke^{-R/Lt} \quad \text{--- 70}$$

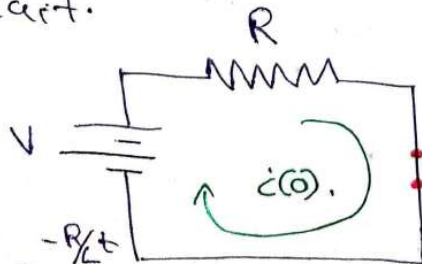At Steady State, when $t = \infty$, the inductors act as short circuit.



$$C'(t) = \frac{V}{R} e^{-R/L t}$$

$$i(O^+) = \frac{V}{R}$$


Self excited
Voltage regulation
in Regulator (1)

$$\begin{array}{r} 292 \\ \times 2 \\ \hline 584 \end{array}$$

Similarly, the voltage across the Resistor


$$V_R(t) = V e^{-\frac{R}{L}t}, \quad V_L(t) = -V e^{-\frac{R}{L}t}$$

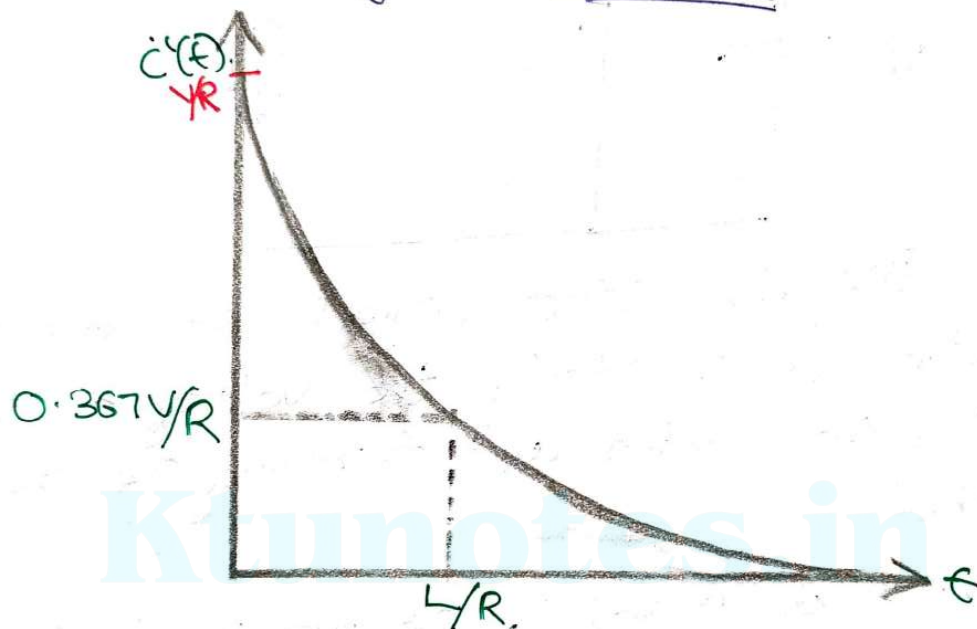Plot the Variation of $i'(t)$, $V_R(t)$ & $V_L(t)$
for this Circuit



$$t = \frac{L}{R}, \quad i'(t) = 0.367 \frac{V}{R}$$

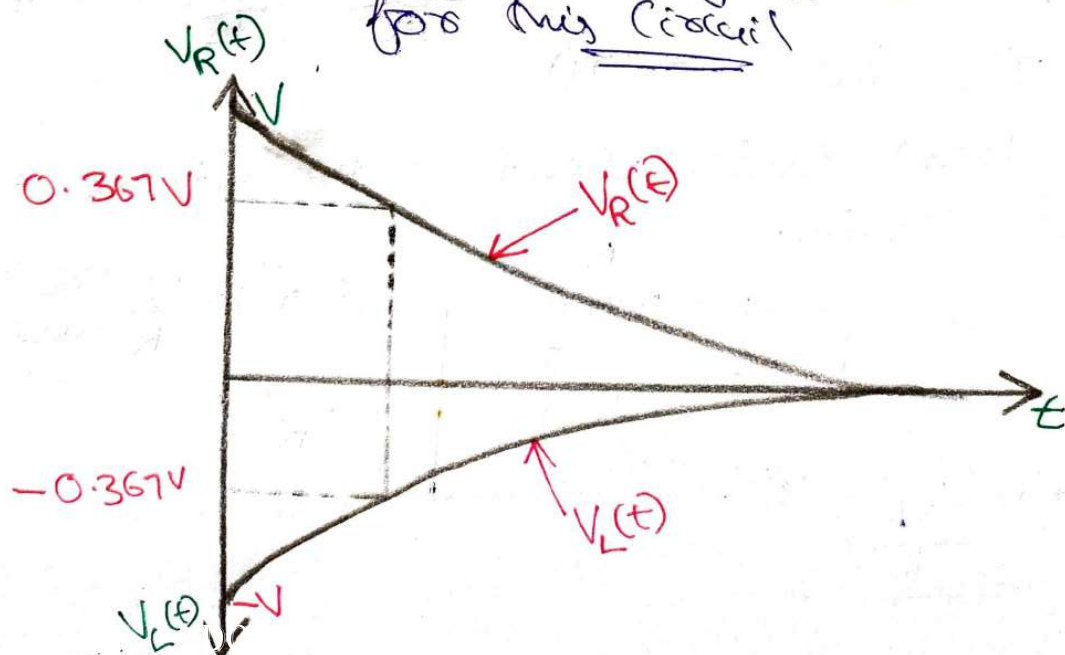
Plot the Variation of $V_R(t)$ & $V_L(t)$
for this Circuit



25-9-20
Monday

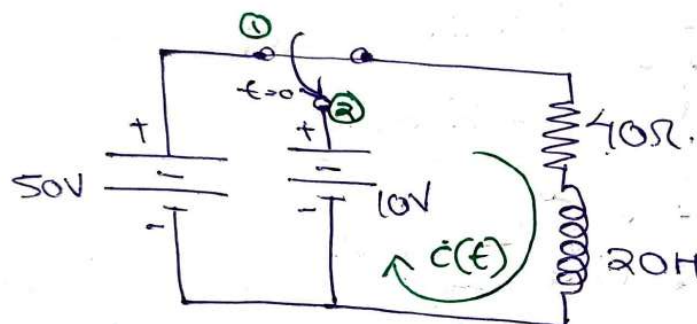
Problem: Analysis of series RL circuit excited by constant voltage or DC voltage

Q) The switch in figure is at Position one for a long time and it is moved to position 2 at $t=0$. Obtain the expression for $i(t)$ for $t > 0$.




Solution) Given, that the switch is in position 1 for a long time. The steady state that is altered.

At position 1 for a long time,

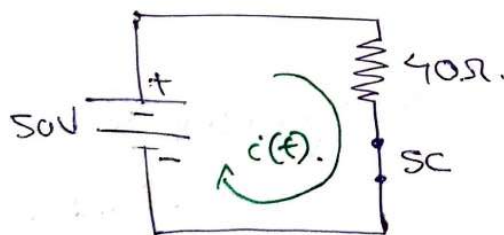

$$i(0) = \frac{50}{40} = \frac{5A}{4} = \underline{\underline{1.25A}}$$

Therefore, At position 2,

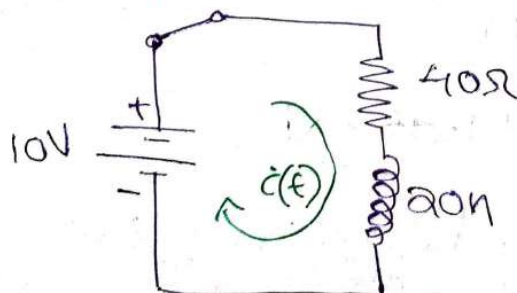

Applying KVL,

$$20 \frac{di(t)}{dt} + 40i(t) = 10 \quad L =$$

$$\frac{di(t)}{dt} + 2i(t) = 0.5 \quad \frac{1}{2} \frac{dq}{dt}$$

This is of the form 1st order non-homogeneous differential equation.


$$i(t) = \frac{0.5}{2} + Ke^{-2t}$$

Sub. the initial condition, $i(0) = \frac{0.5}{2} + K$

$$1.25 = \frac{0.5}{2} + K \Rightarrow \underline{K = 1}$$

Expression for $i(t) = \underline{0.25 + e^{-2t}}$

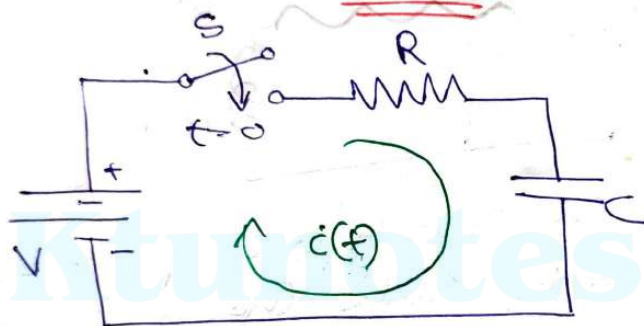Transient Response of Series RC circuit having DC Excitation



Applying KVL

$$Ri(t) + \frac{1}{C} \int_{-\infty}^t i(t) \cdot dt = V$$

$-\infty \rightarrow 0$ [initial condition]
 $0 \rightarrow t$ [transient period]

$$Ri(t) + \frac{1}{C} \int_0^t i(t) \cdot dt + \boxed{V_C(0^+)} = V$$

initial Voltage across the capacitor

Since the capacitor is initially uncharged

$$V_C(0^+) = 0.$$

$$Ri(t) + \frac{1}{C} \int_0^t i(t) \cdot dt = V$$

On Differentiating, $R \frac{di(t)}{dt} + \frac{1}{C} i(t) = 0$

The General Solution is: $i(t) = Ke^{-1/RC t}$

At $t = 0^+$, $i(0^+) = V/R$ [∵ the capacitor is short circuited]
 Apply this condition to the general solution,

$$\frac{V}{R} = Ke^0 \Rightarrow K = \frac{V}{R}$$

$$\boxed{i(t) = \frac{V}{R} e^{-\frac{t}{RC}}}$$

Expressions for $V_R(t)$ & $V_C(t)$

Voltage across the Resistor $V_R(t) = Ri(t) = Ve^{-\frac{t}{RC}}$

Voltage across the Capacitor $V_C(t) = \frac{1}{C} \int_0^t i(t) dt$

$$V_C(t) = V \left[1 - e^{-\frac{t}{RC}} \right] \rightarrow \text{Source-Free response}$$

$$V_C(t) = V - V_R(t)$$

Evaluate the circuit conditions by $\underline{t=0}$ & $\underline{t=\infty}$

At $\underline{t=0}$

$$i(t) = \frac{V}{R} \text{ and } V_R(t) = V, V_C(t) = 0$$

At $\underline{t=\infty}$: $i(t) = 0$, $V_R(t) = 0$ & $V_C(t) = V$

$$\text{At } \underline{t=RC}: i(t) = \frac{V}{R} e^{-1} = 0.367 \frac{V}{R}$$

$$V_R(t) = 0.367 V, V_C(t) = 0.632 V$$

The term "RC" is known as the time constant of RC circuit. It is denoted by τ .



Time constant [In series RC circuit]

$$\tau = RC$$

La
2 d2
ca


And time constant for series RC circuit is the time taken by the response to 36.7% of its final value steady state value.

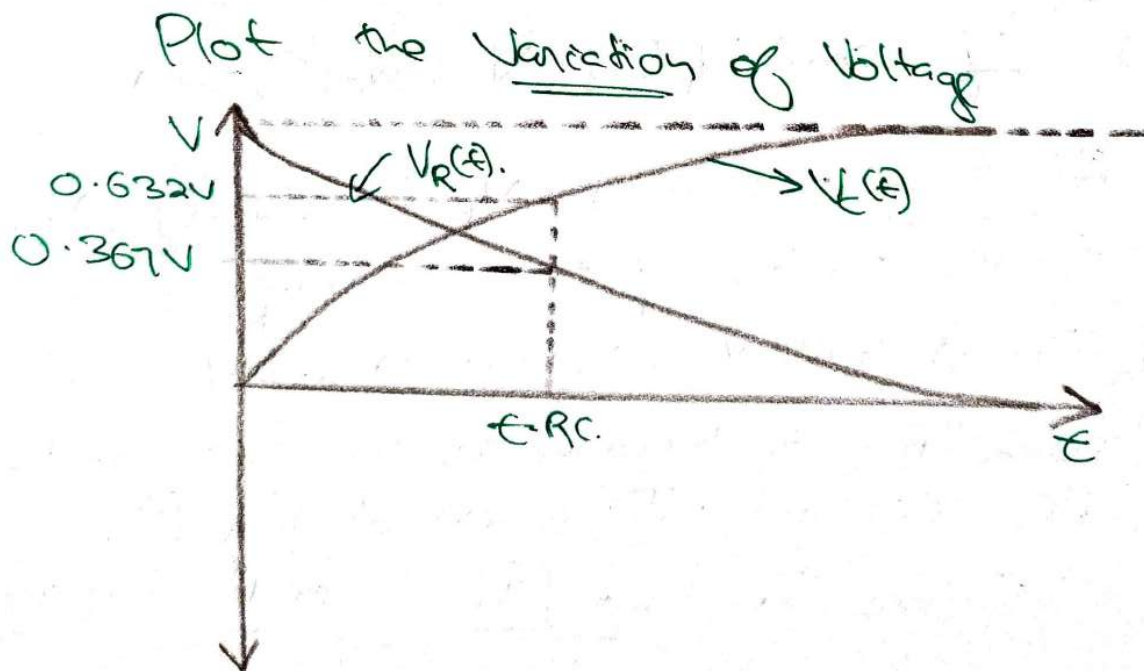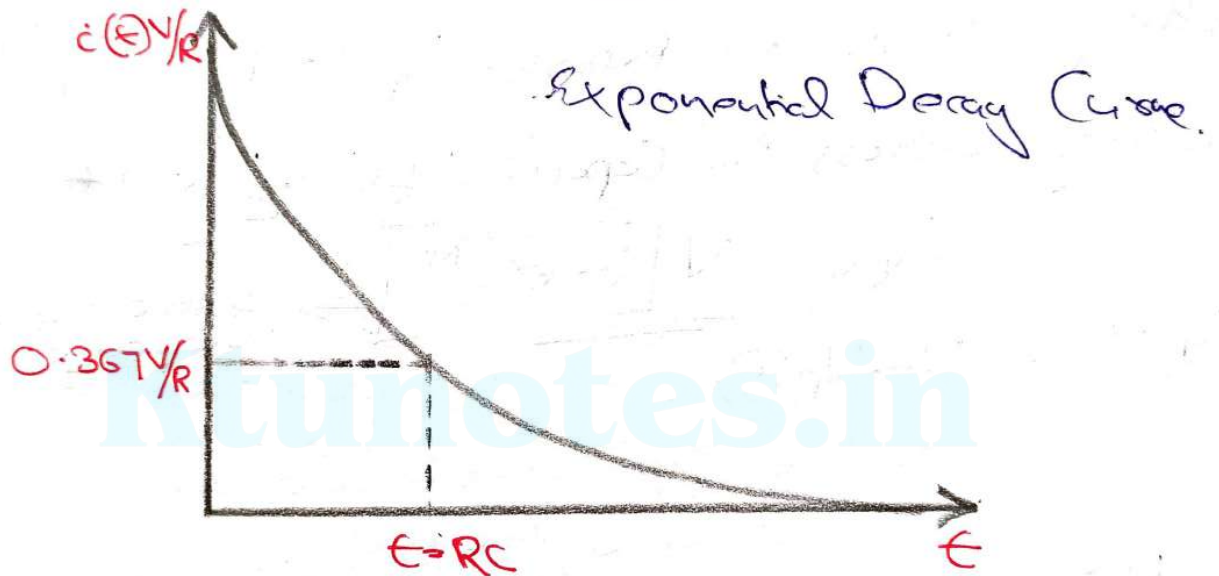Plot the variation of $i(t)$, $V_R(t)$ and $V_C(t)$



Analysis of Another Condition for a Series

RC circuit

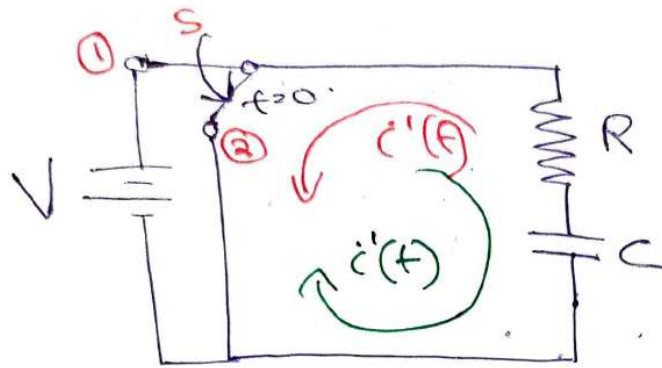

At position 2, apply KVL

$$Ri'(t) + \frac{1}{C} \int_{-\infty}^t i'(t) \cdot dt = 0$$

$$Ri'(t) + \frac{1}{C} \int_0^t i'(t) \cdot dt + V_C(0^+) = 0$$

On Differentiating, $R \frac{di'(t)}{dt} + \frac{1}{C} i'(t) = 0$

$$i'(t) = K e^{-t/RC} \text{ (for a long time)}$$

At position 1, the switch is closed & the capacitor is fully charged with a value of Voltage 'V'. Now, if we switch to position 2, then the capacitor starts discharging in the opposite direction. Now, the current supplied to the circuit, is the voltage & the capacitor in the opposite direction instead of the actual direction.

However, $t = 0^+$, the capacitor keeps the steady state voltage $V_C(0^+) = V$ & the direction of $i'(t)$ during discharging is negative. Phase, $\frac{1}{2}\pi$ or $\frac{3}{2}\pi$.

$i'(0^+) = -\frac{V}{R}$. Sub this initial condition,

$$\rightarrow -\frac{V}{R} = Ke^{-\frac{t}{RC}} \rightarrow \boxed{K = -\frac{V}{R}}$$

Therefore, General solution becomes,

$$\boxed{i'(t) = -\frac{V}{R} e^{-t/RC}}$$


Plot the Variation of $i(t)$

Similarly,

$$V_R'(t) = -Ve^{-t/RC}$$

$$V_C'(t) = Ve^{-t/RC}$$

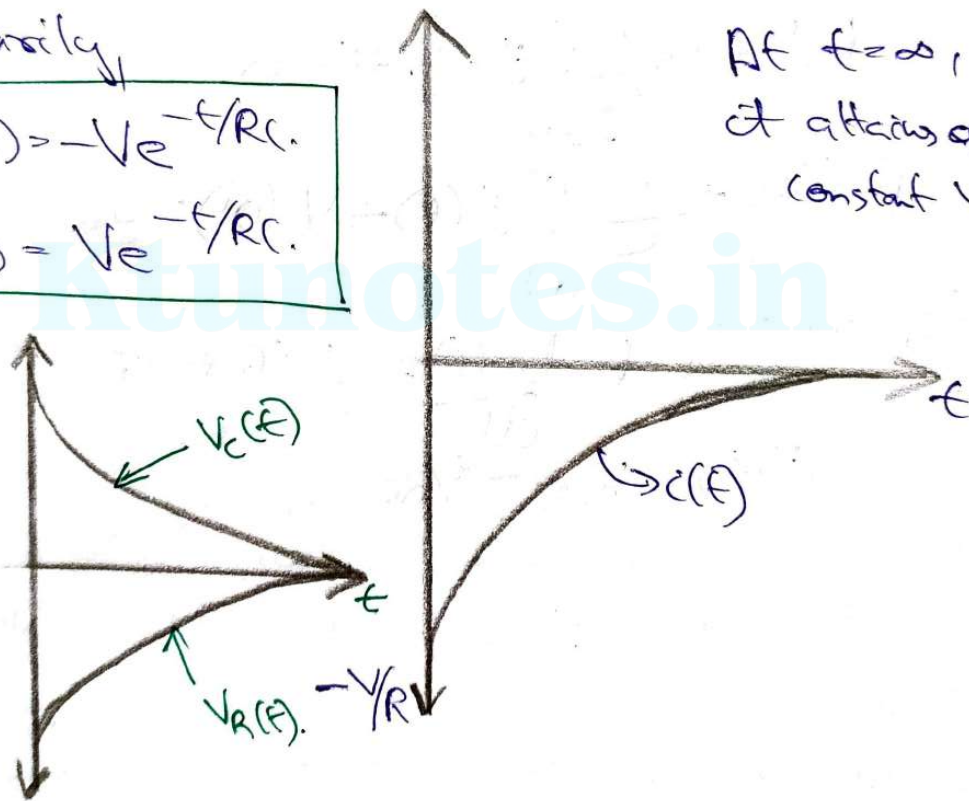At $t = \infty$,
it attains a
constant value



Time Domain Signals $\Rightarrow$ Frequency Domain Signals

LAPLACE TRANSFORM

$$\underline{\underline{S(t) \rightarrow F(s)}}$$

30-9-20
Wednesday

Review of Laplace Transforms

It is one of the mathematical tool for the solution of Linear Ordinary integro-differential equation. The Laplace Transforms converts the integro-differential equation into an algebraic equation in 's' [Laplace's Operator]

Definition of Laplace's Transform: For the time function, $f(t)$ which is zero for $t < 0$ and that satisfy the condition $\int_0^{\infty} |f(t) \cdot e^{-\sigma t}| \cdot dt < \infty$ for some real and positive sigma. The Laplace Transform of $f(t)$ is defined as $F(s) = L[f(t)] = \int_0^{\infty} f(t) \cdot e^{-st} \cdot dt$ where the variable 's' which is the Laplace's Operator is a complex variable, $s = \sigma + j\omega$

Properties of Laplace's Transform

1) Multiplication by a constant.

$$L[kf(t)] = kF(s)$$

2) Sum and Differences

$$L[f_1(t) \pm f_2(t)] = F_1(s) \pm F_2(s)$$

3) Differentiation w.r.t. t,

$$L\left[\frac{d}{dt} f(t)\right] = sF(s) - f(0) \quad \text{where } f(0) = \lim_{t \rightarrow 0} f(t).$$

4) Integration by 't'

$$\mathcal{L}\left[\int_0^t s(\tau) \cdot d\tau\right] = \frac{F(s)}{s}$$

5) Initial Value theorem


$$s(0) = \lim_{t \rightarrow 0} s(t) = \lim_{s \rightarrow \infty} sF(s)$$

6) Final Value theorem

$$s(\infty) = \lim_{t \rightarrow \infty} s(t) = \lim_{s \rightarrow 0} [sF(s)]$$

Laplace Transform Pairs

Sl. No.	$s(t)$	$F(s) = \int_0^{\infty} s(t) \cdot e^{-st} \cdot dt$
1. ✓	1 or Unit Step function $u(t)$ k (constant)	$1/s$; k/s
2. ✓	t, t^n	$1/s^2$; $\frac{n!}{s^{n+1}}$
3. ✓	$\delta(t)$ [impulse function] (very short duration with infinite magnitude)	Unity (1)
4. ✓	$e^{\pm at}$	$\frac{1}{s \mp a}$

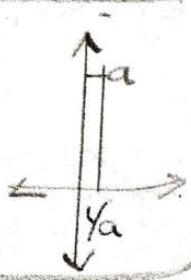

5. ✓	$t \cdot e^{\pm at}$	$\frac{1}{(s \mp a)^2}$
6. ✓	$\sin \omega t$	$\frac{\omega}{s^2 + \omega^2}$
7. ✓	$\cos \omega t$	$\frac{s}{s^2 + \omega^2}$
8. ✓	$e^{-at} \sin \omega t$	$\frac{\omega}{(s+a)^2 + \omega^2}$
9. ✓	$e^{-at} \cos \omega t$	$\frac{(s+a)}{(s+a)^2 + \omega^2}$
10. ✓	$\sin(hat)$	$\frac{a}{s^2 - a^2}$
11. ✓	$\cos(hat)$	$\frac{s}{s^2 - a^2}$

* Partial Fraction Expansion Methods (1st method)

1) Partial Fraction Expansion when all the roots are simple

Example: $F(s) = \frac{P(s)}{(s+s_1)(s+s_2)\dots(s+s_n)}$ where the roots $s_1, s_2, \dots, s_n$ are simple

$$F(s) = \frac{K_1}{s+s_1} + \frac{K_2}{s+s_2} + \dots + \frac{K_n}{s+s_n}$$

where $K_1, K_2, \dots, K_n$ are residues.

$$K_1 = (s+s_1)F(s) / s = -s_1$$

$$\text{General } K_n = (s+s_n)F(s) / s = -s_n$$

Problem Q) Solve the differential equation $x'' + 3x' + 2x = 0$ and $x(0) = 2$ & $x'(0) = -3$

Solution) $L\left[\frac{d^2 x(t)}{dt^2}\right] = s^2 X(s) - sx'(0) - x'(0)$

Taking Laplace's Transform,

$$s^2 X(s) - sx'(0) - x'(0) + 3[sX(s) - x(0)] + 2X(s) = 0$$

$$\Rightarrow s^2 X(s) - 2s + 3 + 3sX(s) - 3 \times 2 + 2X(s) = 0$$

$$\Rightarrow s^2 X(s) + 3sX(s) + 2X(s) = 2s + 3$$

$$\Rightarrow (s^2 + 3s + 2)X(s) = 2s + 3$$

$$X(s) = \frac{2s+3}{s^2+3s+2} = \frac{2s+3}{(s+1)(s+2)}$$

$$X(s) = \frac{2s+3}{(s+1)(s+2)} = \frac{A}{(s+1)} + \frac{B}{(s+2)}$$

$$A = (s+1)X(s) \Big|_{s=-1} = \frac{(s+1)(2s+3)}{(s+1)(s+2)} \Big|_{s=-1}$$

$$A = \frac{(2s+3)}{(s+2)} \Big|_{s=-1} \Rightarrow A = \frac{-2+3}{-1+2} \Rightarrow \boxed{A=1}$$

$$B = \frac{(2s+3)}{(s+1)} \Big|_{s=-2} \Rightarrow B = \frac{2(-2)+3}{-2+1} = \frac{-1}{-1} = 1 \Rightarrow \boxed{B=1}$$

$$X(s) = \frac{1}{(s+1)} + \frac{1}{(s+2)} \quad \text{taking inverse Laplace transform}$$

$$x(t) = e^{-t} + e^{-2t}$$

* Partial Fraction Expansion when some of the roots are of multiple order (2nd method)

$$F(s) = \frac{P(s)}{(s+s_1)^r (s+s_2)} = \frac{K_{11}}{(s+s_1)} + \frac{K_{12}}{(s+s_1)^2} + \dots + \frac{K_{1r}}{(s+s_1)^r} + \frac{K_2}{s+s_2}$$

where $K_{1r} = (s+s_1)^r \cdot F(s) \Big|_{s=-s_1}$

$$K_{1(r-1)} = \frac{d}{ds} \left[(s+s_1)^r F(s) \right] \Big|_{s=-s_1}$$

Similarly $K_{1(r-2)} = \frac{1}{2!} \frac{d^2}{ds^2} \left[(s+s_1)^r F(s) \right] \Big|_{s=-s_1}$

$$K_{11} = \frac{1}{(r-1)!} \frac{d^{r-1}}{ds^{r-1}} \left[(s+s_1)^r F(s) \right] \Big|_{s=-s_1} \quad \leftarrow \text{Important Result.}$$

Problem 9) Find $I(t)$ if $I(s) = \frac{1}{s(s+1)^2(s+2)}$

$$I(s) = \frac{1}{s(s+1)^2(s+2)} = \frac{A}{s} + \frac{B}{(s+1)} + \frac{C_{11}}{(s+1)^2} + \frac{C_{12}}{(s+1)} + \frac{C_2}{(s+2)}$$

$$A = \frac{1}{(s+1)^2(s+2)} \Big|_{s=0} \Rightarrow A = \underline{\underline{\frac{1}{2}}}$$

$$B = \frac{1}{s(s+1)^2} \Big|_{s=-2} = B = \frac{1}{-2(-2+1)^2} = \underline{\underline{-\frac{1}{2}}}$$

$$C_{11} = \frac{1}{s(s+2)} \Big|_{s=-1} = C_{11} = \underline{\underline{-1}}$$

$$C_{12} = \frac{d}{ds} \left[(s+1)^2 I(s) \right] \Big|_{s=-1} = \frac{d}{ds} \left[\frac{1}{s(s+2)} \right] \Big|_{s=-1} = \underline{\underline{0}}$$

Important

$$I(s) = \frac{\frac{1}{2}}{s} - \frac{\frac{1}{2}}{s+2} - \frac{1}{(s+1)^2}$$

Taking Laplace's Inverse,

$$i(t) = \underline{\underline{\frac{1}{2} - \frac{1}{2}e^{-2t} - te^{-t}}}$$

* Partial Fraction Expansion When 2 roots are of complex conjugate Pairs (3rd Method)

$$\text{if } F(s) = \frac{P(s)}{(s+\alpha+j\omega)(s+\alpha-j\omega)}$$

$$F(s) = \frac{K_1}{(s+\alpha+j\omega)} + \frac{K_2}{(s+\alpha-j\omega)} \quad , \quad K_1 = \left. (s+\alpha+j\omega) \cdot F(s) \right|_{s=-\alpha-j\omega}$$

$$K_2 = K_1^* \text{ (conjugate)}$$

Problem Q) Find ~~$i(t)$~~ if $I(s) = \frac{s^2 + 5s + 9}{s^3 + 5s^2 + 12s + 8}$

$$I(s) = \frac{s^2 + 5s + 9}{(s+1)(s^2 + 4s + 8)}$$

Put, $s = -1$ $\Rightarrow -1 + 5 - 12 + 8 = 0$

$$= \frac{s^2 + 5s + 9}{(s+1)(s+2+j2)(s+2-j2)}$$

$$\Rightarrow \frac{A}{s+1} + \frac{B}{s+2+j2} + \frac{B^*}{s+2-j2} \quad s+1 \left| \frac{s^2+4s+8}{s^3+s^2+12s+8} \right.$$

$$\Rightarrow \frac{1}{(s+1)} - \frac{1/j4}{(s+2+j2)} + \frac{1/j4}{(s+2-j2)}$$

$$\begin{array}{r} 4s^2+12s \\ 4s^2+4s \\ \hline 8s+8 \\ 8s+8 \\ \hline 0 \end{array}$$

$$I(s) = \frac{1}{s+1} - \frac{1}{j4(s+2+j2)} + \frac{1}{j4(s+2-j2)} \quad B = \frac{1}{j-1} \quad \begin{array}{r} 8s+8 \\ 8s+8 \\ \hline 0 \end{array}$$

Taking Laplace's ~~Form~~ ^{Inverse}

$$i(t) = e^{-t} - \frac{1}{j4} e^{-(2+j2)t} + \frac{1}{j4} e^{-(2-j2)t}$$

$$= e^{-t} - \frac{1}{j4} [e^{-2t} \cdot e^{-j2t} - e^{-2t} \cdot e^{j2t}]$$

$$B = \frac{1}{j-1}$$

$$B = \frac{-1}{-j4}$$

$$B^* = \frac{1}{j4}$$

$$\Rightarrow e^{-t} - \frac{1}{j4} e^{-2t} [e^{-j2t} - e^{j2t}]$$

$$\Rightarrow e^{-t} + \frac{1}{2} e^{-2t} \left[\frac{e^{j2t} - e^{-j2t}}{j2} \right]$$

$$i(t) = e^{-t} + \frac{1}{2} e^{-2t} \cdot \sin(2t) \cdot A$$

$$\sin(s) = \frac{e^{js} - e^{-js}}{2j}$$

$$\cos(s) = \frac{e^{js} + e^{-js}}{2}$$

Another method

$$I(s) = \frac{s^2+5s+9}{(s+1)(s^2+4s+8)} = \frac{1}{(s+1)} + \frac{1}{s^2+4s+8}$$

$$\frac{A}{s} + \frac{Bs+C}{s^2+4s+8} = s^2+5s+9 = A(s^2+4s+8) + (Bs+C)s$$

$$I(s) = \frac{1}{s+1} + \frac{1}{s^2+4s+8} = \frac{1}{s+1} + \frac{1}{(s+2)^2+2^2}$$

$$I(s) = \frac{1}{s+1} + \frac{1}{2} \cdot \frac{2}{(s+2)^2+2^2}$$



$$i(t) = e^{-t} + \frac{1}{2} e^{-2t} \cdot \sin(2t) \cdot A$$

La
1/2
sin


1-10-2020
Tuesday

Transformed Circuit Component Representation

✓ Independent Sources

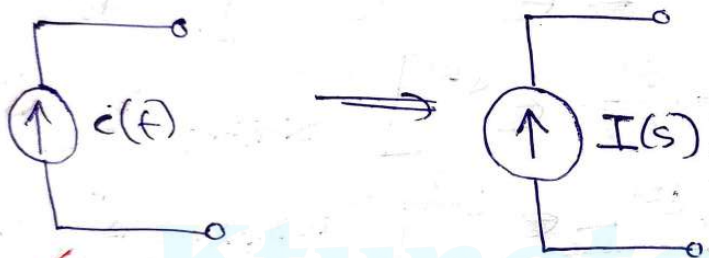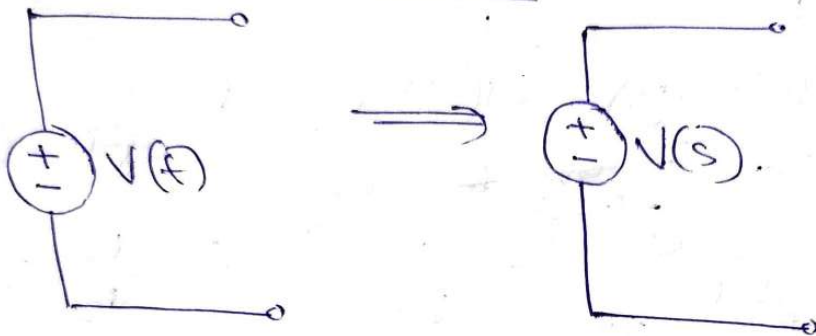


✓ Resistance Parameter

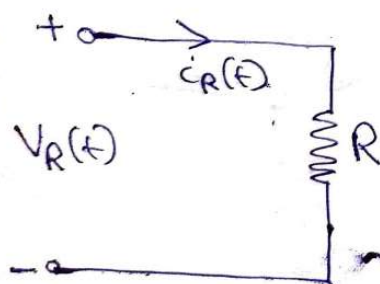


$$V_R(t) = R i_R(t)$$

changing to into Laplace's Transform

$$V_R(s) = R \cdot I_R(s)$$

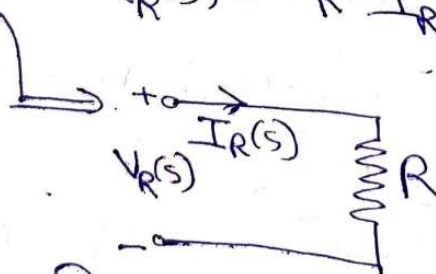


✓ Inductances Parameter

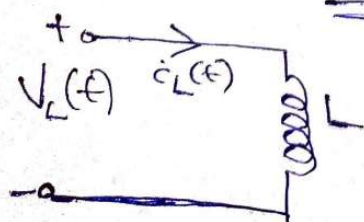

$$V_L(t) = L \frac{di_L(t)}{dt}$$


$$i_L(t) = \frac{1}{L} \int_0^t V_L(\tau) \cdot d\tau + i_L(0^+)$$

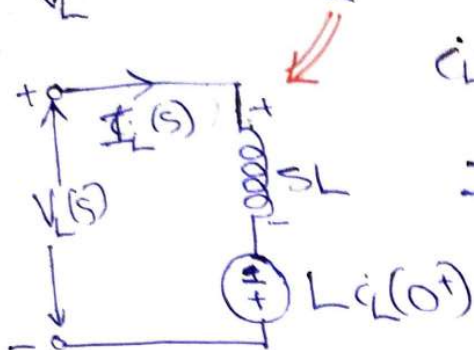Laplace's Transform $\Rightarrow V_L(s) = L[sI_L(s) - i_L(0^+)]$
 $V_L(s) = LSI_L(s) - Li_L(0^+)$




$$i_L(t) = \frac{1}{L} \int_0^t V_L(t) \cdot dt + i_L(0^+)$$
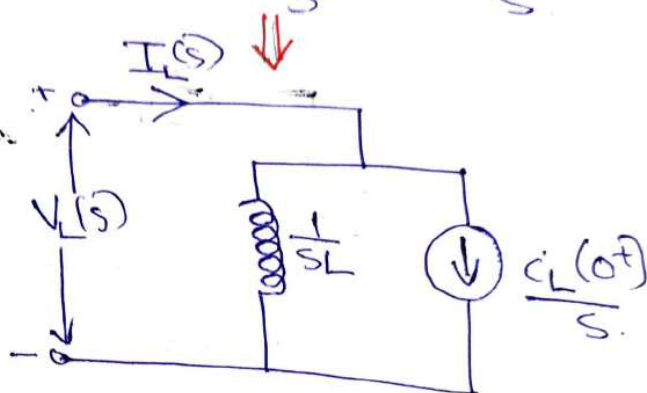
$$I_L(s) = \frac{1}{L} \cdot \frac{V_L(s)}{s} + \frac{i_L(0^+)}{s}$$



✓ Capacitance Parameters


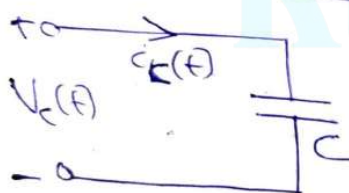


$$V_C(t) = \frac{1}{C} \int_0^t i_C(t) \cdot dt + V_C(0^+)$$

$$i_C(t) = C \frac{dV_C(t)}{dt}$$


Laplace transform $\Rightarrow V_C(s) = \frac{1}{Cs} I_C(s) + \frac{V_C(0^+)}{s}$
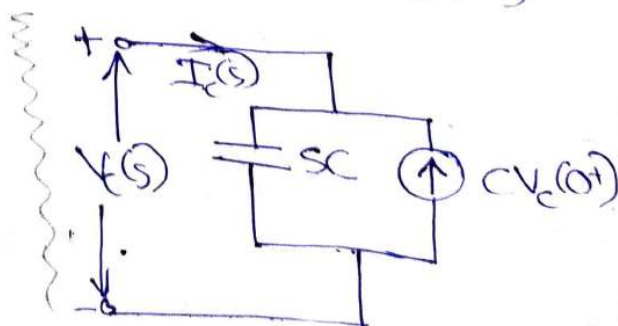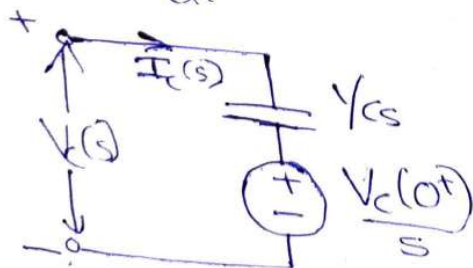
$$i_C(t) = C \frac{dV_C(t)}{dt} \Rightarrow I_C(s) = CS V_C(s) - CV_C(0^+)$$




$$I_C = \frac{1}{s} \frac{dQ}{dt}$$

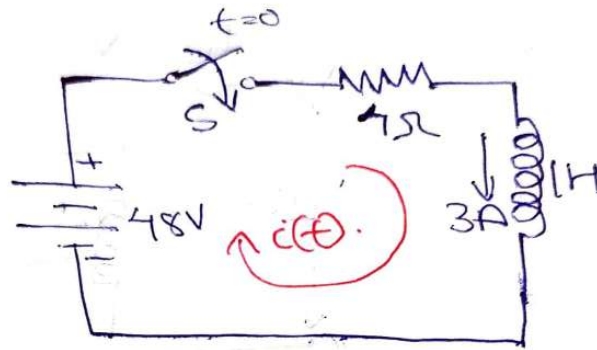Q) Consider the RL circuit with $R=4\Omega$ & $L=1H$ excited by 48V DC Source as shown in Fig. Assume the initial current through inductor as 3A. Using the Laplace's transform, Determine the current $i(t)$. Also Draw the transform circuit.



Solution)

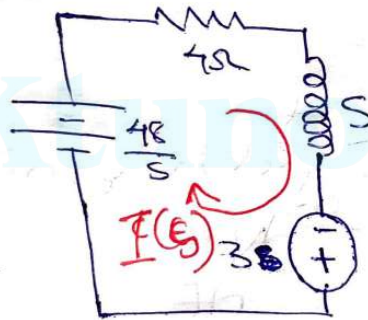

$$4I(s) + sI(s) - 3 = \frac{48}{s}$$

$$I(s)[s+4] = \frac{48+3s}{s}$$

$$I(s) = \frac{3s+48}{s(s+4)}$$

$$I(s) = \frac{A}{s} + \frac{B}{s+4}$$


$$A = \frac{3s+48}{s+4} \Big|_{s=0} = A=12$$

$$B = \frac{3s+48}{s} \Big|_{s=-4} = B=-9$$

$$I(s) = \frac{12}{s} - \frac{9}{s+4} \quad \text{Taking } L^{-1}, i(t) = 12 - 9e^{-4t} \text{ A}$$

Consider a series RLC circuit with the capacitor initially charged to a voltage of 1V as shown in Fig. Find the expression for $i(t)$. Also

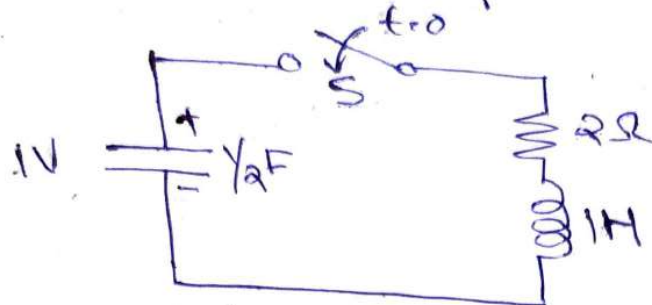draw the s-domain representation of circuit.



Solution) $L \frac{di(t)}{dt} + Ri(t) + \frac{1}{C} \int i(t) dt + V_C(0^+) = 0$

$LSI(s) - L i(0^+) + RI(s) + \frac{1}{Cs} I(s) + \frac{V_C(0^+)}{s} = 0$

$SI(s) + 2I(s) + \frac{I(s)}{s} + \frac{1}{s} = 0$

$I(s) \left\{ s + 2 + \frac{1}{s} \right\} = -\frac{1}{s}$


$I(s) \left\{ \frac{s^2 + 2s + 1}{s} \right\} = -\frac{1}{s}$

$I(s) = -\frac{1}{s} \times \frac{s}{s^2 + 2s + 1} \Rightarrow I(s) = -\frac{1}{(s+1)^2}$

~~$i(t) = -t \cdot e^{-t}$~~

By Inverse Laplace transform

So, $i(t) = -t \cdot e^{-t} \text{ A}$

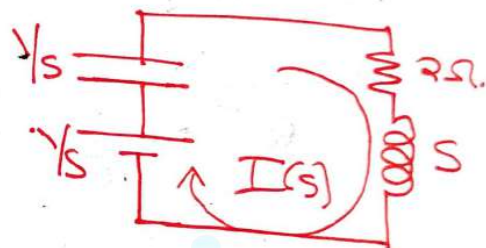

Ca
1/2 d2
ca

2-10-2020 Friday
 Response of Series RC circuit with DC excitation

$$Ri(t) + \frac{1}{C} \int i(t) \cdot dt = V$$

Taking Laplace's Transform


$$RI(s) + \frac{1}{Cs} I(s) = \frac{V}{s}$$

$$I(s) \left[R + \frac{1}{Cs} \right] = V/s \Rightarrow I(s) \left[\frac{RCs + 1}{Cs} \right] = V/s$$


$$I(s) = \frac{CV}{RC \left[s + \frac{1}{RC} \right]} = \frac{V/R}{s + \frac{1}{RC}}$$

Taking Laplace's Inverse,

$$i(t) = \frac{V}{R} e^{-t/RC}$$

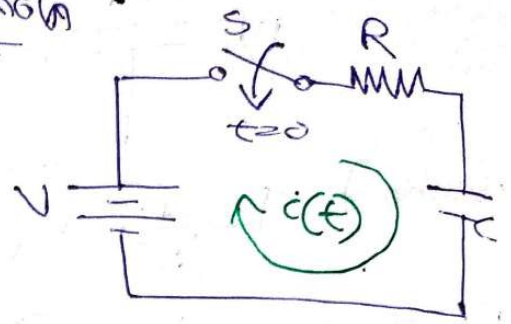

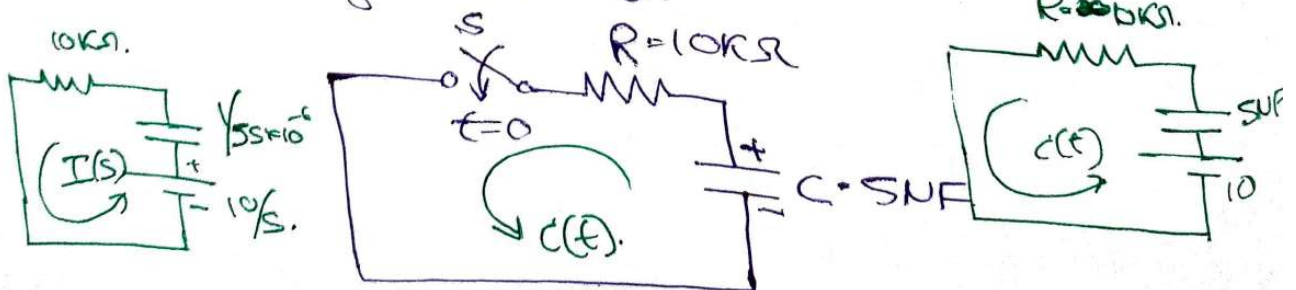Q. A capacitor of SNF been charged initially to 10 Volt & connected to a resistance of 10kΩ and is allowed to discharge through it by switching "OFF" a switch 'S'. Find the Expression for discharged current.



$$Ri(t) + \frac{1}{C} \int_{-\infty}^t i(t) \cdot dt = 0 \Rightarrow Ri(t) + \frac{1}{C} \int_{-\infty}^0 i(t) \cdot dt +$$

$$\int_0^t i(t) \cdot dt \Big] = 0 \Rightarrow Ri(t) + 10V + \frac{1}{C} \int_0^t i(t) \cdot dt = 0.$$

Substituting the values, Taking Laplace's transform

$$RI(s) + \frac{10}{s} + \frac{1}{Cs} I(s) = 0.$$

$$I(s) \left[R + \frac{1}{Cs} \right] = -\frac{10}{s} \Rightarrow I(s) [R(s+1)] = -10C$$

$$I(s) \left[s + \frac{1}{RC} \right] = -\frac{10}{R} \Rightarrow I(s) = \frac{-\frac{10}{R}}{s + \frac{1}{RC}}$$

Taking Laplace's Inverse of the equation, we get

$$i(t) = -\frac{10}{R} e^{-t/RC} \Rightarrow i(t) = \frac{-10}{10 \times 10^3} e^{-t/10 \times 10^3 \times 5 \times 10^{-6}}$$

$$i(t) = -10^{-3} \cdot e^{-\frac{t}{50 \times 10^{-3}}} \Rightarrow i(t) = -10^{-3} \cdot e^{-20t} \text{ A}$$

Response of Series RLC circuit with

Assumption: ^{initially} DC excitation
 Present: Non-stored energy is not

$$Ri(t) + L \frac{di}{dt} + \frac{1}{C} \int i(t) \cdot dt = V$$


Taking Laplace's Transform

$$RI(s) + Ls(I(s)) + \frac{1}{C} I(s) = V/s$$

$$\left[R + Ls + \frac{1}{Cs} \right] I(s) = \frac{V}{s} \Rightarrow [LCS^2 + RCs + 1] I(s) = CV$$

$$\left[s^2 + \frac{R}{L}s + \frac{1}{LC} \right] I(s) = \frac{V}{L}$$
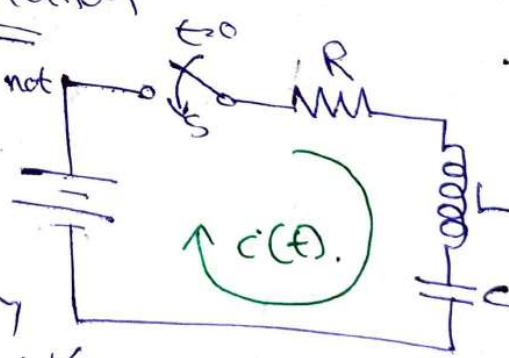
$$I(s) = \frac{V/L}{s^2 + \frac{R}{L}s + \frac{1}{LC}} \quad \text{where } s_1, s_2 = \frac{-R/L \pm \sqrt{(R/L)^2 - 4/LC}}{2}$$



$$s_1, s_2 = \frac{-R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$s_1 = \frac{-R}{2L} + \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}}, s_2 = \frac{-R}{2L} - \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}}$$

For simplification, we can make some assumptions, let $\omega_n = \frac{1}{\sqrt{LC}}$ (SM sem (extended 3/4))

$\omega_n \rightarrow$ natural frequency of oscillation (rad/s)

$\zeta \omega_n = \frac{R}{2L}$, where $\zeta \rightarrow$ damping ratio

$$s_1 = -\zeta \omega_n + \sqrt{(\zeta \omega_n)^2 - \omega_n^2} = -\zeta \omega_n \pm \omega_n \sqrt{\zeta^2 - 1}$$

$$s_2 = -\zeta \omega_n - \sqrt{(\zeta \omega_n)^2 - \omega_n^2} = -\zeta \omega_n \pm \omega_n \sqrt{\zeta^2 - 1}$$

$$I(s) = \frac{V/L}{s^2 + \frac{R}{L}s + \frac{1}{LC}} = \frac{V/L}{(s-s_1)(s-s_2)}$$

Apply partial fraction,

$$I(s) = \frac{A}{s-s_1} + \frac{B}{s-s_2} \text{ where } A = \frac{V/L}{s_1-s_2} + \frac{V/L}{s_2-s_1}$$

$$A = \frac{V/L}{2\omega_n \sqrt{\zeta^2 - 1}}, B = \frac{-V/L}{2\omega_n \sqrt{\zeta^2 - 1}}$$

$$I(s) = \frac{V/L}{2\omega_n \sqrt{\zeta^2 - 1}} \left[\frac{1}{s-s_1} - \frac{1}{s-s_2} \right]$$

Taking Inverse Laplace Trans form

$$i(t) = \frac{V/L}{2\omega_n \sqrt{\zeta^2 - 1}} \left[e^{s_1 t} - e^{s_2 t} \right]$$

$$i(t) = \frac{V/L}{2\omega\sqrt{\delta^2-1}} \left[e^{[-\delta\omega t + \omega\sqrt{\delta^2-1}]t} - e^{[-\delta\omega t - \omega\sqrt{\delta^2-1}]t} \right]$$

$$i(t) = \frac{V/L}{2\omega\sqrt{\delta^2-1}} \cdot e^{-\delta\omega t} \left[e^{(\omega\sqrt{\delta^2-1})t} - e^{-(\omega\sqrt{\delta^2-1})t} \right]$$

There are 3 cases for δ

1) $\delta > 1$, 2) $\delta = 1$, 3) $\delta < 1$

Case 1: $\delta > 1$

$$\sin(\omega t) = \frac{e^{j\omega t} - e^{-j\omega t}}{2j}$$

undamped
 $\delta = 0$

$$\left(\frac{R}{2L}\right)^2 > \frac{1}{LC}, \quad Q = \omega_0 L/R$$

$$i(t) = \frac{V}{\omega L \sqrt{\delta^2-1}} e^{-\delta\omega t} \sinh(\omega\sqrt{\delta^2-1}t)$$

This condition is said to be Over Damped

2) $\delta = 1$: Case 2 [critically damped]

$$\left(\frac{R}{2L}\right)^2 = \frac{1}{LC}, \quad s_1 = -\omega_0, \quad s_2 = -\omega_0$$


$$I(s) = \frac{V/L}{(s + \omega_0)^2}, \quad i(t) = \frac{V}{L} t e^{-\omega_0 t}$$

3) Case 3: $\delta < 1$ [Under Damped]


$$\left(\frac{R}{2L}\right)^2 < \frac{1}{LC}, \quad i(t) = \frac{V}{\omega L \sqrt{1-\delta^2}} \left[\frac{e^{-\delta\omega t} \left[\frac{\cos(\omega\sqrt{1-\delta^2}t)}{\omega\sqrt{1-\delta^2}} - \frac{1}{\omega} \right]}{2j} \right]$$

$$i(t) = \frac{V}{\omega_n \sqrt{1-\zeta^2}} e^{-\zeta \omega_n t} \left[\frac{j \omega_n \sqrt{1-\zeta^2}}{2j} e^{j \omega_n \sqrt{1-\zeta^2} t} - \frac{j \omega_n \sqrt{1-\zeta^2}}{2j} e^{-j \omega_n \sqrt{1-\zeta^2} t} \right]$$
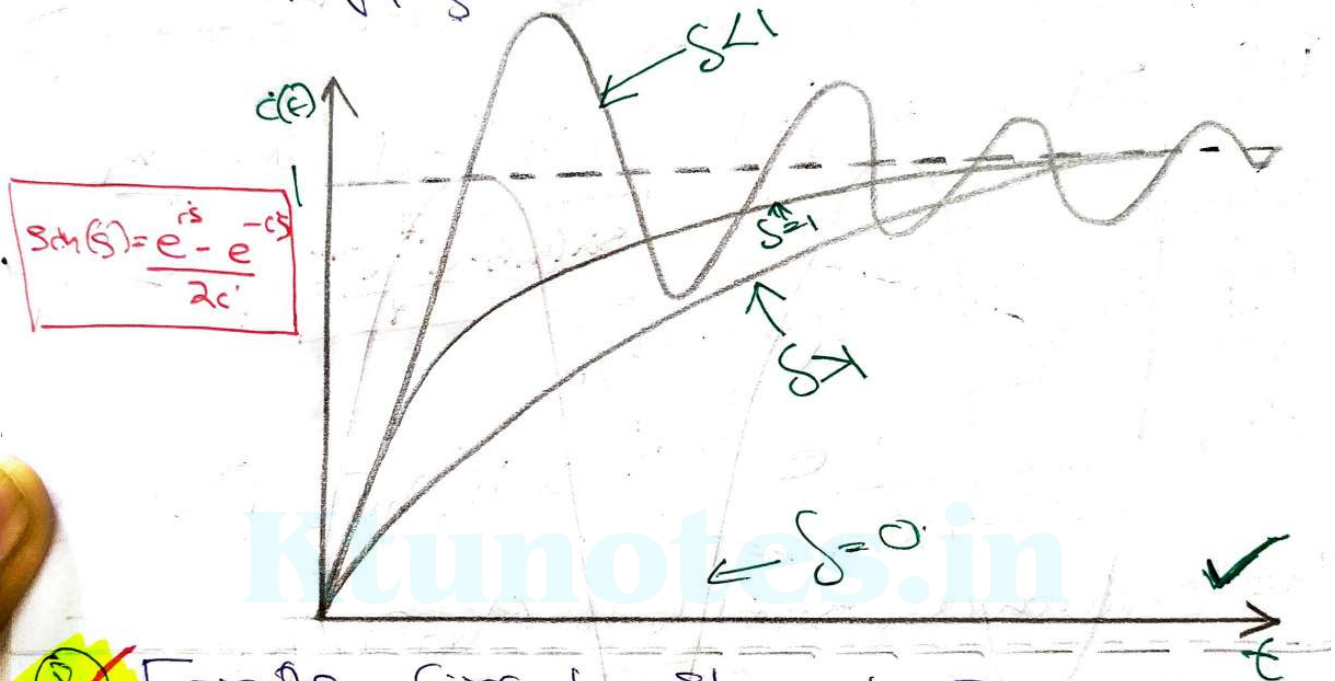
$$i(t) = \frac{V}{\omega_n \sqrt{1-\zeta^2}} e^{-\zeta \omega_n t} \sin \omega_n \sqrt{1-\zeta^2} t$$



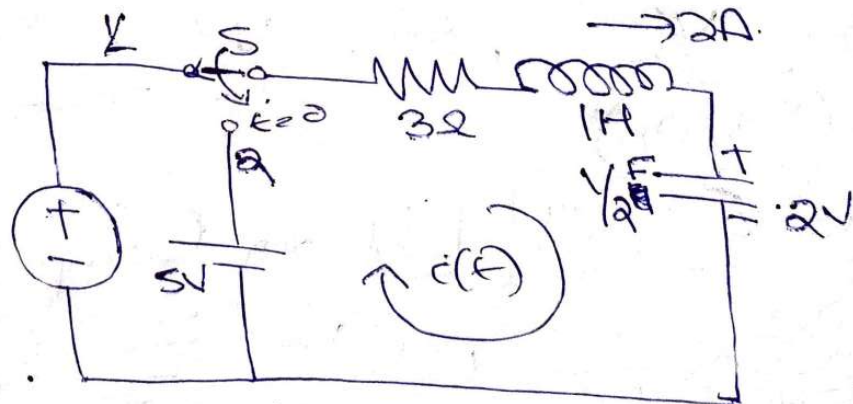Q. For the circuit shown in Fig. the switch is moved from position 1 to position 2 at $t=0$. Find $i(t)$, if $I_L(0^-)$ is 2A & $V_C(0^-)$ is 2V.



With Switch in position 1,
 $i_L(0^-) = 2A$, $V_C(0^-) = 2V$.

With Switch in position 2,

$$Ri(t) + L \frac{di}{dt} + \frac{1}{C} \int_0^t i(t) \cdot dt = 5$$

$$Ri(t) + L \frac{di}{dt} + \frac{1}{C} \int_0^t i(t) \cdot dt + 2 = 5$$

Taking Laplace's transform of the equation,

$$3I(s) + \cancel{SI(s)} - SI(s) - \underset{\substack{\uparrow \\ 2A}}{i(0^-)} + \frac{2}{s} I(s) + \frac{2}{s} = \frac{5}{s}$$

$$3I(s) + SI(s) - 2 + \frac{2}{s} I(s) = \frac{3}{s}$$

$$I(s) \left[3 + s + \frac{2}{s} \right] = \frac{3}{s} + 2$$

$$I(s) = \frac{\frac{3}{s} + 2}{3 + s + \frac{2}{s}} \Rightarrow \frac{2s+3}{(s+1)(s+2)}$$

$$\cancel{I(s) = \frac{2s+3}{(s+1)(s+2)}} \quad i(t) = e^{-t} + e^{-2t} A$$

By Partial Fraction Expansion,

$$\frac{2s+3}{(s+1)(s+2)} = \frac{A}{s+1} + \frac{B}{s+2}$$

$$A = \frac{2s+3}{s+2} \Big|_{s=-1} = A = \frac{-2+3}{-1+2} = 1$$


$$B = \frac{2s+3}{s+1} \Big|_{s=-2} = B = \frac{-4+3}{-2+1} = 1$$

$$I(s) = \frac{1}{s+1} + \frac{1}{s+2}$$

Taking Laplace Inverse,

$$i(t) = e^{-t} + e^{-2t} A$$

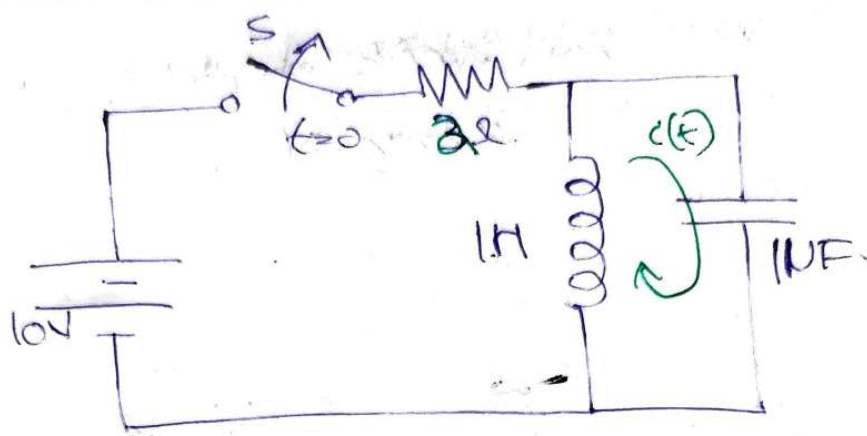For the circuit shown in Figure, the switch 'S' is closed, and steady state condition is reached. At $t=0$, the switch is open. Obtain the expression for current through the Inductor.



There is no voltage across the capacitor since inductor is short circuited.

At Steady State, $i_L(0^-) = \frac{10}{2} = \underline{\underline{5A}}$

$V_C(0^-) = \underline{\underline{0}}$ [Since inductor is short circuited]

At $t=0$, switch is Opened.

Apply KVL in circuit


$$\frac{di}{dt} + \frac{1}{10^{-6}} \int i(t) \cdot dt = 0.$$

$$sI(s) - i_L(0^-) + \frac{1}{s \times 10^{-6}} I(s) = 0.$$

$$s \cdot I(s) - 5 + \frac{10^6}{s} I(s) = 0$$

$$I(s) \cdot \left[s + \frac{10^6}{s} \right] = 5 \Rightarrow I(s) = \frac{5s}{s^2 + 10^6} \Rightarrow \underline{\underline{\frac{5s}{s^2 + (10^3)^2}}}$$
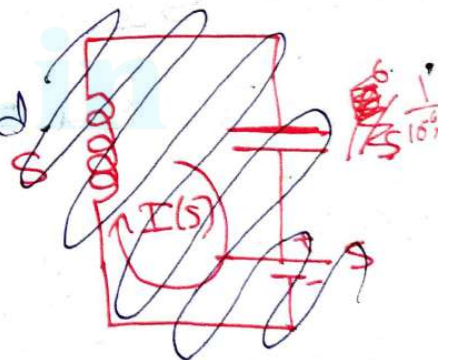
$$i(t) = \underline{\underline{5 \cos(1000)t \text{ A}}}$$




2-10-2022
Friday

Transformed Circuit Component

Representation

Step - Response of Series RL Circuit

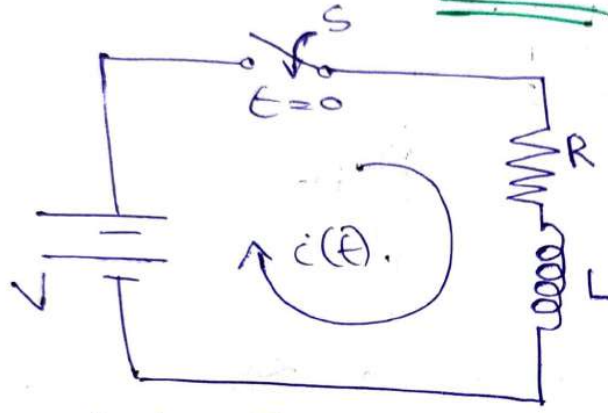

Let us assume that inductance is initially unenergized (That is there is no initially current flowing through it)

Writing KVL Equation

$$Ri(t) + L \frac{di(t)}{dt} = V \quad , \text{ Taking Laplace Transform}$$

$$RI(s) + LS I(s) - Li(0^+) = Vs$$

Since, we assume that there is no initial current through inductor.

$$I(s) [sL + R] = Vs \Rightarrow I(s) L [s + \frac{R}{L}] = Vs$$

$$I(s) = \frac{V}{L} \frac{1}{s(s + \frac{R}{L})}$$

Now, we can apply Partial Fraction Technique,

$$\frac{I(s)}{V/L} = \frac{1}{s(s + R/L)} = \frac{A}{s} + \frac{B}{s + R/L}$$


$$A = \frac{V/L}{s + R/L} \Big|_{s=0} = \frac{V}{R} \quad , \quad B = \frac{V/L}{s} \Big|_{s=-R/L} = -\frac{V}{R}$$

$$I(s) = \frac{V/R}{s} - \frac{V/R}{s + R/L} \Rightarrow \text{Taking Laplace's Inverse}$$

$$i(t) = \frac{V}{R} - \frac{V}{R} e^{-R/L t} \Rightarrow \frac{V}{R} [1 - e^{-R/L t}] \rightarrow \text{Forced Response}$$


$\frac{1}{s} \rightarrow \frac{1}{s} \rightarrow \frac{1}{s}$

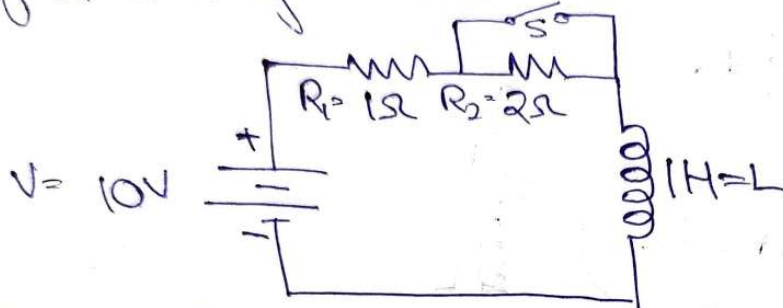Q) In the circuit shown in Figure, the Battery voltage is applied for a steady state period. Obtain the complete expression for the current after closing the switch 'S'.



Solution) The current is at steady state condition before closing the switch.

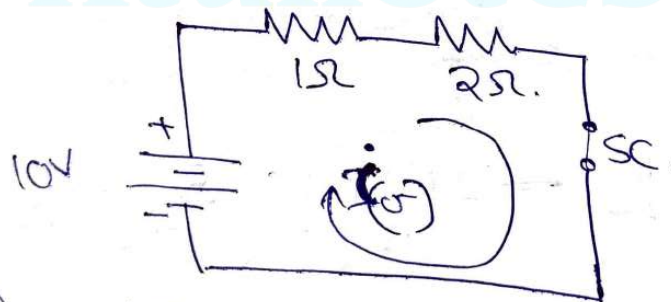Before closing the switch, the circuit attains steady state & inductor is short circuited.



$$i(0^-) = \frac{10}{3} \text{ A}$$

At $t=0$, the switch is closed, the R_2 becomes short-circuited $\therefore$ we get, the new circuit.



$$R_1 i(t) + L \frac{di}{dt} = V$$

Taking Laplace's Transform

$$R_1 I(s) + L [sI(s) - i(0^-)] = \frac{V}{s}$$

$$i(0^+) = i(0^-) = \frac{10}{40} \text{ A} \quad \text{KVL(s)} + \text{LS } I(s) - L i(0^-) = V/s$$

$$I(s) [sL + R] = V/s - L i(0^-)$$

$$I(s) [s+1] = \frac{10}{s} - \frac{10}{3} \Rightarrow I(s) = \frac{10}{s(s+1)} - \frac{10/3}{s+1}$$

$$\frac{10}{s(s+1)} = \frac{A}{s} + \frac{B}{s+1} \Rightarrow A = \frac{10}{s+1} \Big|_{s=0} = 10$$


$$B = \frac{10}{s} \Big|_{s=-1} = -10$$

$$I(s) = \frac{10}{s} - \frac{10}{s+1} - \frac{10/3}{s+1} = \frac{10}{s} - \frac{6.67}{s+1}$$

Taking Laplace's Inverse,

$$i(t) = 10 - 6.67 e^{-t} \text{ A}$$

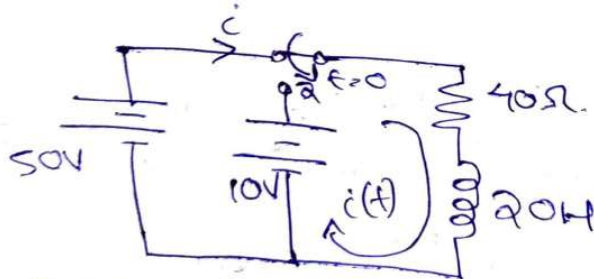For an RL series circuit, shown in Fig. the switch is position 1 for a long time, and moved to position 2 at $t=0$. Obtain the expression for $i(t)$ for $t > 0$.



Solution) With the switch in position (1), the critical current $i(0^-) = \frac{50}{40} = 1.25 \text{ A}$

With the switch in position (2),

$$\text{Apply KVL, } 40i(t) + 20 \frac{di}{dt} = 10$$

$$40I(s) + 20 [sI(s) - i(0^-)] = 10/s$$

[Inductor is behaving as a short circuit] $L = 20 \text{ mH}$

$$\frac{1}{s} \frac{d}{dt} \frac{1}{s}$$

$$40I(s) + 20sI(s) - 20 \times 1.25 = 10/s$$

$$I(s) [20s + 40] = \frac{10}{s} + 25$$

$$I(s) = \frac{\frac{10}{s} + 25}{20s + 40} = \frac{10}{20s[s+2]} + \frac{25}{20(s+2)}$$

$$I(s) = \frac{0.5}{s(s+2)} + \frac{1.25}{s+2}$$

$$\frac{0.5}{s(s+2)} = \frac{A}{s} + \frac{B}{s+2} \Rightarrow A = \frac{0.5}{s+2} \Big|_{s=-2} = \frac{0.5}{-2} = \underline{\underline{-0.25}}$$

$$B = \frac{0.5}{s} \Big|_{s=0} = \underline{\underline{0.25}}$$

$$I(s) = \frac{0.25}{s} - \frac{0.25}{s+2} + \frac{1.25}{s+2}$$


Taking Inverse Laplace,

$$i(t) = 0.25 - 0.25e^{-2t} + 1.25e^{-2t}$$


$$i(t) = \underline{\underline{0.25 + e^{-2t} \text{ A}}}$$

7-10-2020
Wednesday

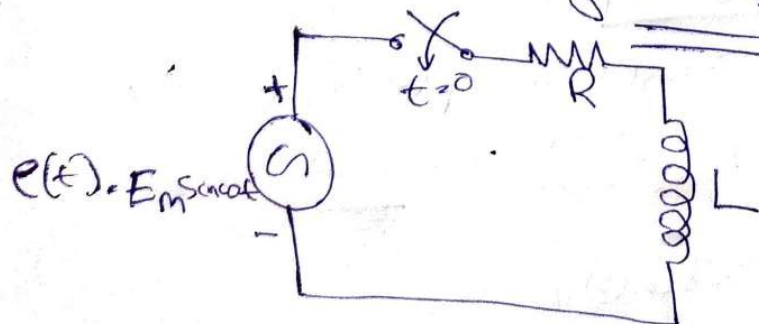Transient Analysis of Series
RL Circuit excited
by AC Source



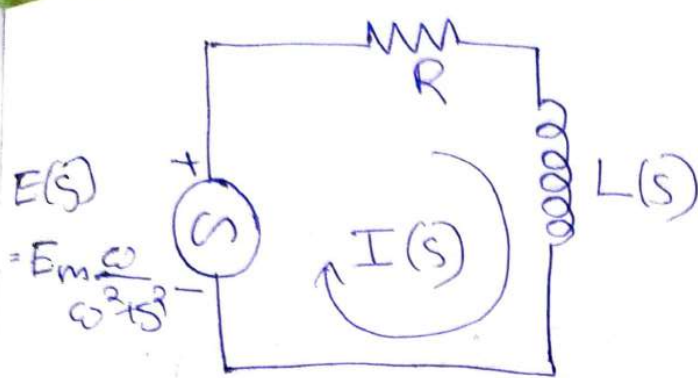There is no initial
stored energy in
the circuit.



$$I(s) = \frac{E(s)}{R + sL}$$

$$= \frac{E_m \frac{\omega}{\omega^2 + s^2}}{L \left[s + \frac{R}{L} \right]}$$

$$\Rightarrow \frac{\omega E_m}{L} = \frac{\omega E_m / L}{\left(s + \frac{R}{L} \right) (s^2 + \omega^2)}$$

Applying Partial Fraction method,

$$\Rightarrow \frac{A}{s + \frac{R}{L}} + \frac{Bs + C}{s^2 + \omega^2}$$

Where $A = \frac{\omega E_m / L}{s^2 + \omega^2} \Big|_{s = -\frac{R}{L}}$

$$\Rightarrow A = \frac{\omega E_m / L}{\frac{R^2}{L^2} + \omega^2}$$

$$A = \frac{\omega E_m}{L} \times \frac{L^2}{R^2 + \omega^2 L^2} \Rightarrow A = \frac{\omega E_m L}{R^2 + \omega^2 L^2} \Rightarrow \frac{\omega L \cdot E_m}{R^2 + \omega^2 L^2}$$

$$Z = \sqrt{R^2 + X_L^2} = \sqrt{R^2 + \omega^2 L^2}$$

$$Z^2 = R^2 + \omega^2 L^2$$

$$A = \frac{\omega L \cdot E_m}{Z^2}$$

$$\frac{\omega E_m}{L} = A(s^2 + \omega^2) + (Bs + C)\left(s + \frac{R}{L}\right)$$

$$= As^2 + A\omega^2 + Bs^2 + \frac{BSR}{L} + Cs + \frac{CR}{L}$$

Equating Co-efficients of \$s^2\$

$$A + B = 0 \quad \text{or} \quad B = -A = -\frac{\omega L E_m}{Z^2}$$

$$\frac{BR}{L} + C = 0 \Rightarrow C = -\frac{BR}{L}$$

$$B = \frac{\omega L E_m R}{L \cdot Z^2} \Rightarrow B = \frac{\omega E_m R}{Z^2}$$

$$I_L = \frac{1}{\omega} \frac{dI}{dt}$$

$$I(s) = \frac{\frac{\omega L E_m}{Z^2}}{s + \frac{R}{L}} + \frac{-\frac{\omega L E_m \cdot s + \frac{\omega R E_m}{Z^2}}{Z^2}}{s^2 + \omega^2}$$

$$I(s) = \frac{\omega L E_m}{Z^2} \cdot \frac{1}{s + \frac{R}{L}} - \frac{\omega L E_m \cdot s}{Z^2 (s^2 + \omega^2)} + \frac{R E_m \cdot \omega}{Z^2 (s^2 + \omega^2)}$$

$$i(t) = \frac{\omega L E_m}{Z^2} \cdot e^{-\frac{R}{L}t} - \frac{\omega L E_m}{Z^2} \cdot (\cos(\omega t)) + \frac{R E_m \sin(\omega t)}{Z^2}$$


$$i(t) = \frac{\omega L \cdot E_m}{Z^2} \cdot e^{-\frac{R}{L}t} + \frac{E_m}{Z^2} [R \cdot \sin \omega t - \omega L \cdot \cos \omega t]$$

Construct a Right Angled triangle,

$$\cos \phi = \frac{R}{Z}, \quad \sin \phi = \frac{\omega L}{Z}$$

$$R = Z \cdot \cos \phi$$

$$\omega L = Z \cdot \sin \phi$$

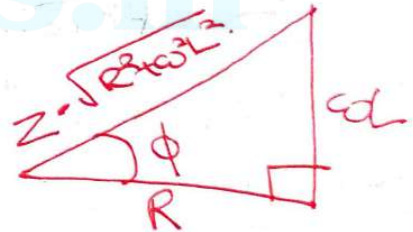

~~$$i(t) = \frac{Z \sin \phi E_m}{Z^2} e^{-\frac{R}{L}t}$$~~

$$i(t) = \frac{\omega L \cdot E_m}{Z^2} e^{-\frac{R}{L}t} + \frac{E_m}{Z^2} [Z \cdot \cos \phi \cdot \sin \omega t - Z \sin \phi \cdot \cos \omega t]$$

$$i(t) = \frac{\omega L \cdot E_m}{Z^2} e^{-\frac{R}{L}t} + \frac{E_m}{Z} [\cos \phi \cdot \sin \omega t - \sin \phi \cdot \cos \omega t]$$



$$i(t) = \frac{\omega L \cdot E_m}{Z^2} e^{-\frac{R}{L}t} + \frac{E_m}{Z} \cdot \sin(\omega t - \phi)$$

Transient Part

Steady State Part. ✓

Transient Analysis of Series RC Circuit excited by AC Source.

RC circuit excited by AC source.

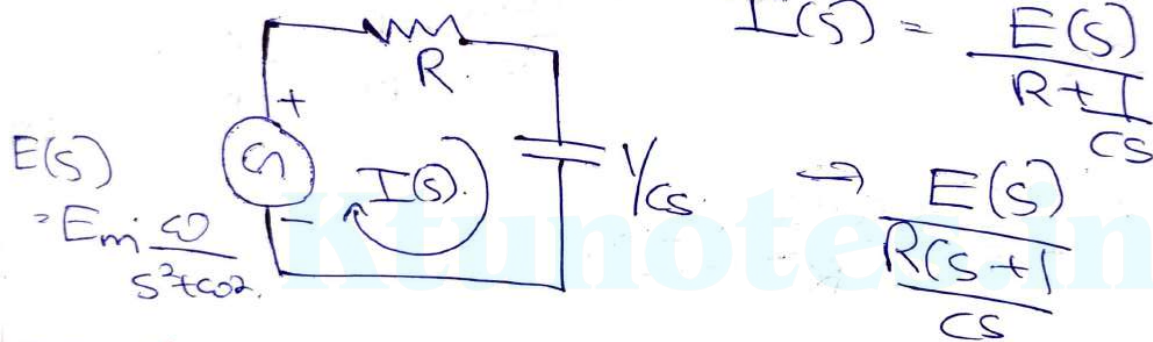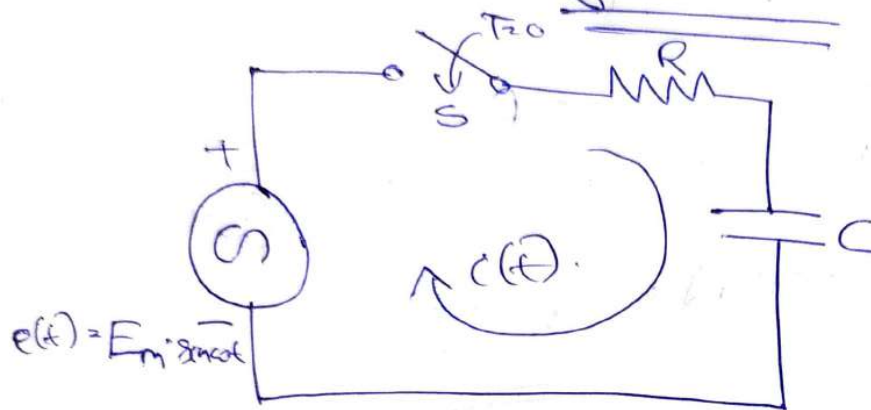

$$I(s) = \frac{E(s)}{R + \frac{1}{Cs}}$$

$$\rightarrow \frac{E(s)}{\frac{R(s + \frac{1}{RC})}{Cs}}$$

$$\Rightarrow \frac{SEm \cdot \frac{\omega}{s^2 + \omega^2}}{R \left[s + \frac{1}{RC} \right]}$$

$$\Rightarrow I(s) = \frac{SEm \cdot \frac{\omega}{\omega^2 + s^2}}{R \left[s + \frac{1}{RC} \right]}$$

$$I(s) = \frac{\omega Em}{R} \cdot \frac{s}{\left(s + \frac{1}{RC} \right) (s^2 + \omega^2)}$$

Applying Partial Fraction Technique,

$$I(s) = \frac{A}{s + \frac{1}{RC}} + \frac{Bs + C}{s^2 + \omega^2}$$

1. $\frac{1}{s}$
2. $\frac{1}{s^2}$
3. $\frac{1}{s^3}$

$$A = \frac{\omega \cdot E_m}{R} \cdot \frac{S}{s^2 + \omega^2} \Big|_{s = -1/Rc}$$

$$A = \frac{\omega E_m}{R} \times \frac{-1}{RC(s^2 + \omega^2)} \Rightarrow A = \frac{-\omega E_m}{R^2 C (s^2 + \omega^2)}$$

$$A = \frac{-\frac{E_m}{\omega C}}{R^2 + \left(\frac{1}{\omega C}\right)^2} \Rightarrow A = \frac{-\frac{E_m}{\omega C}}{\underline{\underline{Z^2 \omega C}}}$$

$$B = \frac{E_m}{Z^2 \omega C} \quad 1 \quad C = \frac{\omega E_m}{R} - \frac{B}{RC} - \frac{\omega E_m}{R} - \frac{E_m}{Z^2 \omega C R}$$

$$\Rightarrow \frac{Z^2 \omega C^2 \times \omega E_m - E_m}{Z^2 \omega C^2 R}$$

$$\Rightarrow E_m \left[\frac{\omega^2 C^2 Z^2 - 1}{\omega C^2 Z^2 R} \right] \Rightarrow E_m \left[\cancel{\omega^2 C^2} \right]$$

$$C = \frac{E_m}{\omega R C^2 Z^2} \left[\omega^2 C^2 \left[R^2 + \left(\frac{1}{\omega C}\right)^2 \right] - 1 \right]$$

$$C = \frac{E_m}{\omega R C^2 Z^2} \left[\omega^2 C^2 R^2 + 1 - 1 \right]$$


$$C = \frac{E_m \cdot \omega R}{\underline{\underline{Z^2}}}$$

$$I(s) = \frac{-\frac{E_m}{Z^2 \omega C}}{s + \frac{1}{RC}} + \frac{\left(\frac{E_m}{Z^2 \omega C}\right)s + \frac{E_m \omega R}{Z^2}}{s^2 + \omega^2}$$

$$I(s) = -\frac{E_m}{Z^2 \omega C} \cdot \frac{1}{s + \frac{1}{RC}} + \frac{E_m}{\omega C Z^2} \cdot \frac{1}{s^2 + \omega^2} + \frac{R E_m}{Z^2} \cdot \frac{\omega}{s^2 + \omega^2}$$

$$i(t) = \frac{-E_m}{\omega C Z^2} \cdot e^{-t/RC} + \frac{E_m}{\omega C Z^2} \cdot (\cos(\omega t) + \frac{R E_m}{Z^2} \sin(\omega t))$$
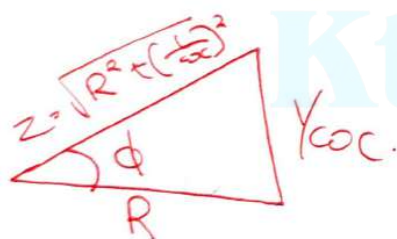
$$i(t) = \frac{-E_m}{\omega C Z^2} \cdot e^{-t/RC} + \frac{E_m}{Z^2} \left[\cos(\omega t) \cdot \frac{1}{\omega C} + \sin(\omega t) \cdot R \right]$$



$$= \frac{E_m}{Z^2} \left[\cos \omega t \cdot \sin \phi + \sin \omega t \cdot \cos \phi \right]$$

$$i(t) = \frac{-E_m}{\omega C Z^2} \cdot e^{-t/RC} + \frac{E_m}{Z^2} \cdot \sin(\omega t + \phi)$$



Transient Part

Steady State Part

U.W Transient Analysis of Series RLC circuit.
excited by AC source

Q. In the RL circuit shown in Fig. the switch is closed at $t=0$. Find the current $i(t)$ & voltage across resistance & inductor.

1. L
2. ϕ
3. ω

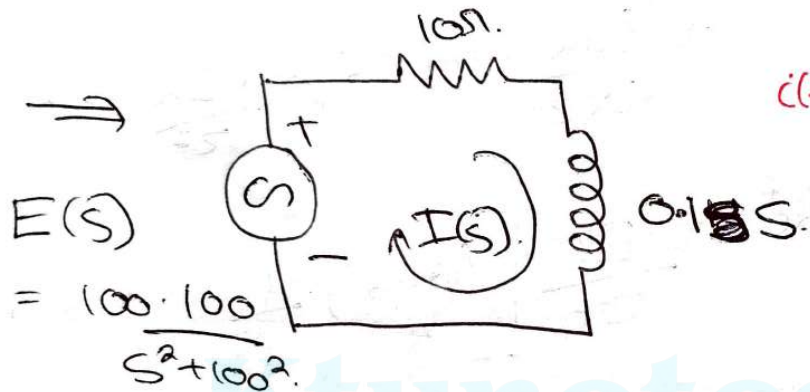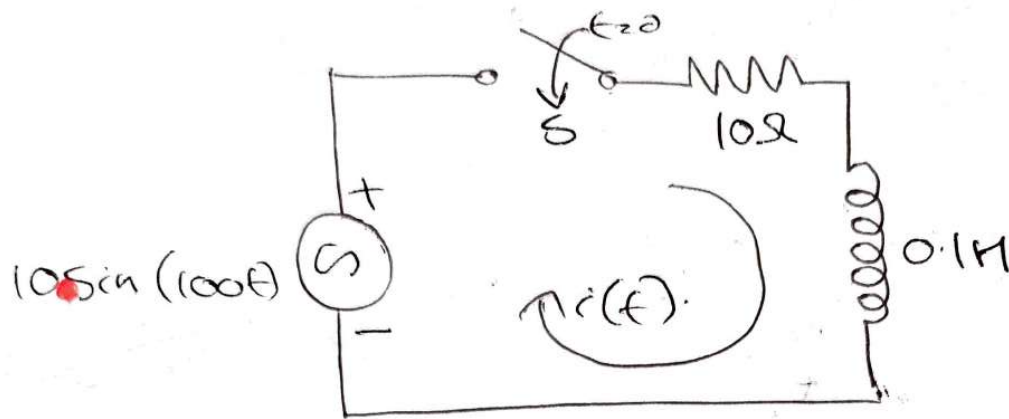

$$i(t) = \frac{V_m}{Z} \sin(\omega t + \phi - \tan^{-1}(\frac{\omega L}{R}))$$

$$I(s) = \frac{E(s)}{0.1s + 10} \Rightarrow \frac{10^4}{s^2 + 10^4} \Rightarrow \frac{10^4}{0.1[s + 100][s^2 + 10^4]} \Rightarrow \frac{10^4}{[s + 100][s^2 + 10^4]}$$

Applying Partial Fraction Technique,

$$\Rightarrow \frac{A}{s + 100} + \frac{Bs + C}{s^2 + 10^4}$$

$$A = \frac{10^4}{s^2 + 10^4} \Big|_{s = -100} = \frac{10000}{10^4 + 10^1} = \frac{1}{2} \approx 0.5$$

$$B = -0.5$$


$$10^4 = A[s^2 + 10^4] + [Bs + C][s + 100]$$

$$100B + C = 0 \Rightarrow C = -100 \times -0.5 = \underline{\underline{50}}$$

$$I(s) = \frac{0.5}{s+100} - \frac{0.5s + 50}{s^2 + 104}$$

$$I(s) = \frac{0.5}{s+100} - \frac{0.5s}{s^2+104} + \frac{100}{2} \times \frac{100}{s^2+104}$$
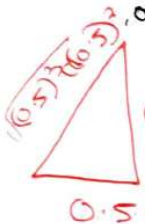
$$i(t) = 0.5e^{-100t} - 0.5 \cdot (\cos(100t) + 0.5 \sin(100t))$$



$$0.5 \Rightarrow 0.5e^{-100t} + \sin(100t) \cdot \cos\phi$$

$$\cos\phi = \frac{0.5}{0.707} \Rightarrow 0.5 = 0.707 \cos\phi$$

$$\sin\phi = \frac{0.5}{0.707} \Rightarrow 0.5 = 0.707 \sin\phi$$

$$i(t) = 0.5e^{-100t} + 0.707 \sin(100t) \cdot \cos\phi - 0.707 \cdot \cos(100t) \cdot \sin\phi$$

$$- 0.707 \sin\phi \sin(100t)$$

$$i(t) = 0.5e^{-100t} + 0.707 \cdot \sin(100t - \phi)$$

$$i(t) = 0.5e^{-100t} + 0.707 \cdot \sin(100t - 45^\circ)$$


$$\tan^{-1}\left(\frac{\omega L}{R}\right) = \phi$$

$$\tan\phi > 1$$


$$\phi = 45^\circ$$

10-10-2020
Saturday

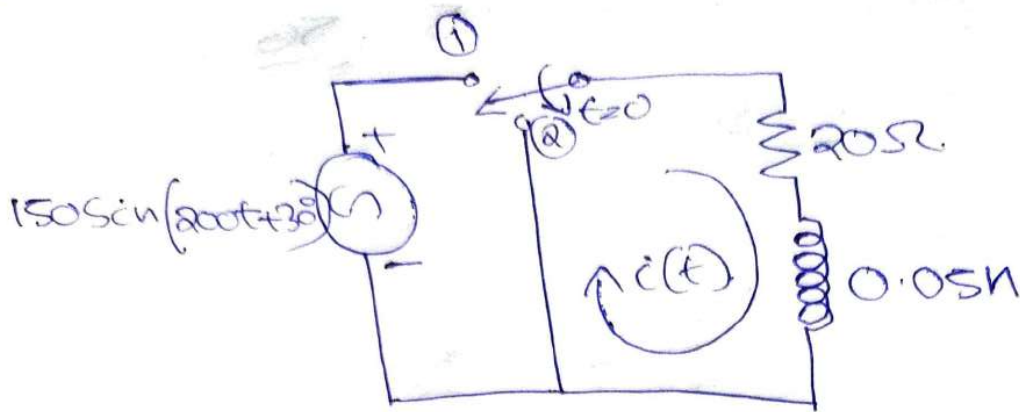In the circuit, shown in figure, the switch remained in position 1 until steady state is reached. At time $t=0$ the switch is changed to position 2. Find $i(t)$.



Solution) At Position 1

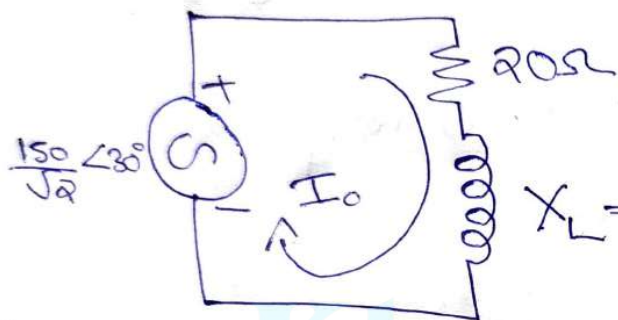

$$Z = R + jX_L = R + j\omega L$$


Let I_0 be the magnitude of rms value of current flowing in the circuit.

$$|I_0| = \frac{150/\sqrt{2}}{\sqrt{(20)^2 + (10)^2}} \Rightarrow |I_0| = \frac{150}{\sqrt{500}}$$


$$|I_0| = 4.74 \text{ A}$$

At Position 2

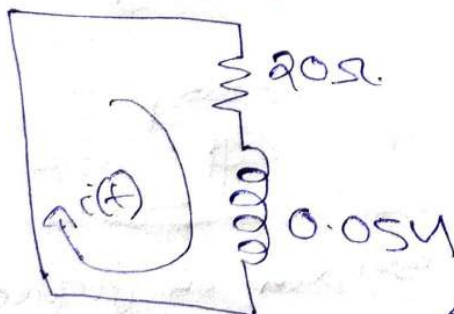→ Mrs steady rms current I_0 will be the initial current when the switch is moved from position 1 to position 2.



4.74 A

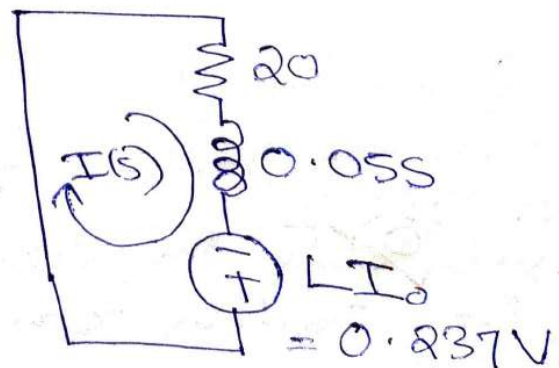


$$\Rightarrow [20 + 0.05] I(s) = 0.237$$

$$0.05 \left[s + \frac{20}{0.05} \right] I(s) = 0.237$$

$$I(s) = \frac{4.74}{s+400} \Rightarrow \text{Now, Taking Inverse Laplace's of.}$$

$$i(t) = 4.74 e^{-400t}$$

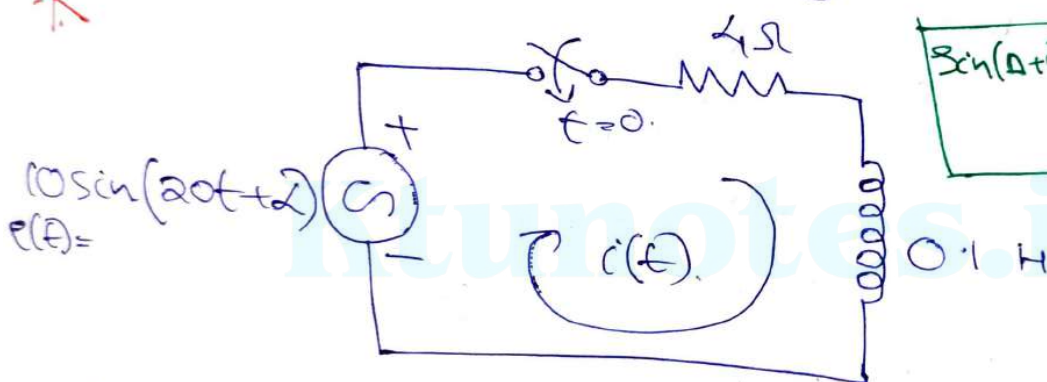Q In the circuit shown in Figure, the switch is closed at a particular value of α so that there is no transient in the RL circuit, find the value of α .




$$\sin(A+B) = \sin A \cdot \cos B + \cos A \cdot \sin B$$

$$\text{Solution) } E(s) = L[10 \sin(20t + \alpha)]$$

$$\Rightarrow 10L[\sin 20t \cdot \cos \alpha + \cos 20t \cdot \sin \alpha]$$

$$\Rightarrow 10 \cos \alpha \times \frac{20}{s^2 + 400} + 10 \sin \alpha \times \frac{s}{s^2 + 400}$$
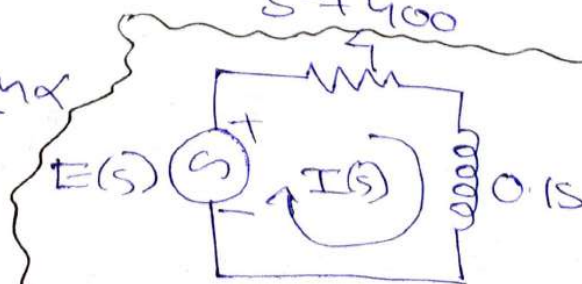
$$\Rightarrow \frac{200 \cos \alpha + 10 s \sin \alpha}{s^2 + 400}$$



$$I(s) = \frac{200 \cos \alpha + 10 s \sin \alpha}{s^2 + 400}$$

$$\Rightarrow [4 + 0.1s] I(s) = E(s)$$

$$\Rightarrow 0.1 \left[s + \frac{4}{0.1} \right] I(s) = E(s)$$

$$\Rightarrow I(s) = \frac{10E(s)}{s + 40}$$

$$I(s) = \frac{2000 \cos \alpha + 100 \sin \alpha \cdot s}{(s + 40)(s^2 + 400)}$$

$$I(s) = \frac{A}{s + 40} + \frac{Bs + C}{s^2 + 400}$$

$$A = \frac{2000 \cos \alpha + 100 \sin \alpha}{s^2 + 400} \Big|_{s = -40}$$

~~$$A = \frac{2000 \cos \alpha + 100 \sin \alpha}{s^2 + 400} \Big|_{s = -40}$$~~

$$A = \frac{100 \cos \alpha - 200 \sin \alpha}{s^2 + 400}$$

$$\Rightarrow A(s^2 + 400) + (Bs + C)(s + 40)$$

Equating the co-efficients of s^2 .

$$B = -A = -\cos \alpha + 2 \sin \alpha$$

Equating co-efficients of s

$$100 \sin \alpha = 40B + C$$

$$C = 40 \cos \alpha + 20 \sin \alpha$$

$$I(s) = \frac{(100 - 2 \sin \alpha)}{s + 40} + \frac{(-100 + 2 \sin \alpha)s + 40(100 + 20 \sin \alpha)}{s^2 + 400}$$

$$I(s) = \frac{A}{s + 40} + \frac{B s}{s^2 + 400} + \frac{C \times 20}{20(s^2 + 400)}$$

$$i(t) = \underbrace{A e^{-40t}}_{\text{Transient}} + \underbrace{B \cos(20t) + \frac{C}{20} \sin(20t)}_{\text{Steady State}}$$


For No transients in current $i(t)$, the transient part must be zero.

$$A e^{-40t} = 0 \quad / \quad \text{At } t = 0, e^{-40 \times 0} = 1, \underline{A = 0}$$

$$\text{If } 100 - 2 \sin \alpha = 0 \Rightarrow 2 \sin \alpha = 100$$

$$\tan \alpha = \frac{1}{2} \Rightarrow \boxed{\alpha = 26.5^\circ}$$

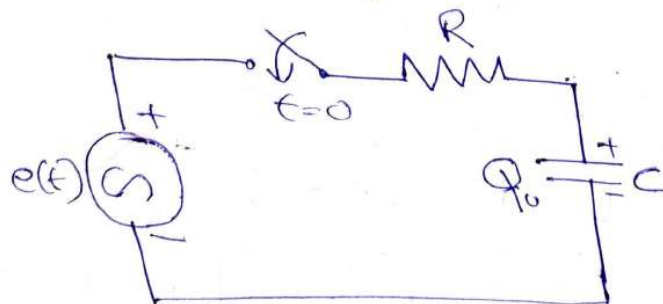Q) For the RC circuit shown in Figure, the switch is closed @ $t = 0$. Determine the voltage across the capacitor.



$$Q_0 = 250 \text{ nC}$$


$$e(t) = 100 \sin(200t + 40^\circ) \text{ V}$$

$$i_C = \frac{1}{C} \frac{dq_C}{dt}$$

Solution) $E(s) = 100(100 \times 40 \times \frac{200}{s^2 + 200^2} + 100 \sin 40 \times \frac{s}{s^2 + 200^2})$

$$E(s) = \frac{64.218s + 15320.88}{s^2 + (200)^2}$$

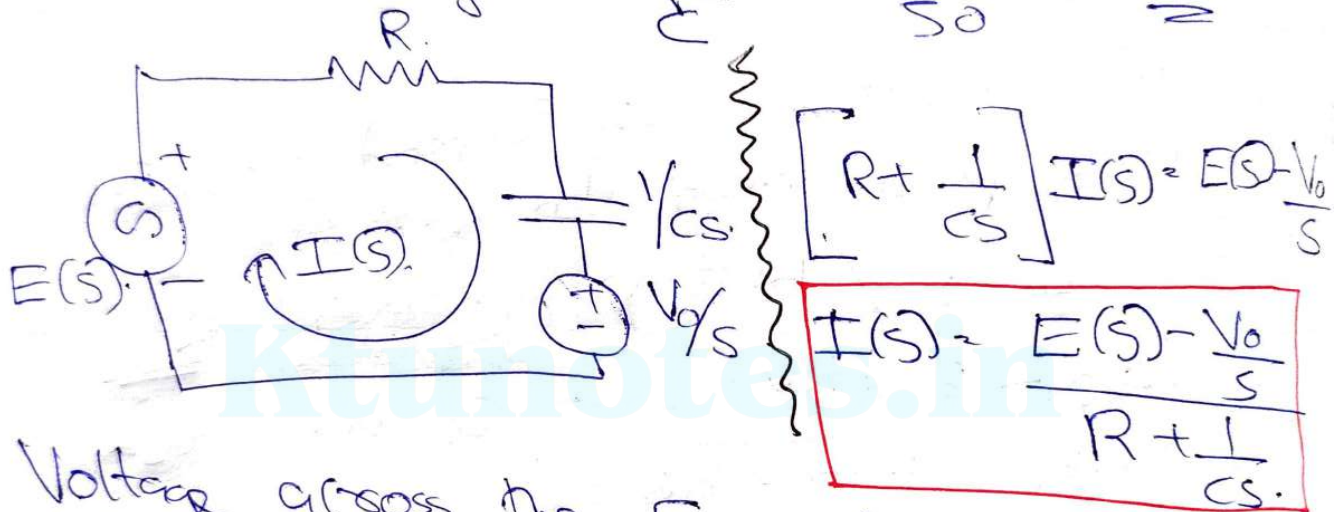Initial Voltage = $\frac{Q_0}{C} = \frac{250 \times 10^{-6}}{50} = 5V$



Voltage across the Capacitor

$$V_c(s) = \frac{1}{cs} I(s) + \frac{V_0}{s}$$

$$V_c(s) = \frac{1}{cs} \left[\frac{E(s) - \frac{V_0}{s}}{R + \frac{1}{cs}} \right] + \frac{V_0}{s}$$

$$V_c(s) = \frac{cs}{cs} \left[\frac{E(s) - \frac{V_0}{s}}{Rcs + 1} \right] + \frac{V_0}{s}$$

$$V_c(s) = \frac{1}{Rc} \left[\frac{E(s) - \frac{V_0}{s}}{s + 1/Rc} \right] + \frac{V_0}{s}$$

$$V_c(s) = \frac{1}{RC} \cdot \frac{E(s)}{s + \frac{1}{RC}} - \frac{V_0/s}{RC \left[s + \frac{1}{RC} \right]} + \frac{V_0}{s}$$

$$V_c(s) = \frac{1}{RC} \cdot \frac{E(s)}{s + \frac{1}{RC}} + \frac{V_0}{s} \left[1 - \frac{1}{RC \left[s + \frac{1}{RC} \right]} \right]$$

$$V_c(s) = \frac{1}{RC} \cdot \frac{E(s)}{s + \frac{1}{RC}} + \frac{V_0}{s} \left[\frac{RC \left[s + \frac{1}{RC} \right] - 1}{RC \left[1 + \frac{1}{RC} \right]} \right]$$

$$V_c(s) = \frac{V_0}{s} \left[\frac{sRC + 1 - 1}{RC + 1} \right] \Rightarrow V_c(s) = \frac{V_0 \times 8RC}{8 RC \left[1 + \frac{1}{RC} \right]}$$

$$V_c(s) = \frac{1}{RC} \cdot \frac{E(s)}{s + \frac{1}{RC}} + \frac{V_0}{s + \frac{1}{RC}}$$

$$V_c(s) =$$

$$\frac{200 (64.2785 + 15320.88)}{(s+200)(s^2 + (200)^2)} + \frac{s}{s+200}$$

$$V_c(s) = \frac{12855.76s + 3064176}{(s+200)(s^2 + (200)^2)} + \frac{s}{s+200}$$

$$V_c(s) = \frac{A}{s+200} + \frac{Bs+C}{s^2 + (200)^2}$$

$$A = 6.1628$$

$$B = -6.1628$$

$$C = 14088.33$$

$$16$$

$$\frac{1}{2} \phi_2$$

$$V_C(s) = \frac{6.1628}{s+200} + \frac{-6.1628s + 1408 \times 32}{s^2 + (200)^2} + \frac{s}{s+200}$$

$$\Rightarrow \frac{6.1628}{s+200} + \frac{s}{s+200} - \frac{6.1628 \times s}{s^2 + (200)^2} +$$

$$\frac{1408 \times 32}{200} \times \frac{200}{s^2 + (200)^2}$$

Calculate damping ratio?

Solution The ratio of real part to imaginary part.

of a circuit & it exists for critical damping is called damping ratio.

Taking L^{-1}

$$V_C(t) = 11.1628 e^{-200t} + 6.1628 \cdot (\cos(200t) +$$

$$70.4416 \sin(200t))$$