

EEET202

PHINES & TRANSFORMERS

MODULE: 4

ecture:3 – Phasor Diagram

Prepared By,

ADARSH SR

Asst. Professor

EEE Department



SCET Kodakara




Syllabus

ers –constructional details, principle of operation, EMF equation, convention, magnetising current, transformation ratio, phasor no load and on load, equivalent circuit, percentage and per unit regulation. Transformer losses and efficiency, condition for 7/A rating. Testing of transformers– polarity test, open circuit test, Sumpner's test – separation of losses, all day efficiency.Parallel transformers– numerical problems

Transformer on No-Load

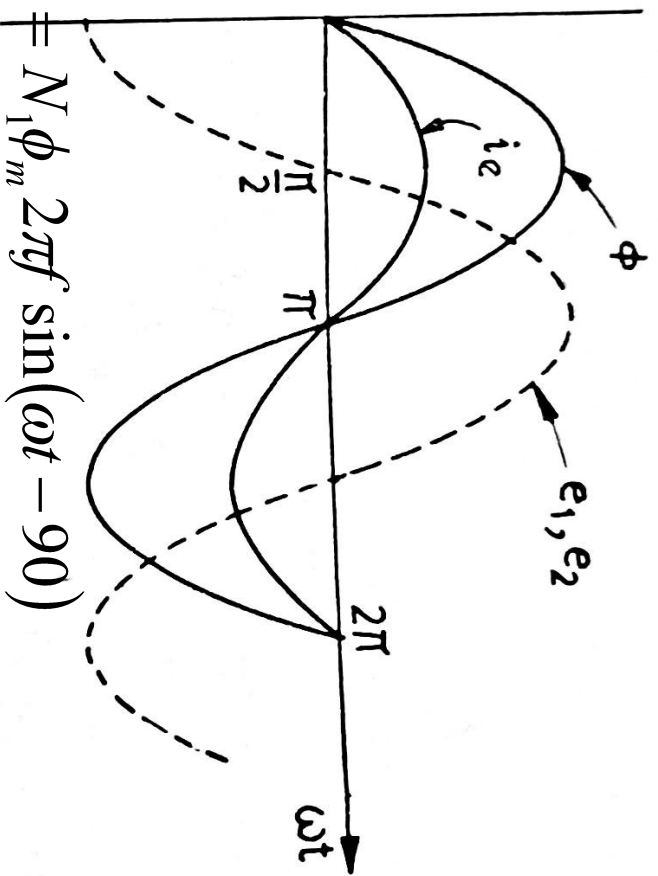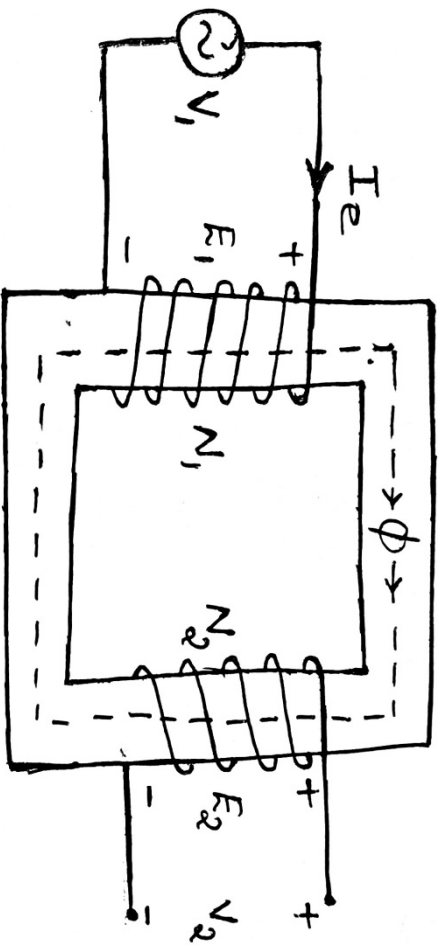

Transformer on No-Load

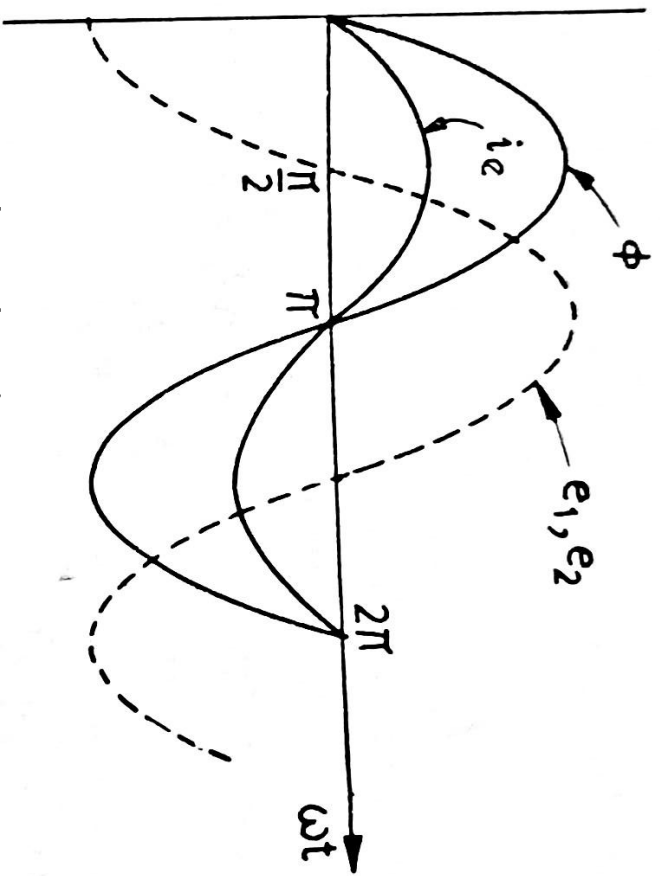


$$\phi = \phi_m \sin \omega t$$

$$e_1 = N_1 \phi_m 2\pi f \sin(\omega t - 90^\circ)$$

$$e_2 = N_2 \phi_m 2\pi f \sin(\omega t - 90^\circ)$$

Transformer on Load

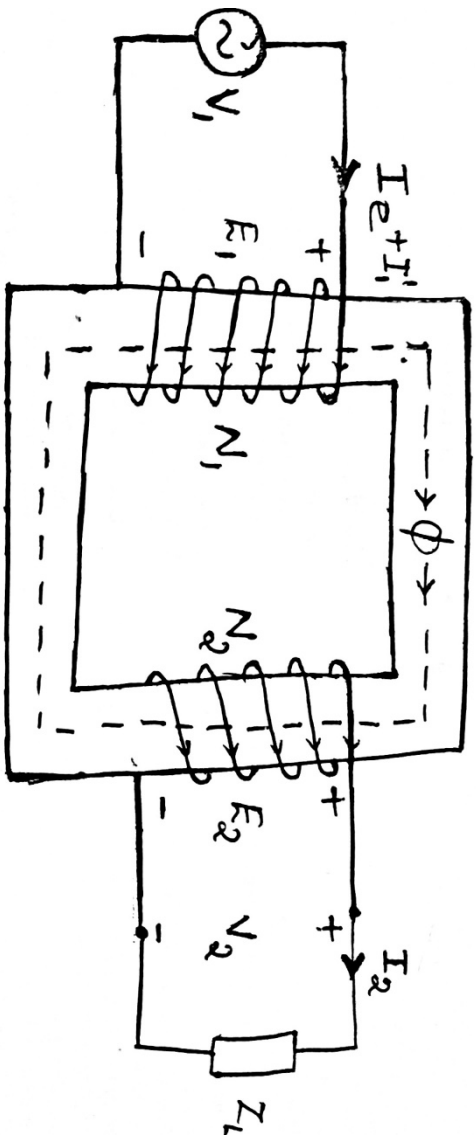

$$\phi = \phi_m \sin \omega t$$

$$e_1 = N_1 \phi_m 2\pi f \sin(\omega t - 90^\circ)$$

$$e_2 = N_2 \phi_m 2\pi f \sin(\omega t - 90^\circ)$$

Transformer on Load

er is loaded, a current I_2 flows through the
ng.

roduce a flux, and it will oppose the main flux ϕ .
flux, will cause reduction in E_1 .

nsformer, $V_1 = -E_1$

ant, E_1 can not be varied.

current I_1' will be drawn from the supply to
reduction in main flux.

current I_1 will be equal to the vector sum of I_1'

$$\vec{I_e} + \vec{I_1'}$$

Transformer on No-Load

Transformer, there will be following imperfections:


Transformer core loss: Current I_e will not be in phase with flux lags behind the current.

Winding resistance: In the primary side there will be a drop across this winding resistance.


Leakage flux: This leakage flux will induce an emf in the secondary winding and according to Lenz's law, it will oppose the primary flux. This can be represented as a reactance acting along with the primary resistance.

$$+ \overline{I_e r_1} + j \overline{I_e x_1}$$


Transformer on No-Load

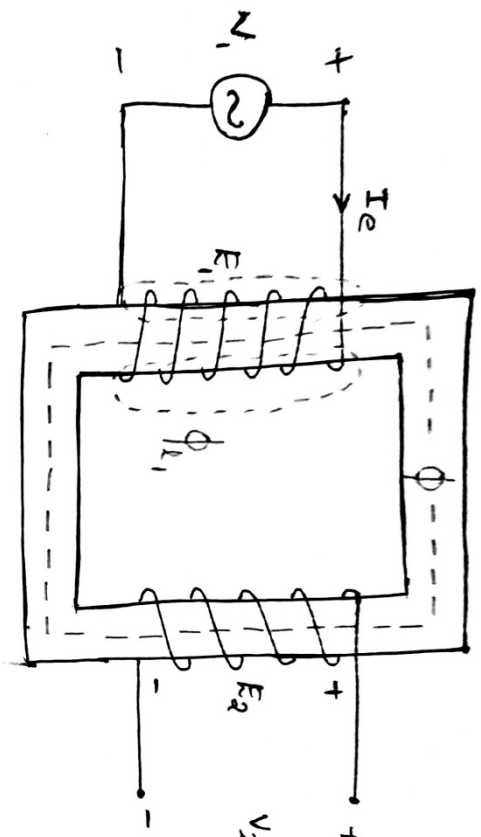

H_1 or I_e

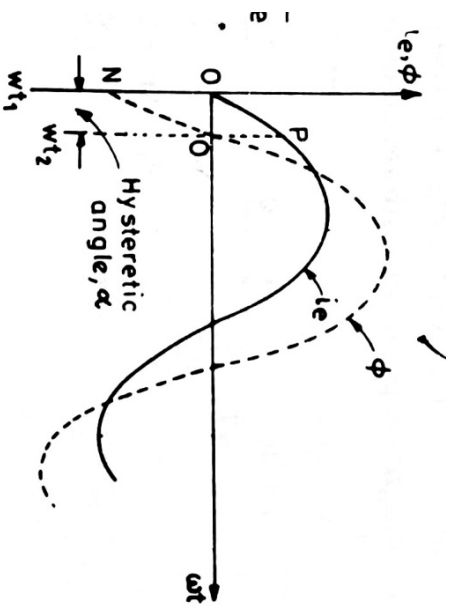

Transformer on No-Load

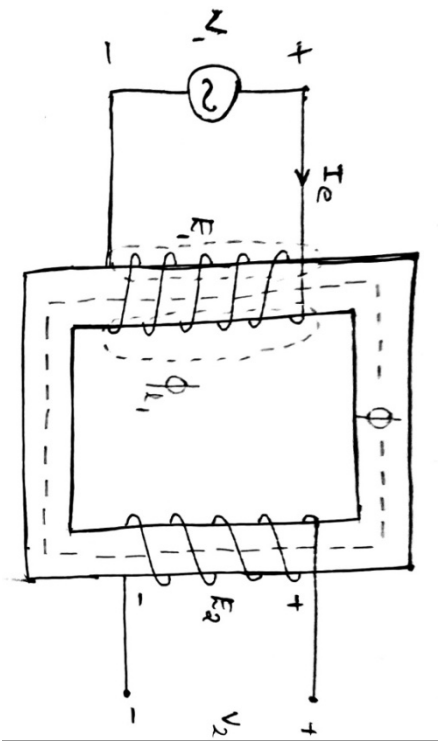


ϕ

I_e is called as **no-load current** or **exciting current**.

It can be resolved into two components.

- Along x-axis: I_m – **Magnetizing component**
- Along y-axis: I_c – **Core loss component**

Real Transformer on Load

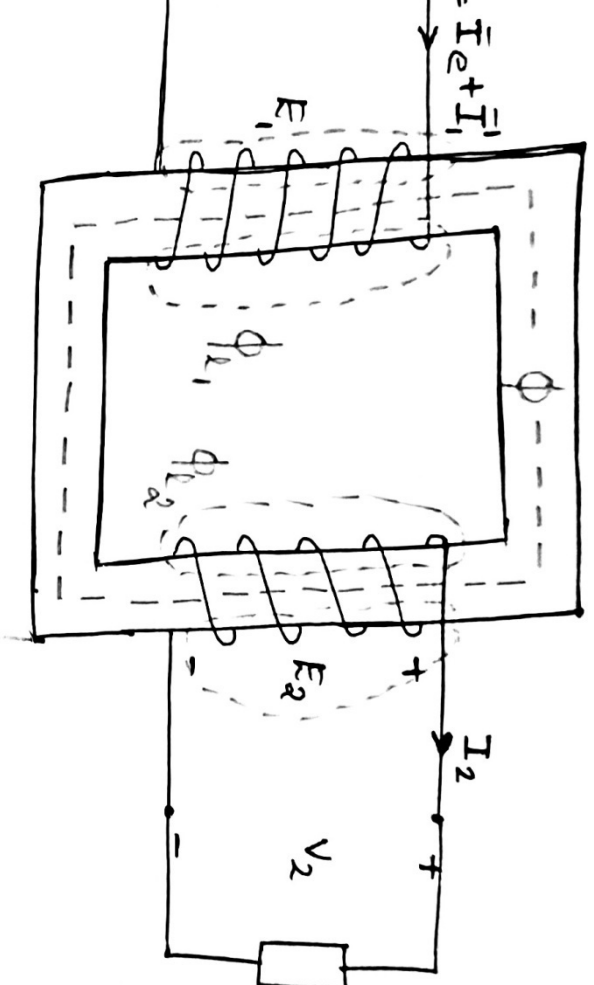

Local Transformer on Load

er is loaded, a current I_2 flows through the
ng.

winding resistance and leakage reactance at
hence, $\overline{E_2} = \overline{V_2} + \overline{I_2 r_2} + j \overline{I_2 x_2}$

urrent fill produce a flux, and it will oppose the

is demagnetizing effect, an extra current(I_1') is
supply.

$$\overline{I_1'}$$

ing resistance and leakage reactance at primary

$$\overline{+ I_1 r_1} + j \overline{I_1 x_1}$$

Transformer on Load

am

erence.

θ_e , which leads the flux by some angle α .

components. I_m along x axis and I_c along y axis.

by 90° . Reverse E_1 to get $-E_1$.

rticular direction.

to the nature of load.

o get E_2 .

, .


at I_1 .

o $-E_1$ to get V_1 .

and I_1 can be marked as θ_1 and $(\cos \theta_1)$ will be the
tor.

- ✓ For Resistive load (upf):
 I_2 and V_2 are in phase
- ✓ For RL load (lagging pf):
 I_2 lags V_2
- ✓ For RC load (leading pf):
 I_2 leads V_2

Transformer on Unity PF Load

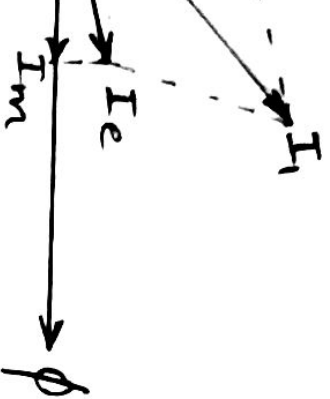

Transformer on Lagging PF Load



Transformer on Leading PF Load

