

EEET202

CHINES & TRANSFORMERS

MODULE: 4

- Equivalent Circuit, Losses and Efficiency

Prepared By,

ADARSH SR

Asst. Professor

EEE Department


SCET Kodakara

Syllabus



ers –constructional details, principle of operation, EMF equation, convention, magnetising current, transformation ratio, phasor no load and on load, equivalent circuit, percentage and per unit regulation. Transformer losses and efficiency, condition for 7/A rating. Testing of transformers– polarity test, open circuit test, Sumpner's test – separation of losses, all day efficiency.Parallel transformers– numerical problems

Equivalent Circuit

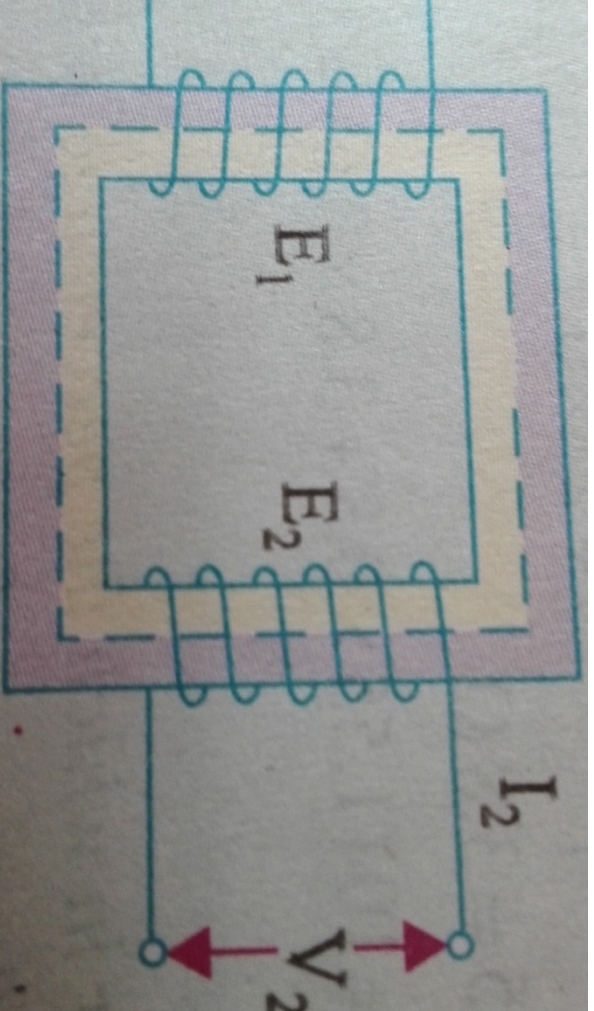
t of a machine means, the circuit which exactly
performance and working of the machine.



Equivalent Circuit

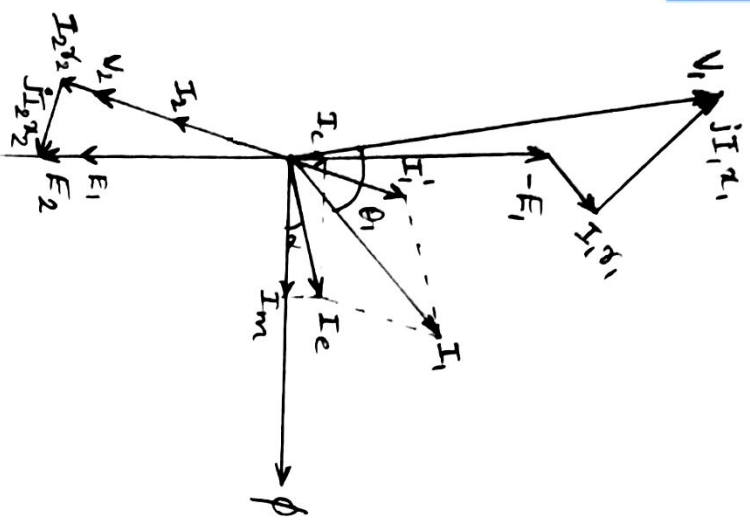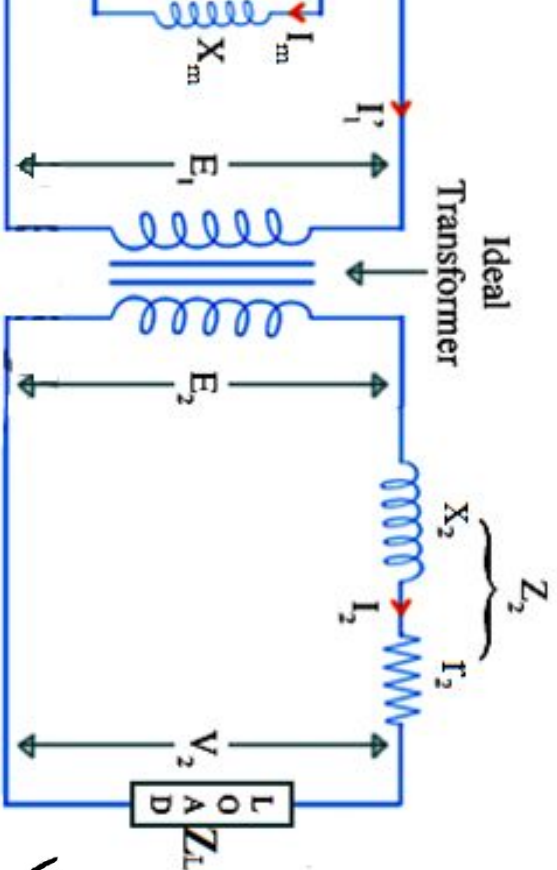

Equivalent Circuit referred to Primary

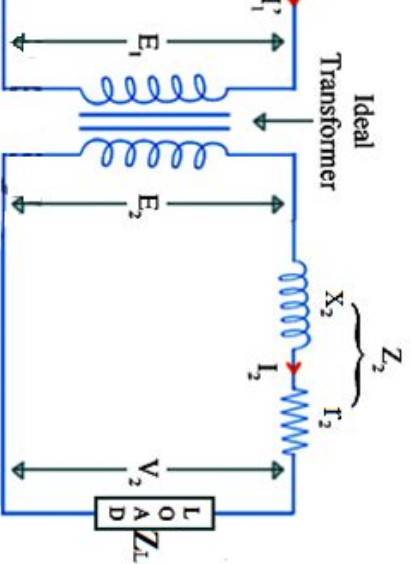


$$\frac{V_2}{V_1} = K = \frac{I_1}{I_2}$$

$$V_2' = \frac{V_2}{K}$$

$$I_2' = KI_2$$


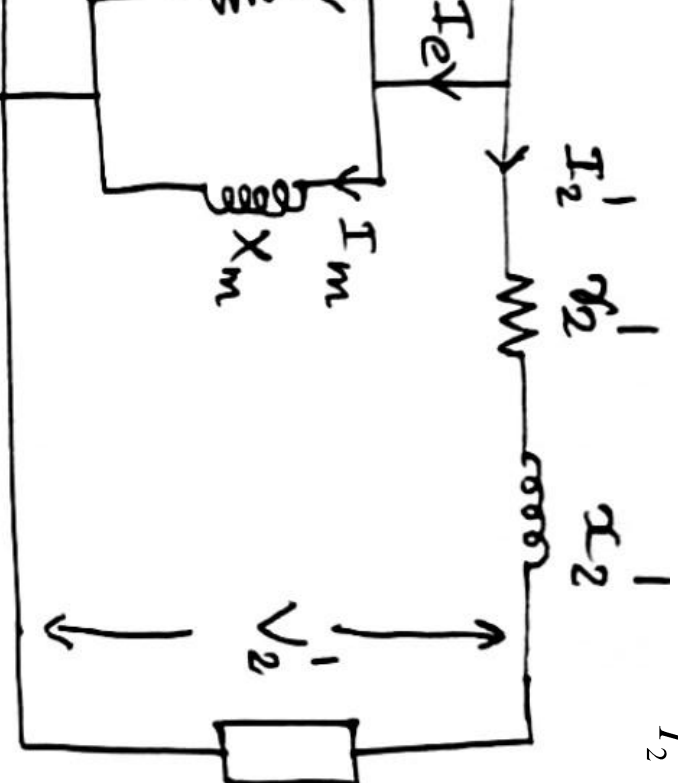
$$Z_2' = \frac{V_2'}{I_2'} = \frac{(V_2/K)}{KI_2} = \frac{1}{K^2} \frac{V_2}{I_2} = \frac{Z_2}{K^2}$$




$$r_2' = \frac{r_2}{K^2}$$

$$x_2' = \frac{x_2}{K^2}$$

Approximate Equivalent Circuit

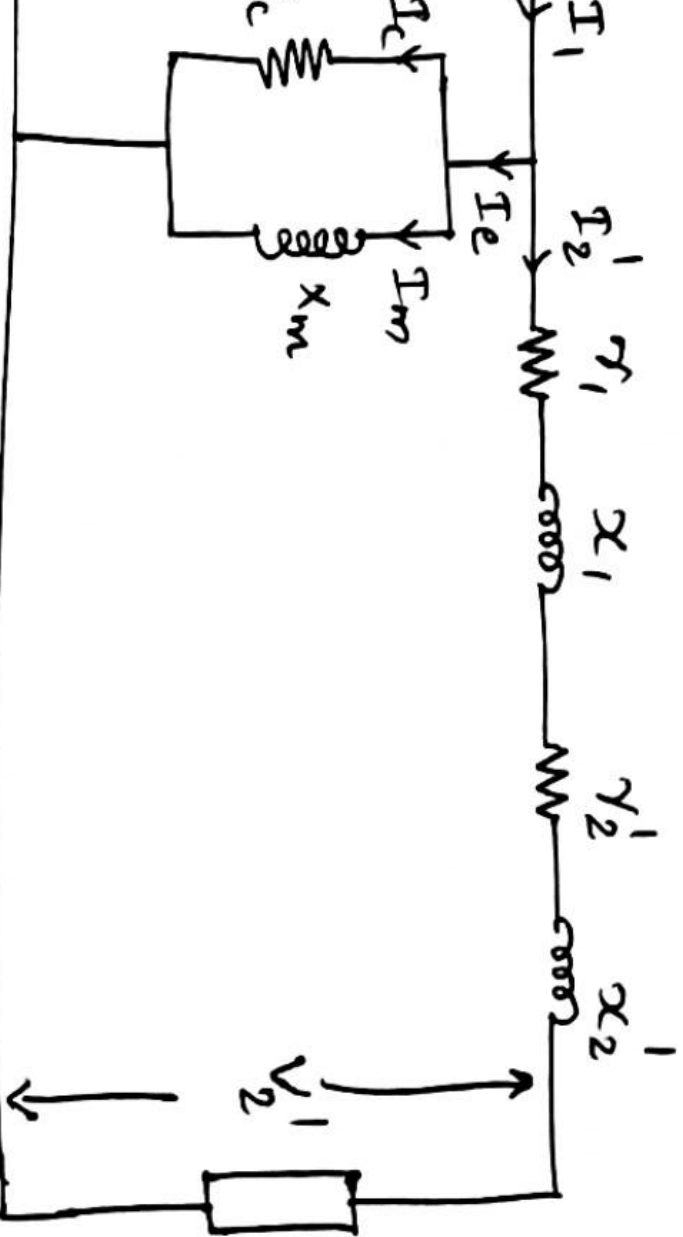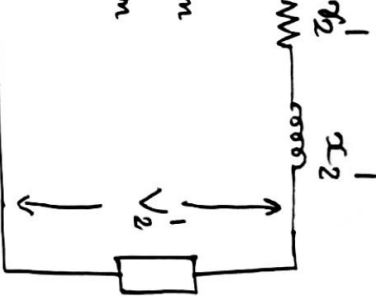


Equivalent Circuit referred to Primary

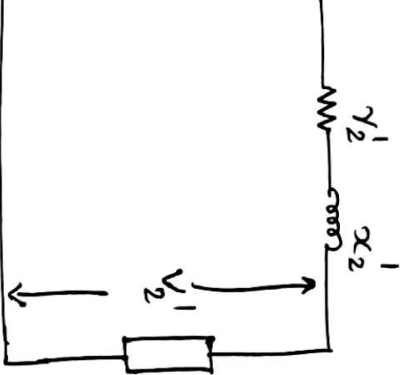


$$r_{01} = r_1 + r_2'$$

$$x_{01} = x_1 + x_2'$$

$$Z_{01} = \sqrt{r_{01}^2 + x_{01}^2}$$

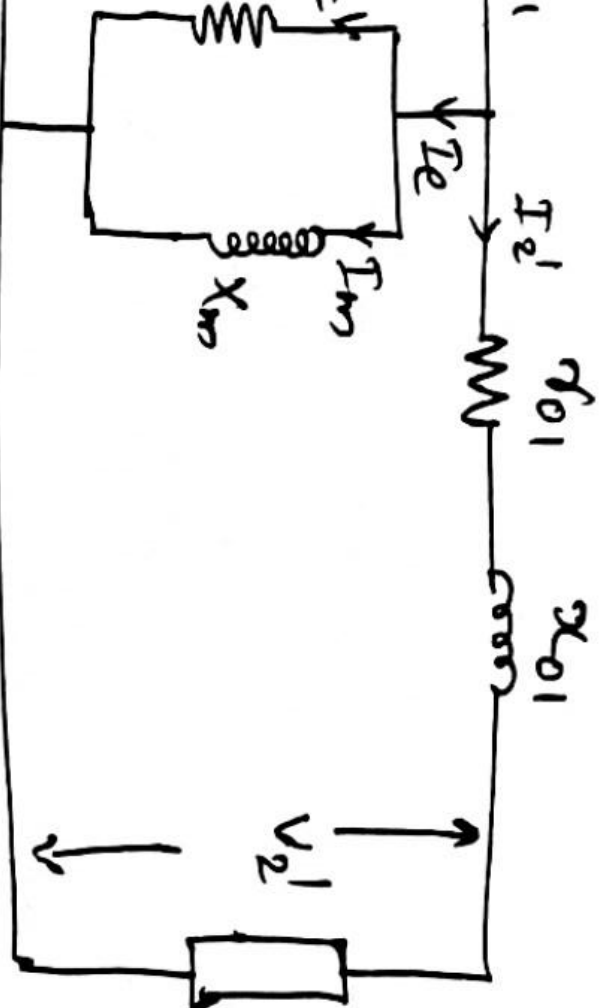

Equivalent Circuit referred to Secondary

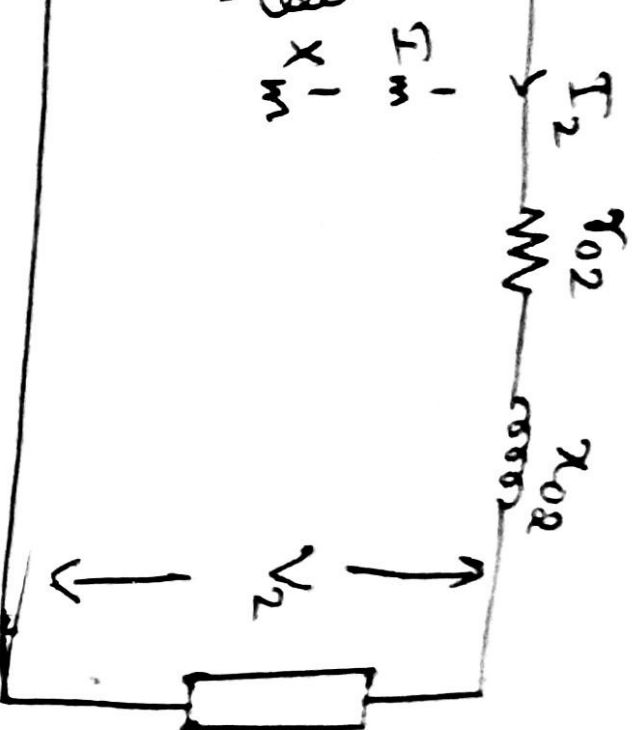

$$r_1' = K^2 r_1$$

$$x_1' = K^2 x_1$$

$$X_m' = K^2 X_m$$

$$R_c' = K^2 R_c$$

$$I_1' + r_2$$

$$I_1' + x_2$$

$$\sqrt{r_{02}^2 + x_{02}^2}$$

Losses and Efficiency

and with a transformer are:

Iron Losses)

S

Output / Input = (Input – Losses) / Input

n for Maximum Efficiency

$$= I_2^2 r_{02}$$

$$\frac{output}{input} = \frac{Input - Losses}{Input}$$

$$\frac{I_1 \cos \phi_1 - I_1^2 r_{01} - W_i}{V_1 I_1 \cos \phi_1}$$

$$\frac{I_1 \cos \phi_1}{I_1 \cos \phi_1} \quad \frac{I_1^2 r_{01}}{V_1 I_1 \cos \phi_1} \quad \frac{W_i}{V_1 I_1 \cos \phi_1}$$

$$\frac{I_1 r_{01}}{V_1 \cos \phi_1} \quad \frac{W_i}{V_1 I_1 \cos \phi_1}$$

η for Maximum Efficiency

η respect to I_1

$$\frac{d\eta}{dI_1} = 0 - \frac{r_{01}}{V_1 \cos \phi_1} + \frac{W_i}{V_1 I_1^2 \cos \phi_1}$$

Efficiency, $\frac{d\eta}{dI_1} = 0$

$$\frac{r_{01}}{V_1 \cos \phi_1} = \frac{W_i}{V_1 I_1^2 \cos \phi_1}$$

$$I_1^2 r_{01} = W_i$$

$$Cu \text{ loss} = Core \text{ loss}$$