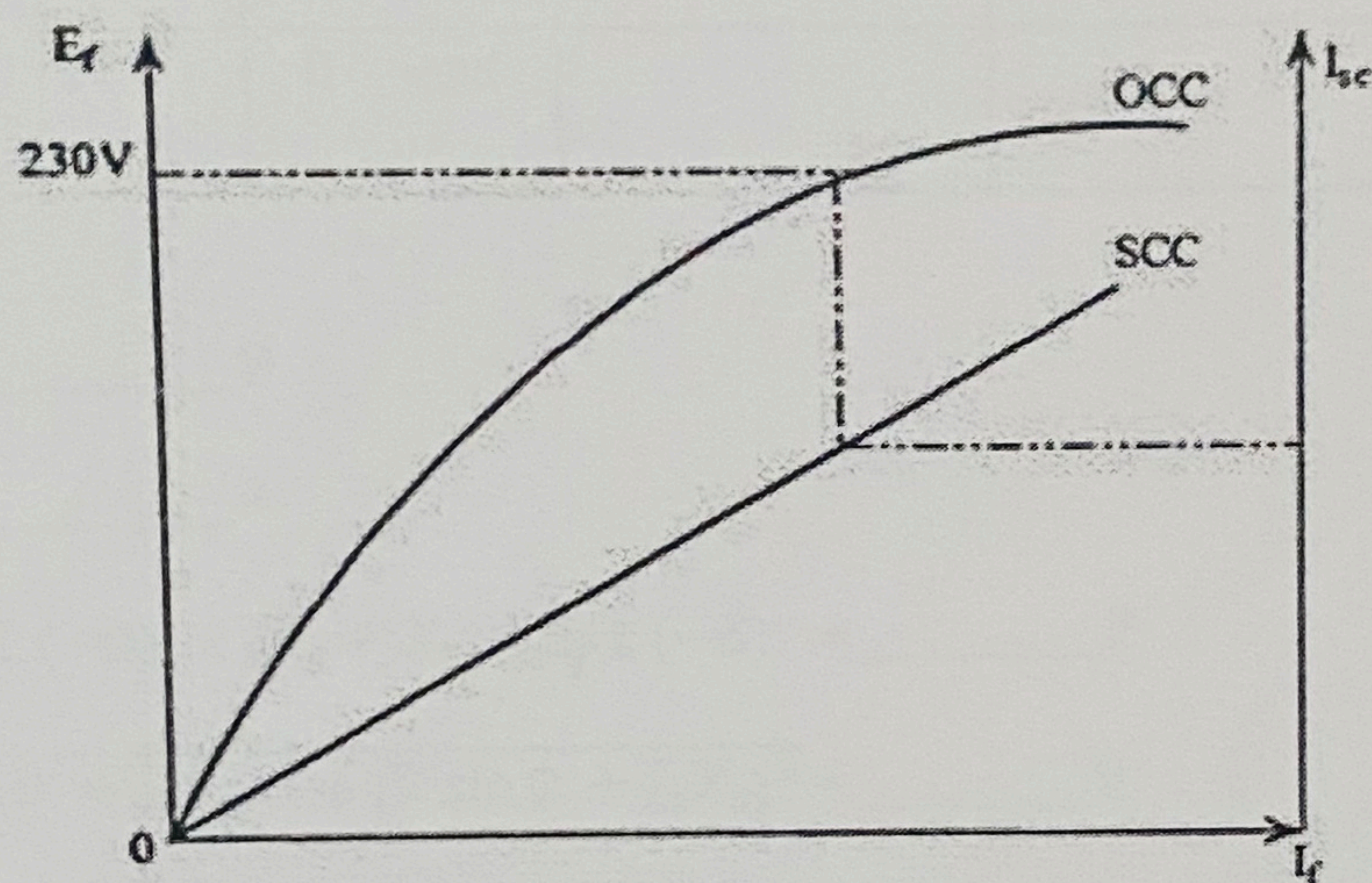




Rdc

SAMPLE CALCULATIONEMF METHODRated voltage/phase $V = 230V$ Short circuit current corresponding to rated voltage from SCC, $I_{sc} = \dots\dots\dots A$ Synchronous impedance, $Z_s = \frac{V}{I_{sc}} = \dots\dots\dots \Omega$ Armature resistance, $R_a = 1.2 \times R_{dc} = \dots\dots\dots \Omega$ Synchronous reactance, $X_s = \sqrt{Z_s^2 - R_a^2} = \dots\dots\dots \Omega$ **SAMPLE CALCULATION**

Regulation at full load and ____ power factor lag

Full load current = ____ $V =$ ____ $X_s =$ ____ Ω $R_a =$ ____ Ω $\cos \phi =$ ____ lag

EMF METHOD			
SI No	pf	Full load $I_a =$ ____ A	
		Ef	Regulation
1	0 lag		
2	0.2 lag		