Circuit Diagram

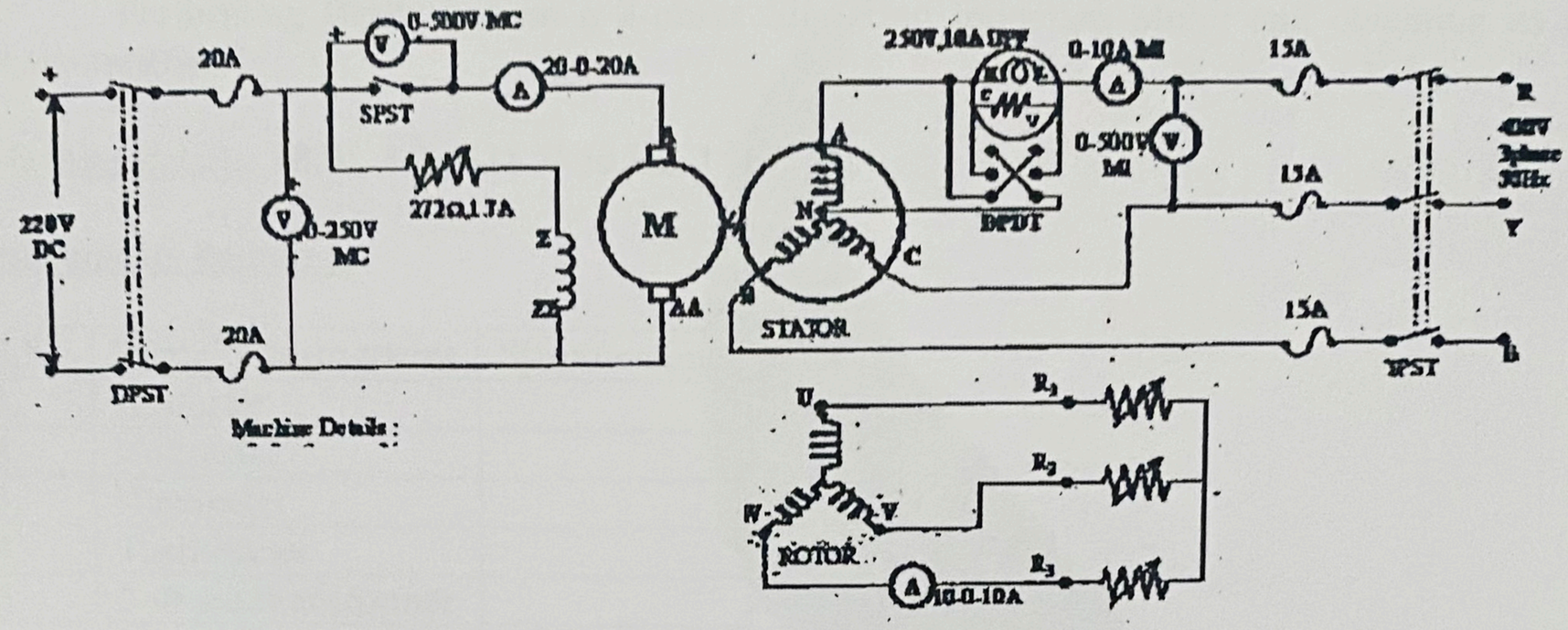


Observations

Induction Machine as Motor

| Vdc | Idc | Vac | Iac | W | 3 Phase power | Time for 10 rev | Rotor frequency | Slip % | Speed | O/p | I/p | Efficiency % |
|---|---|---|---|---|---|---|---|---|---|---|---|---|
| | | | | | | | | | | | | |
| | | | | | | | | | | | | |

Induction Machine as Generator

| Vdc | Idc | Vac | Iac | W | 3 Phase power | Time for 10 rev | Rotor frequency | Slip % | Speed | O/p | I/p | Efficiency % |
|---|---|---|---|---|---|---|---|---|---|---|---|---|
| | | | | | | | | | | | | |

Sample Calculation

Rotor frequency, f2 = 10 /T = _____ Hz

Input= 3 Wph = _____ W

Output = Vdc * Idc = _____ W

% Slip = f2f *100 = _____ %

Speed = Ns(1-s) = _____rpm

Efficiency = outputinput * 100