CIRCUIT DIAGRAM

LOAD TEST ON THREE PHASE SLIP RING INDUCTION MOTOR

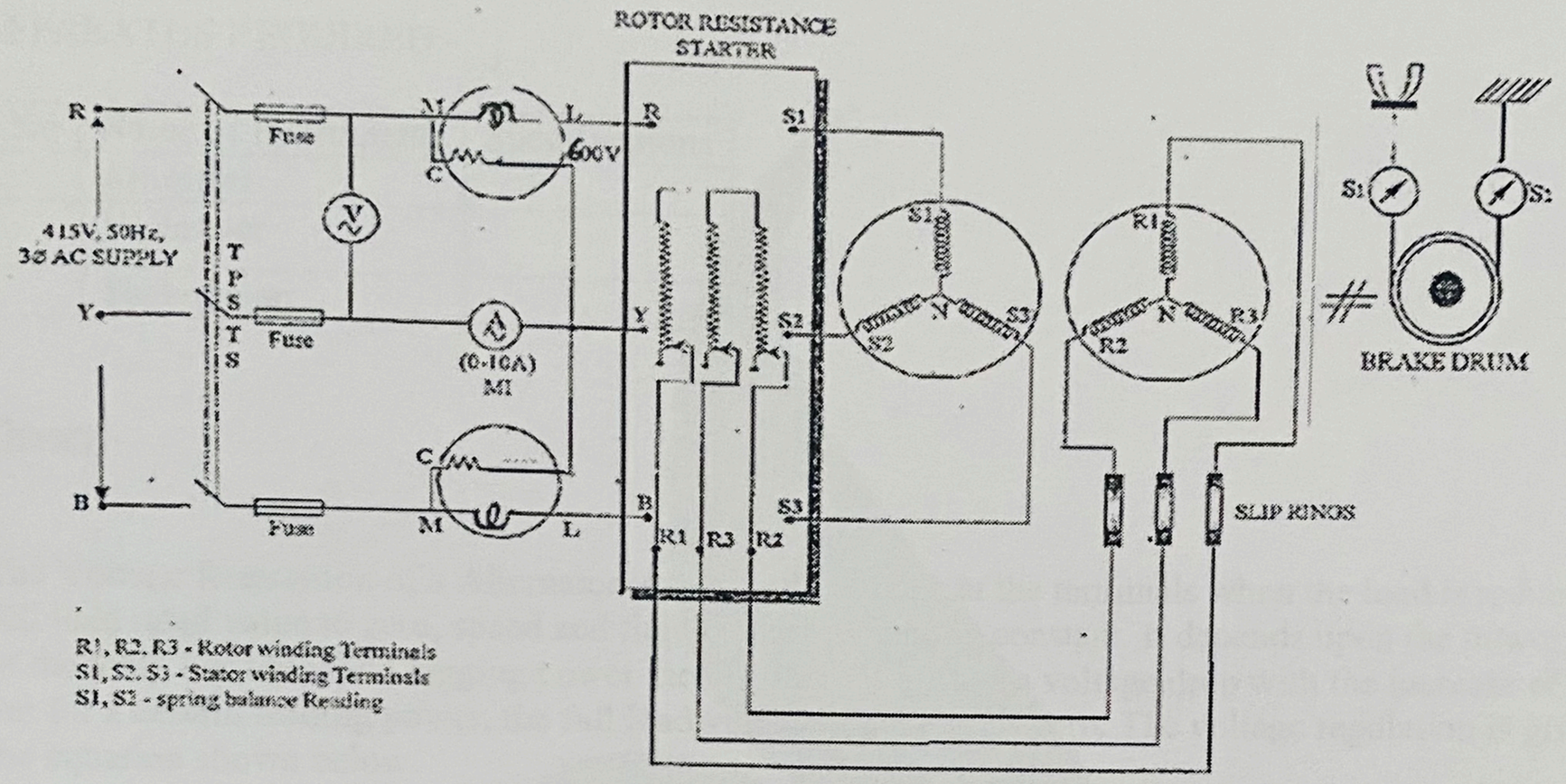

TABULATION FOR LOAD TEST ON THREE PHASE SLIP RING INDUCTION MOTOR

S.No	Load Current (I_L)	Load Voltege (V_L)	Wattmeter readings				Input power	Speed of the motor (N)	Spring balance reading			Torque (T) (S1~S2) (R*1/2) (9.81)	Output power 2πNT/60	Efficiency (η) o/p / i/p x100	Slip (S) $(N_s-N)/N_s$ x100	Power Factor ($\cos\phi$) i/p / $\sqrt{3}\,V_L I_L$
			W1		W2		W1+W2		S1	S2	S1~S2					
			Obs	Act	Obs	Act										
	Amps	Volts	Watts				Watts	rpm	Kg	Kg	Kg	N-m	Watts	%	%	